



University of  
**Nottingham**

UK | CHINA | MALAYSIA

# LECTURE 1B

## Electrical Engineering Fundamentals

### Electromechanical Devices MMME2051

Module Convenor – Surojit Sen



- What is **Engineering**?
  - **Mechanical**
  - **Electrical** – sub-branch **Electronic engineering**
  - **Electromechanical**
  - **Computer/Software**
- Fundamentals of **Electrical Engineering**
  - **Charge, Current, Voltage** – concept of **Across & Through** variables
  - Resistance & **Ohm's Law**
  - Kirchhoff's Current Law (**KCL**) & Kirchhoff's Voltage Law (**KVL**)
  - **Power & Energy**
- Electrical **energy storage** devices – **Reactive** elements
  - **Capacitor**
  - **Inductor**



# What is Engineering?

**“Creative application of scientific principles to design or develop structures, machines, apparatus, processes; utilising them singly or in combination”**


Derived from *ingenium*, meaning “**cleverness**”, and *ingeniare*, meaning “to **contrive, devise, fabricate, invent, build**”

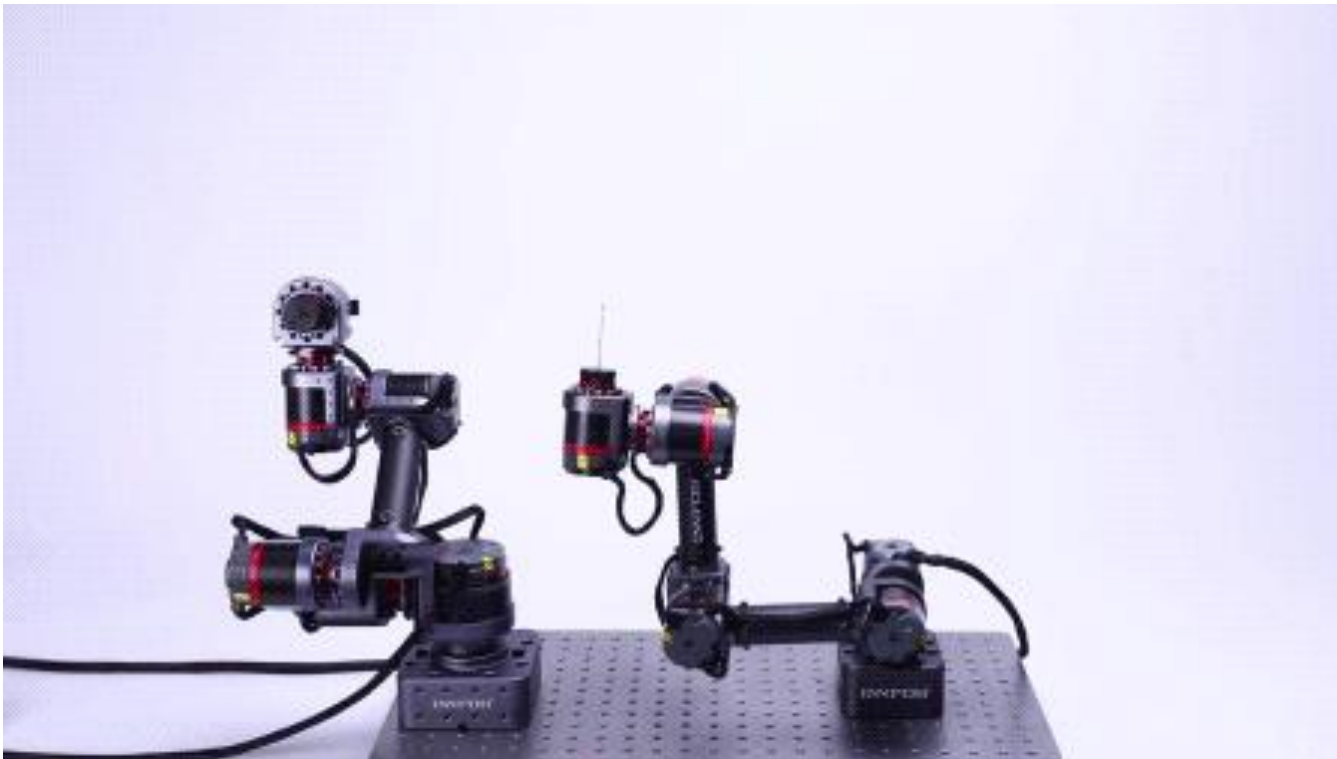**“Put together a bunch of things to do some form of useful work”**





Study of **physical machines** that may involve **force** and **motion/movement**




TurboCAD AnimationLab





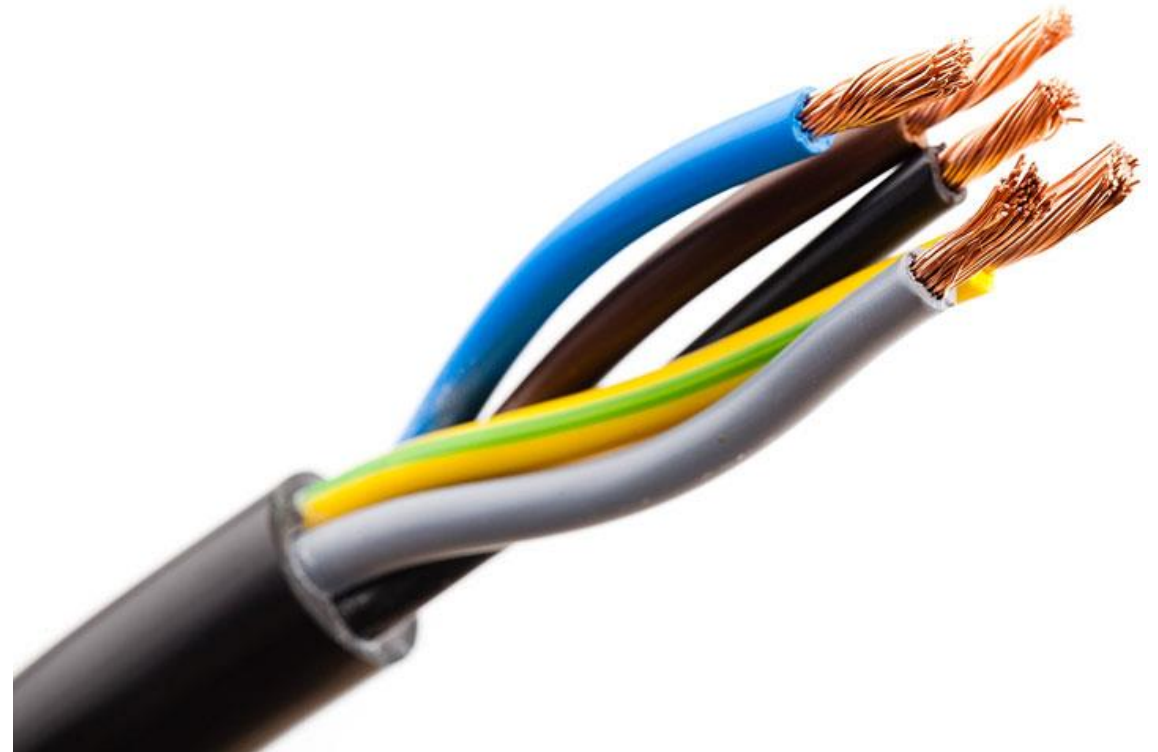Study and application of devices that use **electricity** and **electromagnetism**






Electrical systems that deal with **less than 5V** and **50mA**

Electronics specifically employs **active devices** like **amplifiers** and **rectifiers**

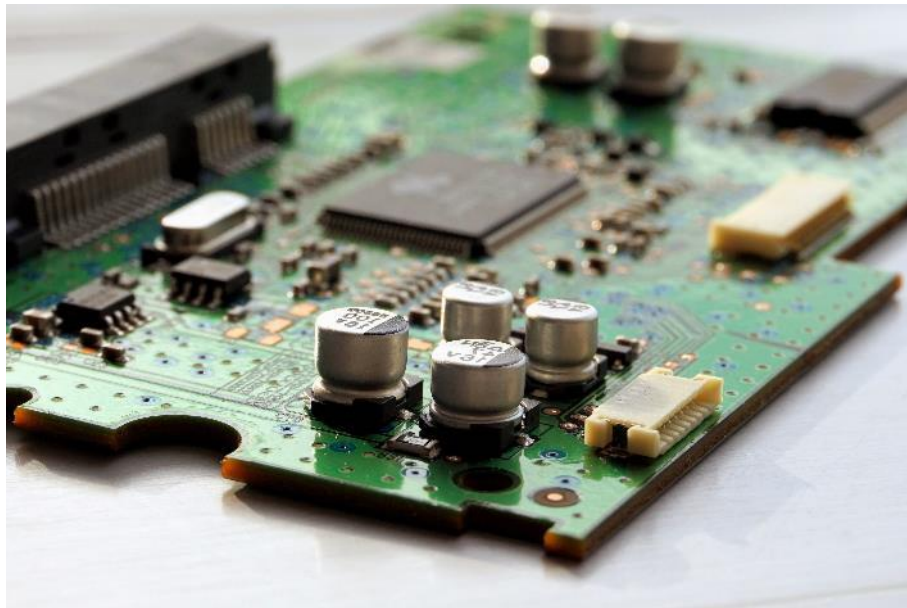Electronics with higher voltage/current and active devices are classed under **Power Electronics** – power converter in an electric car








Study of ways to use **electricity to turn or move something**, or use force or movement to **generate electricity**



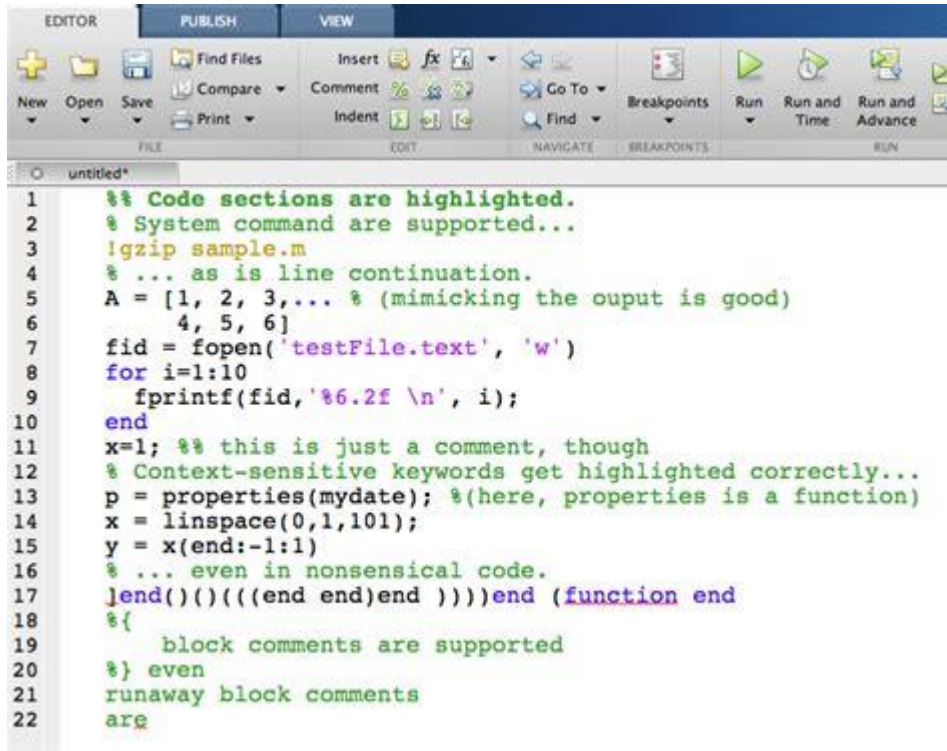**Systematic “writing” of “instructions”** to operate an electronic system like a **computer** to do a specific set of tasks in a downstream system




```
1 %% Code sections are highlighted.
2 % System command are supported...
3 !gzip sample.m
4 % ... as is line continuation.
5 A = [1, 2, 3,... % (mimicking the output is good)
6      4, 5, 6]
7 fid = fopen('testFile.text', 'w')
8 for i=1:10
9     fprintf(fid,'%6.2f \n', i);
10 end
11 x=1; %% this is just a comment, though
12 % Context-sensitive keywords get highlighted correctly...
13 p = properties(mydate); %(here, properties is a function)
14 x = linspace(0,1,101);
15 y = x(end:-1:1)
16 % ... even in nonsensical code.
17 |end()(((end end)end ))))end (function end
18 %{
19     block comments are supported
20 %} even
21 runaway block comments
22 are
```

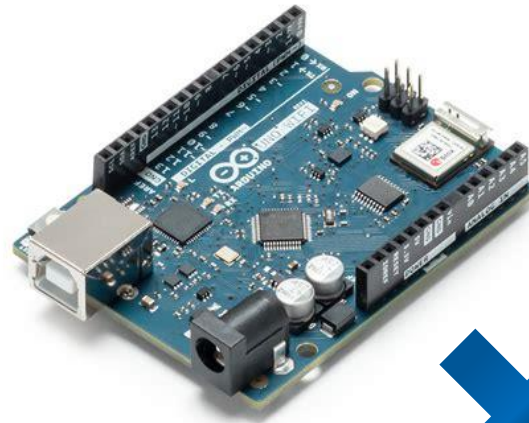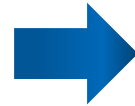




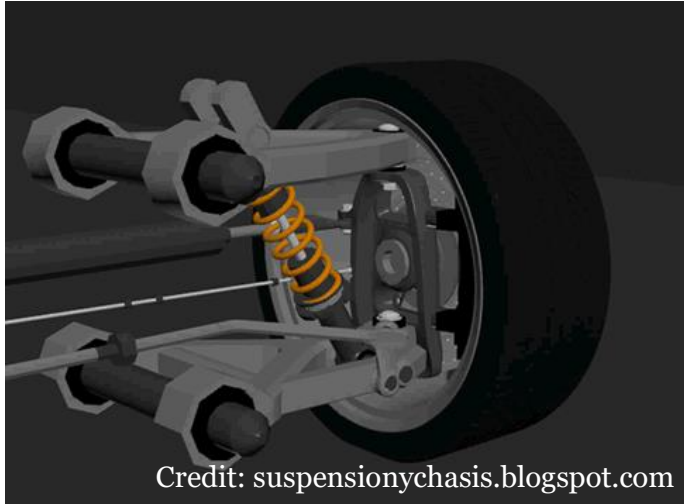
# Engineering Application – Tesla Model S



Credit: suspensionychasis.blogspot.com

Suspension & chasses  
**Mechanical Engineering**



Credit: pinterest.com

**Vehicle Control Unit (VCU)** that sends signals/commands to drive/stop the car  
**Electronic Engineering**

Code written to program the VCU  
**Computer/Software Engineering**




Credit: tesla.com



**Motor** that converts electrical power from battery to mechanical motion  
**Electromechanical Engineering**

**Battery** that supplies power to drive the motor  
**Electrical Engineering**

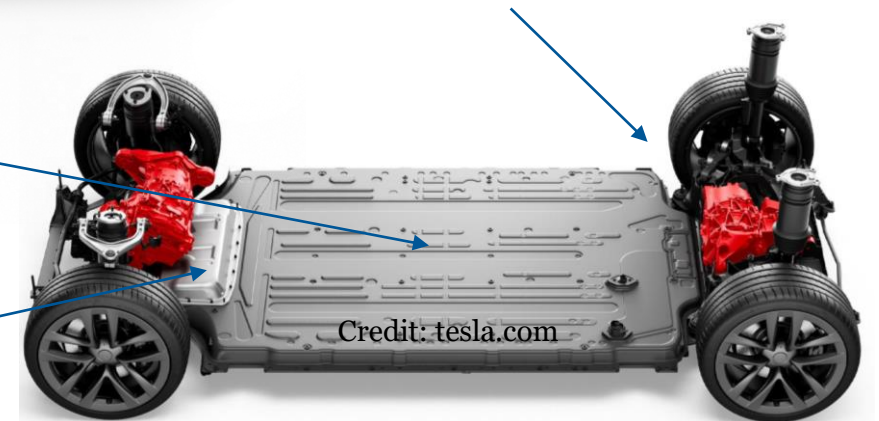
**Power Converter** that controls the flow of electrical power between battery and motor  
**Power Electronics**



Credit: tesla.com



- What is **Engineering**?
  - **Mechanical**
  - **Electrical** – sub-branch **Electronic engineering**
  - **Electromechanical**
  - **Computer/Software**
- Fundamentals of **Electrical Engineering**
  - **Charge, Current, Voltage** – concept of **Across & Through** variables
  - **Resistance & Ohm's Law**
  - **Kirchhoff's Current Law (KCL) & Kirchhoff's Voltage Law (KVL)**
  - **Power & Energy**
- **Electrical energy storage** devices – **Reactive** elements
  - **Capacitor**
  - **Inductor**

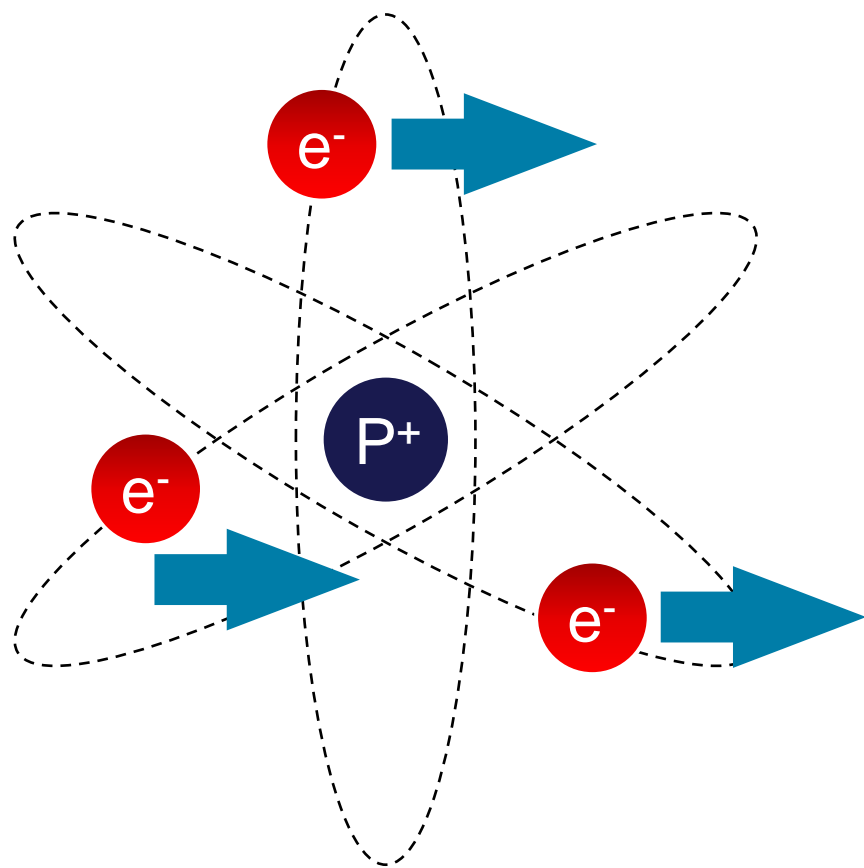


Is it the **electrons**?  
No, electrons are everywhere!

Is it **free** electrons?  
No, **free electrons** are present in electrical  
**conductors**, like all metals you see  
around.

**A cumulative flow of electrons in a particular direction consistently, is electricity!**



# Charge

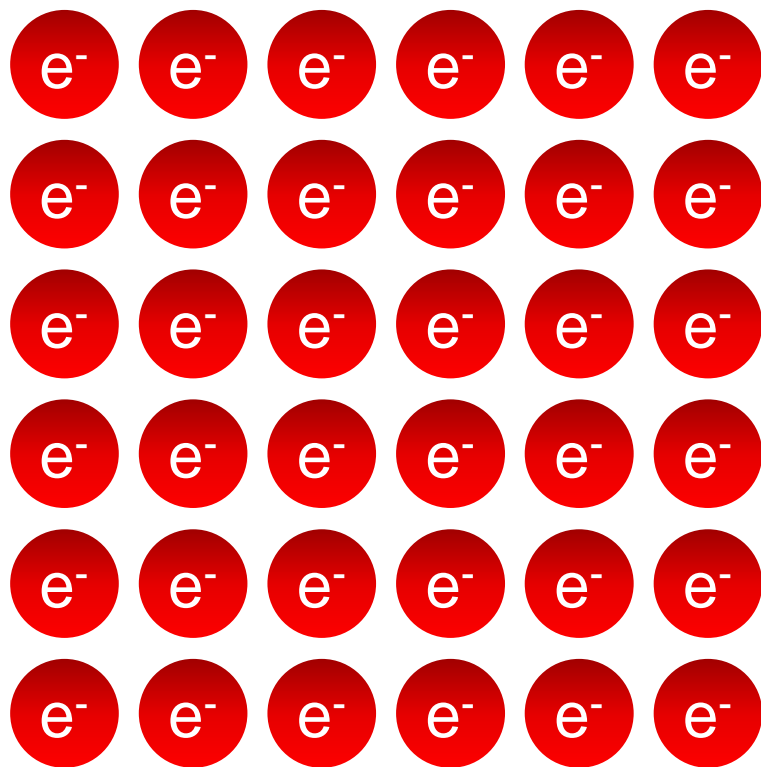

An electron has a charge of  
 $-1.6022 \times 10^{-19} \text{ C}$  (coulomb)




*Charles-Augustin de Coulomb*, French engineer who did some studies to figure out the force of attraction/repulsion between charged particles in late 1700s. The SI unit is named after him.

If there were  $\frac{1}{1.6022 \times 10^{-19}} = 6.2 \times 10^{18}$  electrons together, they would hold  $-1\text{C}$  charge

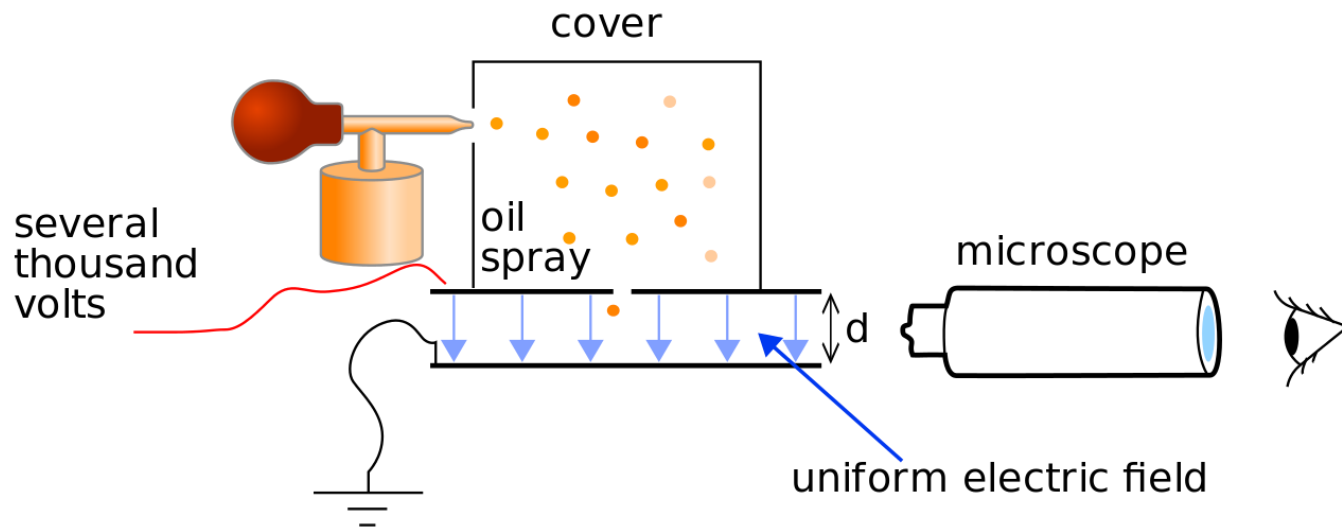
## A quick worthwhile detour!

This scientist called *Rob Millikan* in early 1900s wanted to identify the charge of a single electron. The setup was very interesting!



- A mist of **aerosolised oil droplets** were ionised using X-Ray in the top chamber.
- An **electric field applied** and adjusted to **hold** the “charged clusters of electrons” dead in space.

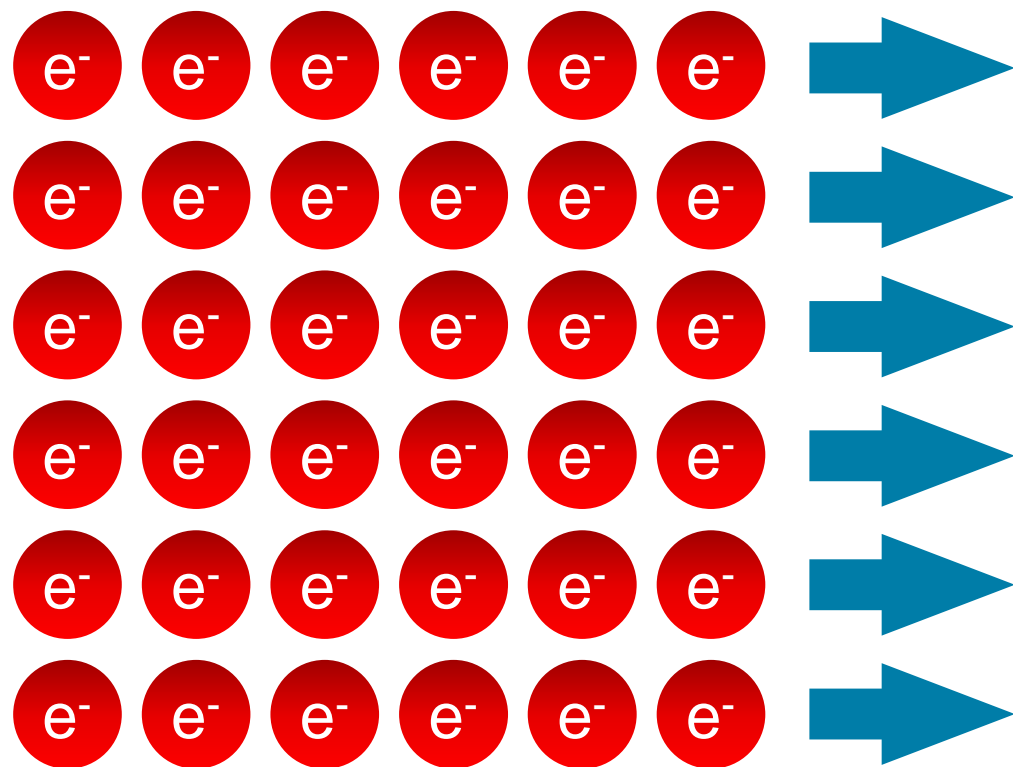It was deduced (with different field and charge settings) that all droplets were an **integral multiple of a single value**, i.e.,  $-1.6022 \times 10^{-19} \text{ C}$




When **1C** of charged particles cumulatively pass through a surface area every second, that is **1A (ampere) of current**



*André-Marie Ampère*, French physicist and mathematician conducted groundbreaking experiments with Danish physicist *Hans Christian Ørsted* to bring together electricity and magnetism in early 1800s.

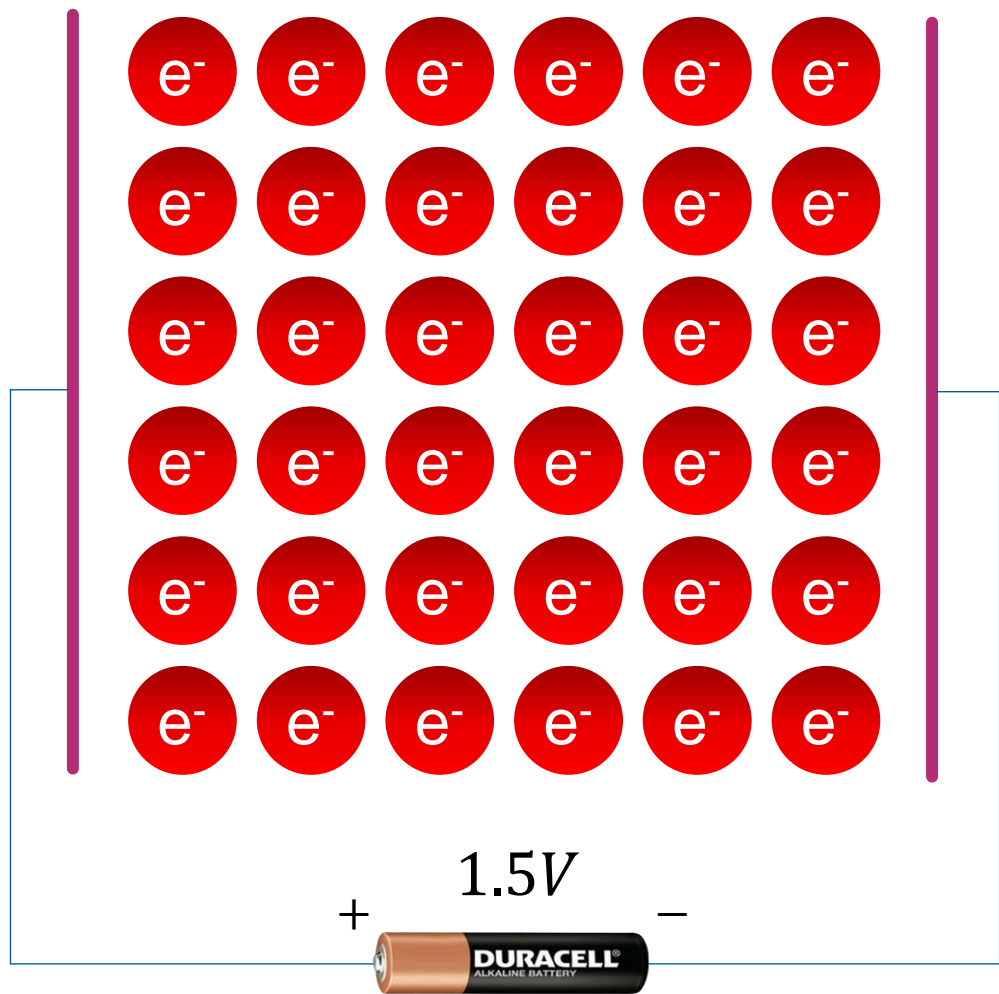If  $6.2 \times 10^{18}$  electrons moved together from **left to right**, we would say 1A current is flowing **right to left** (notice the polarity of an electron!)



So how can we **push these electrons** to create current?

We do so by creating a **potential difference** between two points, or **voltage** (between two points)



*Alessandro Volta*, Italian physicist and chemist was the inventor of the first battery in 1800. He was the pioneer of the novel field of electrochemistry.

Think of voltage as **electric pressure**  
The battery is an **electric pump**



**Volume of Water**  
(Litre)

**Charge**  
(Coulomb)



<http://waterengnet.com>

**Flow Rate of Water**  
(Litre/sec)

**Current**  
(Ampere)




**Water Pressure**  
(Pascal)

**Voltage**  
(Volt)



# Electric-Hydraulic Analogy

Mechanical work done

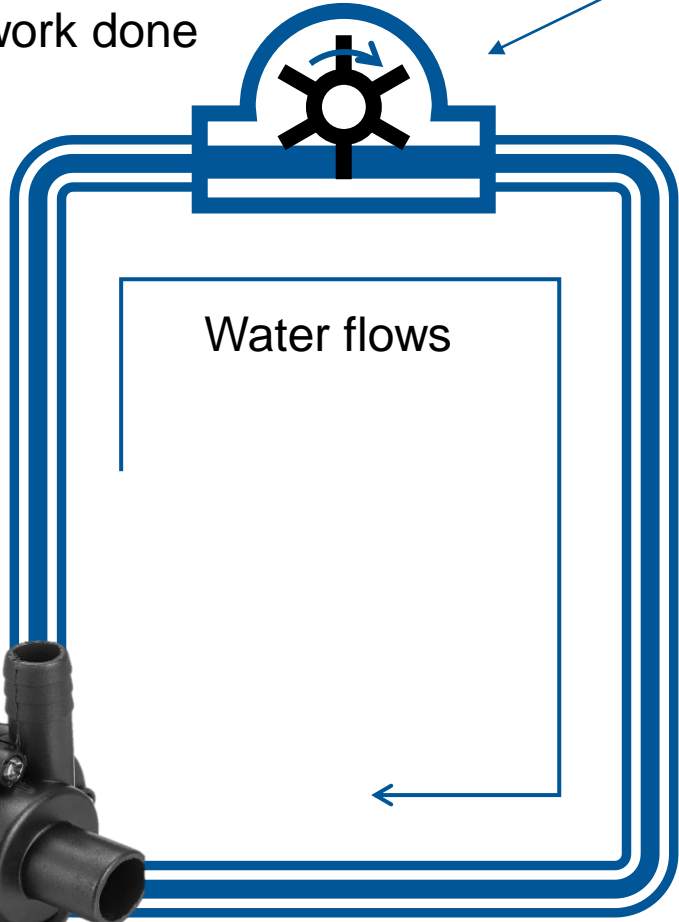

Water Pressure applied




Pipe filled with water

What is this new thing?

This is **impedance**, something that **hinders** or **impedes** the **flow** of water/electrons

*Nothing is free! If you want some work done (turbine turned or lightbulb lit), you need to apply pressure/volts!*

Bulb lights up

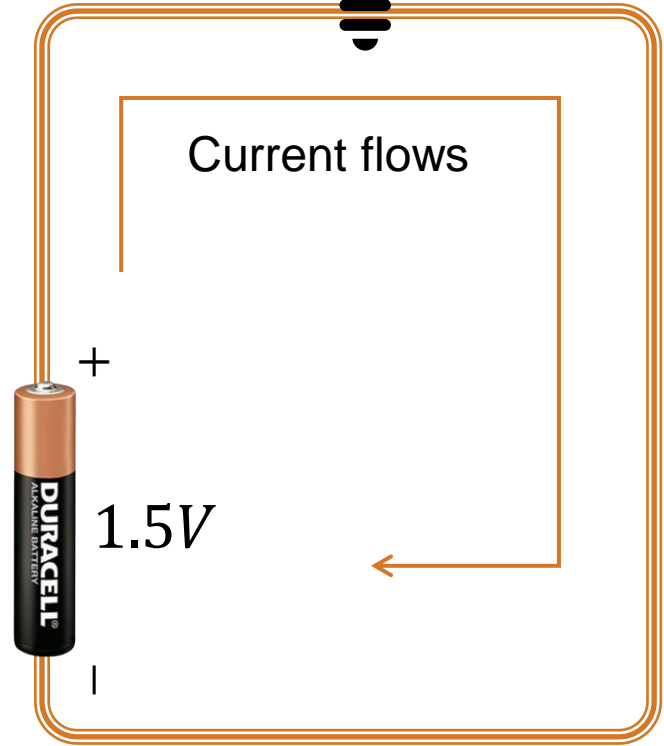

Voltage applied

1.5V

Copper wire (filled with electrons!)

## Across Variable

Appears **across the two terminals** of an element

Measured **relative to a reference** point

“Pressure applied by the water pump is 25 Pascals (at the outlet w/r/t inlet)”

“I am driving on the highway at 60 mph (w/r/t the ground)”

“This battery when fully charged applies 1.5 Volts (at the + terminal w/r/t the – terminal)”

## Through Variable

**Passes through**, or acts through an element

Value is **same at both terminals** of the element

“10 L/min of water is flowing through the water pipe”

“I am applying a force of 100 N”

“There is 5 Amperes of current flowing through the lightbulb”

We talked about **flow of charge** (current) as a consequence of application of a **potential difference** (voltage) **between two points**

Ask yourself, what defines **how much current** would flow when **an amount of voltage** is applied?

For all practical purposes, **voltage & current** follow a **linearly proportional** relationship

This is called the **Ohm's Law**





*Georg Simon Ohm*, German physicist began his research with Alessandro Volta's electrochemical cell in mid 1800s to define this law.

$$V \propto I$$

$$V = IR$$

Voltage
Current
Resistance

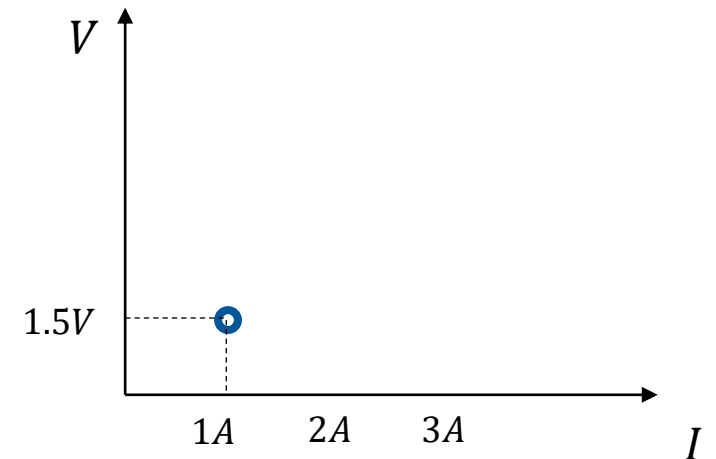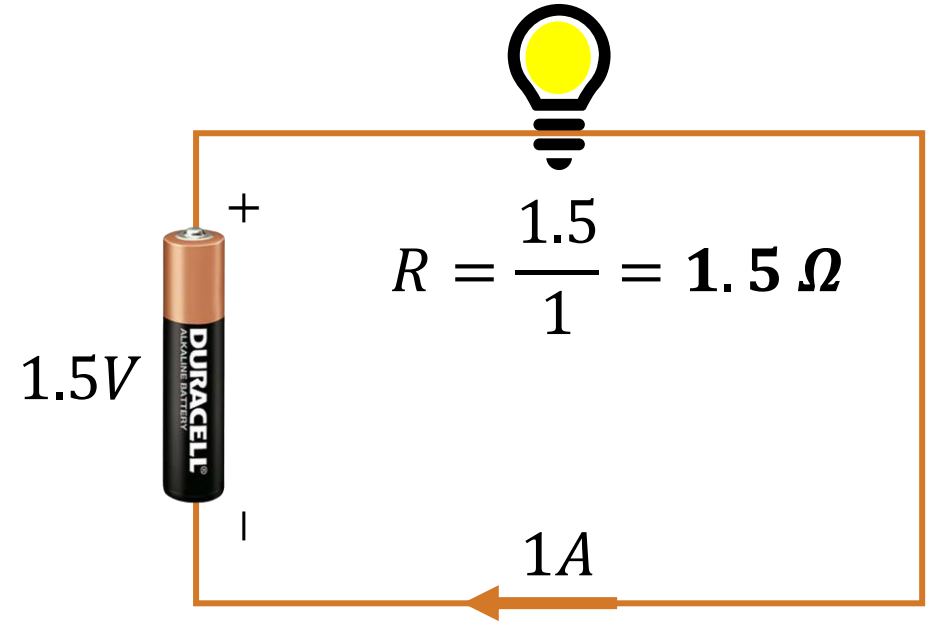

# Ohm's Law

We talked about **flow of charge** (current) as a consequence of application of a **potential difference** (voltage) **between two points**

Ask yourself, what defines **how much current** would flow when **an amount of voltage** is applied?

For all practical purposes, **voltage & current** follow a **linearly proportional** relationship

This is called the **Ohm's Law**





*Georg Simon Ohm*, German physicist began his research with Alessandro Volta's electrochemical cell in mid 1800s to define this law.

$$V \propto I$$

$$V = IR$$

Voltage
Current
Resistance

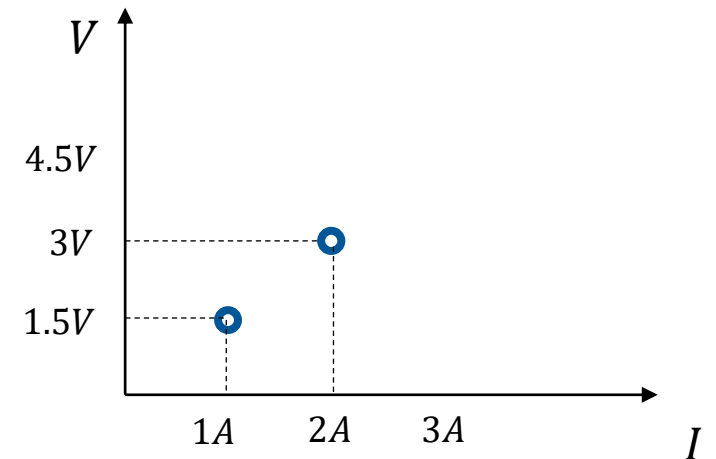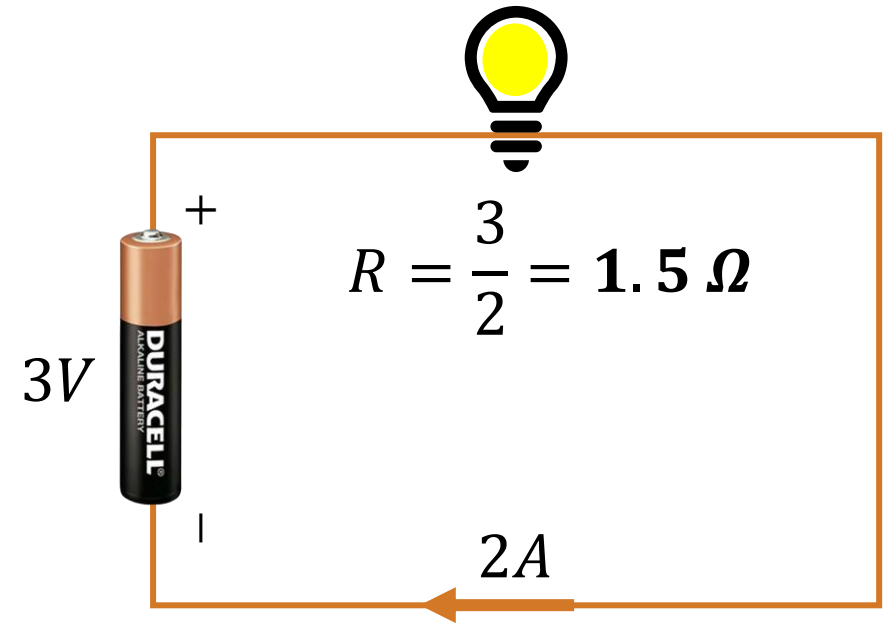

# Ohm's Law

We talked about **flow of charge** (current) as a consequence of application of a **potential difference** (voltage) **between two points**

Ask yourself, what defines **how much current** would flow when **an amount of voltage** is applied?

For all practical purposes, **voltage & current** follow a **linearly proportional** relationship

This is called the **Ohm's Law**





*Georg Simon Ohm*, German physicist began his research with Alessandro Volta's electrochemical cell in mid 1800s to define this law.

$$V \propto I$$

$$V = IR$$

Voltage
Current
Resistance

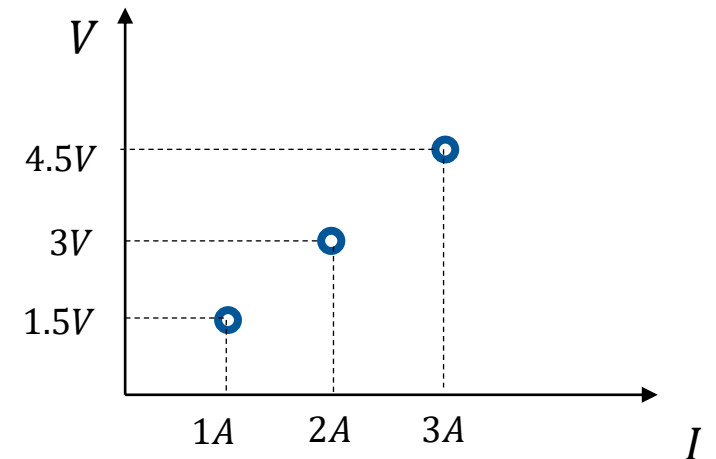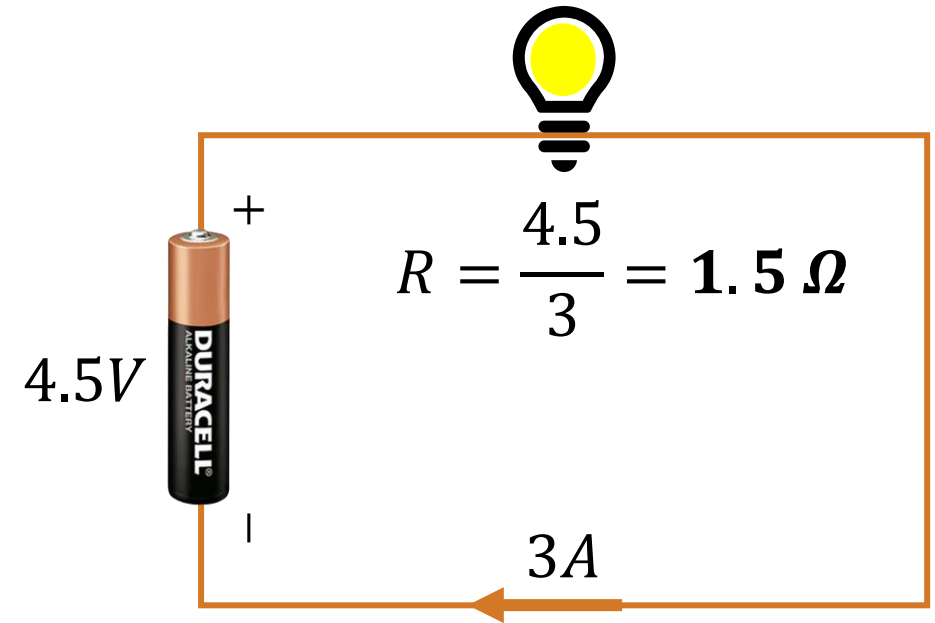

We talked about **flow of charge** (current) as a consequence of application of a **potential difference** (voltage) **between two points**

Ask yourself, what defines **how much current** would flow when **an amount of voltage** is applied?

For all practical purposes, **voltage & current** follow a **linearly proportional** relationship

This is called the **Ohm's Law**





*Georg Simon Ohm*, German physicist began his research with Alessandro Volta's electrochemical cell in mid 1800s to define this law.

$$V \propto I$$

$$V = IR$$

Voltage → Current → Resistance

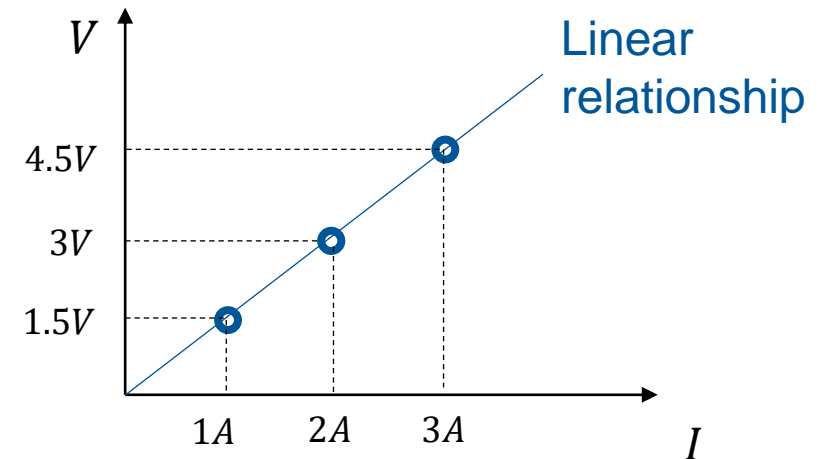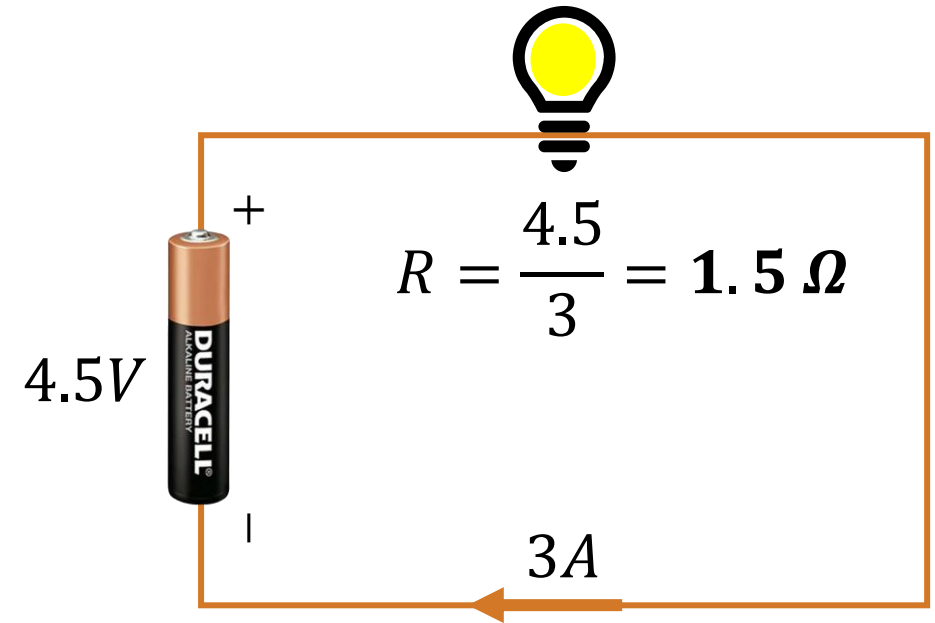




**Impedance** is the **generic** term, of which **Resistance** is a **special case**

**Impedance** is used when there **are energy storage elements** (like **capacitor** or **inductor** – we will discuss them in the next section) in the circuit

**Resistance** is used for non-energy-storage elements, like a **resistor**

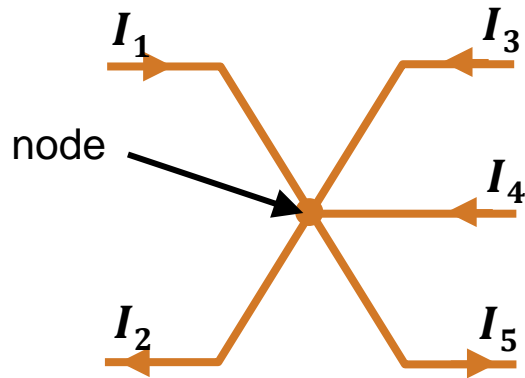
## Kirchhoff's Current Law

Algebraic sum of current entering a node is zero



$$I_1 + I_3 + I_4 = I_2 + I_5$$


$$I_1 - I_2 + I_3 + I_4 - I_5 = 0$$

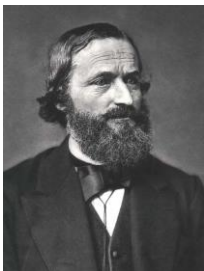

*Gustav Kirchhoff*, German physicist contributed to the fundamental understanding of electric circuits in mid 1800s. He also contributed to spectroscopy and black-body radiation.
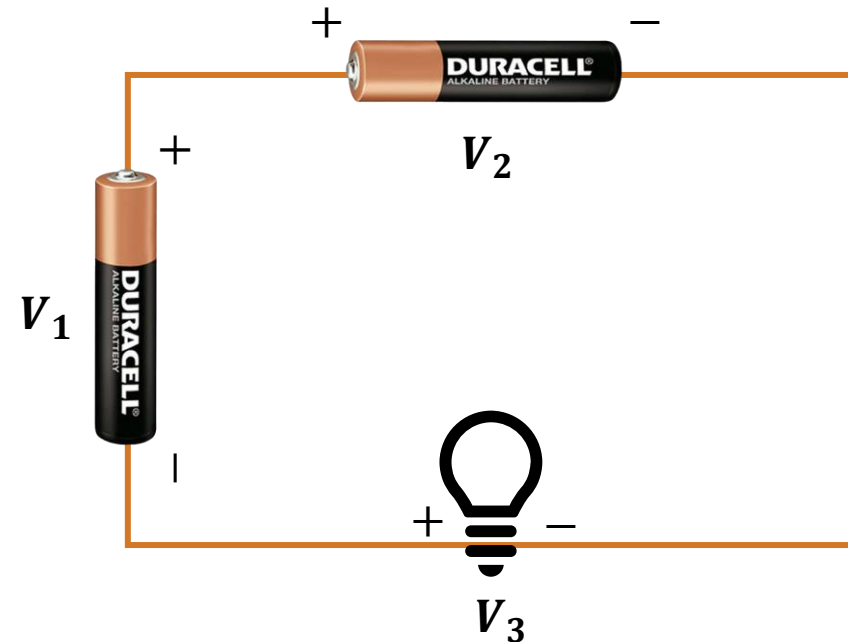
## Kirchhoff's Voltage Law

Algebraic sum of voltages around a closed loop is zero




$$V_1 - V_2 + V_3 = 0$$


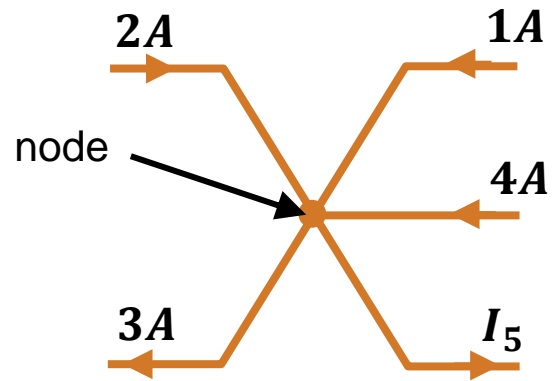
## Kirchhoff's Current Law


Algebraic sum of current entering a node is zero




$$2 - 3 + 1 + 4 - I_5 = 0$$

$$2 - 3 + 1 + 4 = I_5$$


$$4A = I_5$$

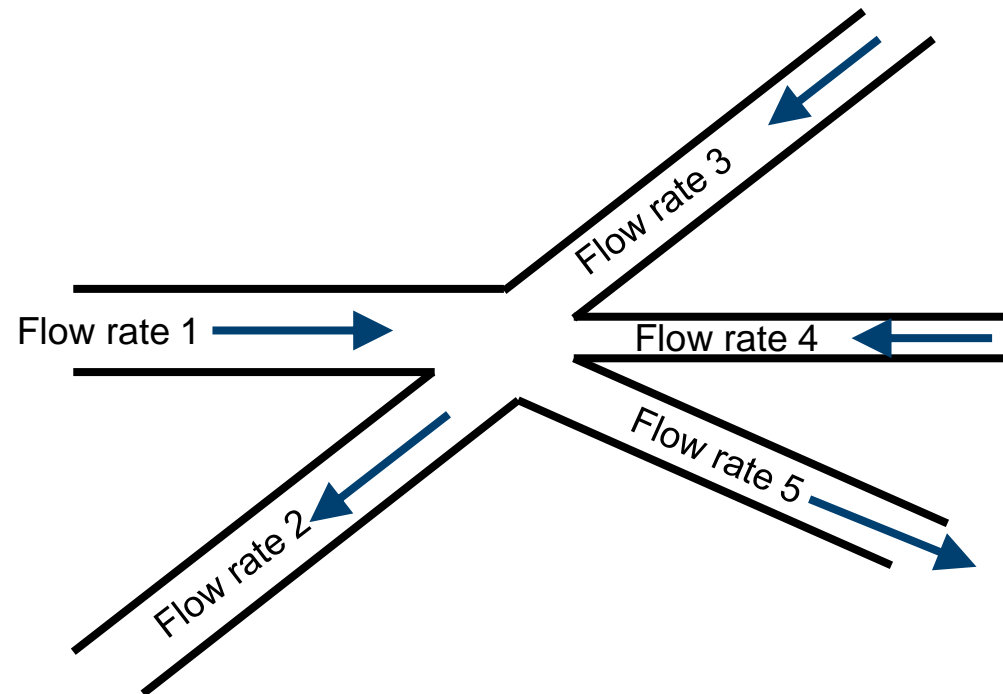

# Kirchhoff's Laws

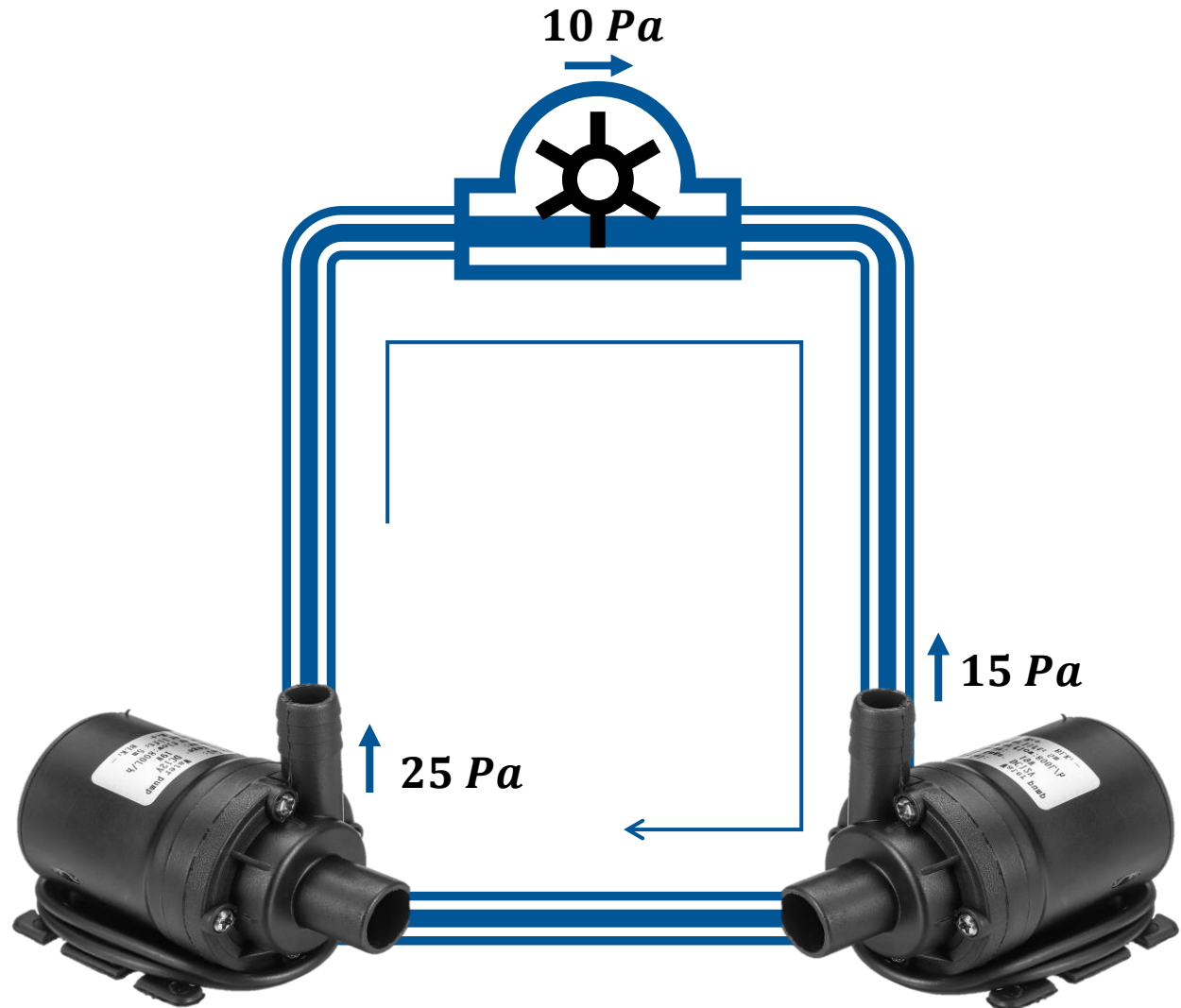

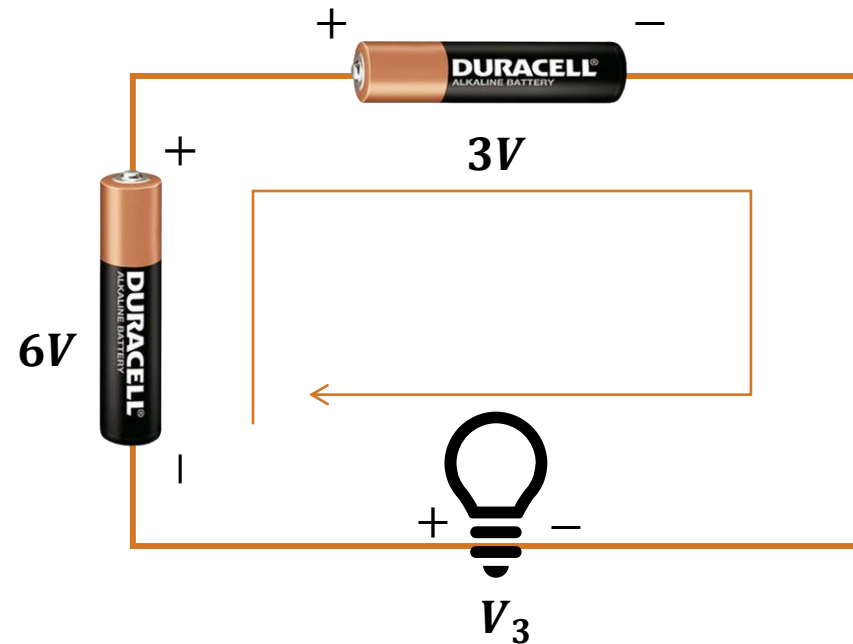**Kirchhoff's Voltage Law**  
Algebraic sum of voltages around a closed loop is zero



$$6 - 3 + V_3 = 0$$

$$V_3 = -3V$$

Indication of how much **electrical energy** has been produced/consumed/transferred over an **amount of time**

SI unit is **Joule (J)**, but **kilowatt-hour (kWh)** is widely used for practical purposes

**Energy consumed** translates to **Work done**, they have the same units

If a device (like battery, or generator) has pushed 5A of current at 10V in an electrical circuit for 10s, we say the device has pushed 500Wh of energy

$$E = 5A \times 10V \times 10s = 50W \times 10s = 500J$$



*James Prescott Joule*, English physicist discovered the relationship between heat and work in mid 1800s.

**Rate** of production/consumption/transmission of electrical energy

SI unit is **Watt** (W) that is Work done per unit time (**J/s**)

If a device (like battery) is pushing 5A of current at 10V in an electrical circuit, we say the device is producing 50W of power

$$P = 5A \times 10V = \mathbf{50W}$$

If a battery is not connected to any circuit, i.e., left open, it may have 5V across its terminals, but as **no current is flowing, power is zero**. Similarly, say there is 5A flowing in an electrical circuit, there is **zero power** in the copper cables as there is **no voltage across them**



*James Watt*, Scottish engineer invented the Watt steam engine by improving upon an earlier design in late 1700s.





- What is **Engineering**?
  - **Mechanical**
  - **Electrical** – sub-branch **Electronic engineering**
  - **Electromechanical**
  - **Computer/Software**
- Fundamentals of **Electrical Engineering**
  - **Charge, Current, Voltage** – concept of **Across & Through** variables
  - **Resistance & Ohm's Law**
  - **Kirchhoff's Current Law (KCL) & Kirchhoff's Voltage Law (KVL)**
  - **Power & Energy**
- **Electrical energy storing elements – Reactive elements**
  - **Capacitor**
  - **Inductor**
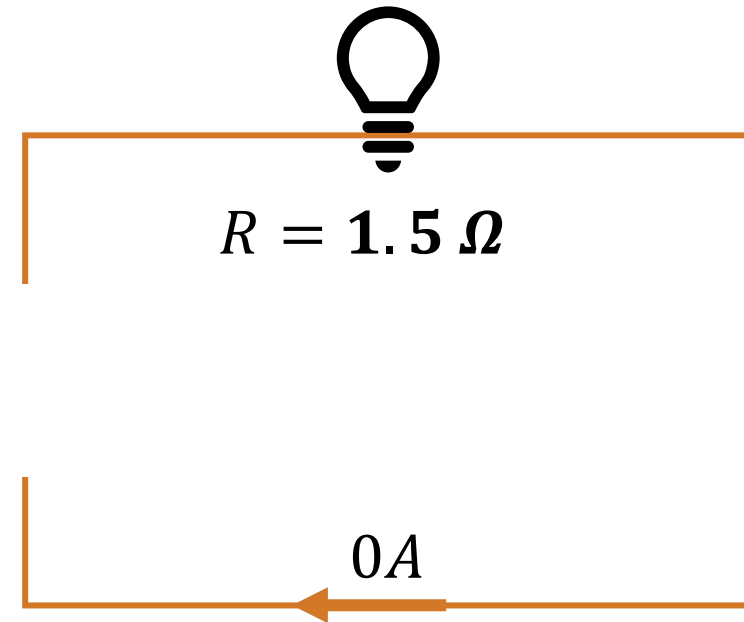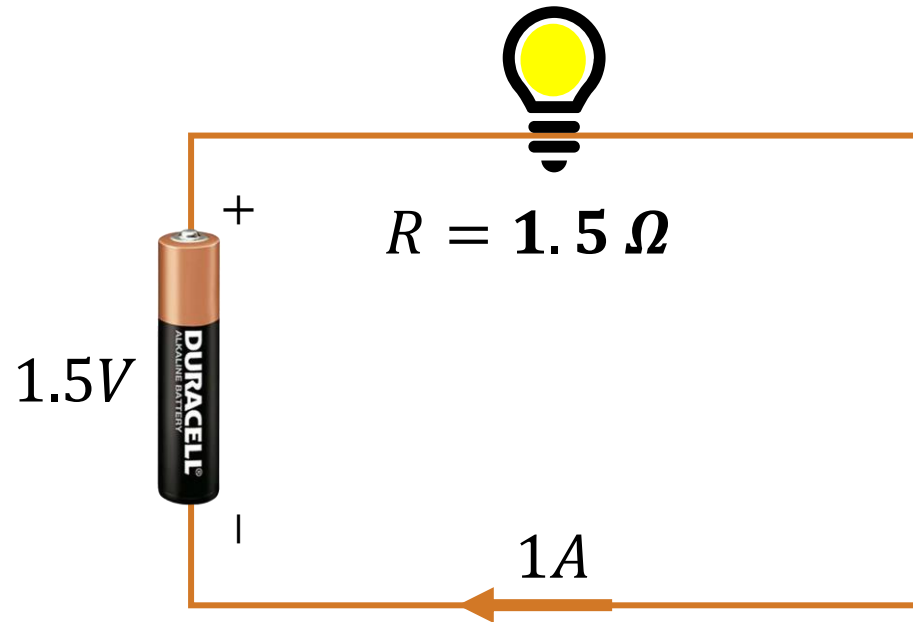
# Energy Storing Elements – Reactive Elements

So far, we have looked at a resistor. A **resistor responds instantaneously** to the **application of voltage** across it, by **allowing current to flow** (as per Ohm's Law)


If you **remove the voltage**, the **current flow immediately stops**.




There is another type of element, called **reactive element**, or **energy storing element**, that responds/behaves according to the **present AND the past!**

When you **apply voltage** to a reactive element, the reactive element **starts storing energy** (in various forms – discussed next) while allowing current to flow

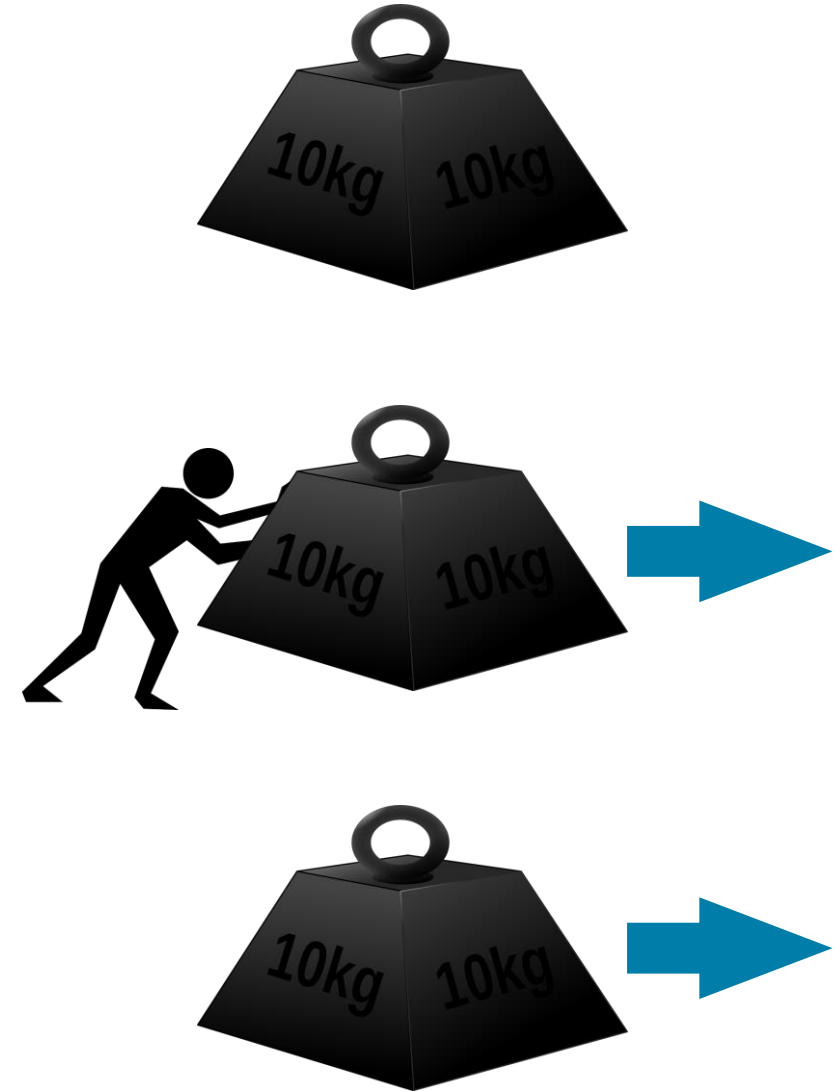
When you **remove the voltage**, the stored energy in it **still pushes current** until all the **stored energy is dissipated**



## Inductors

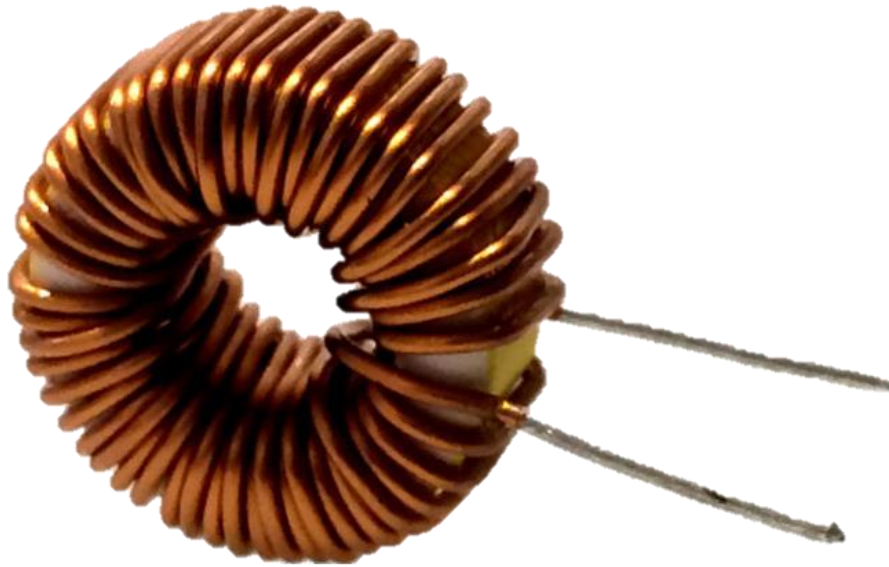


## Capacitors

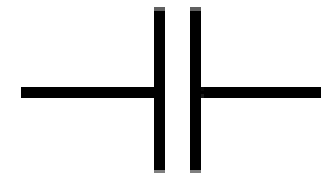





# Inductor

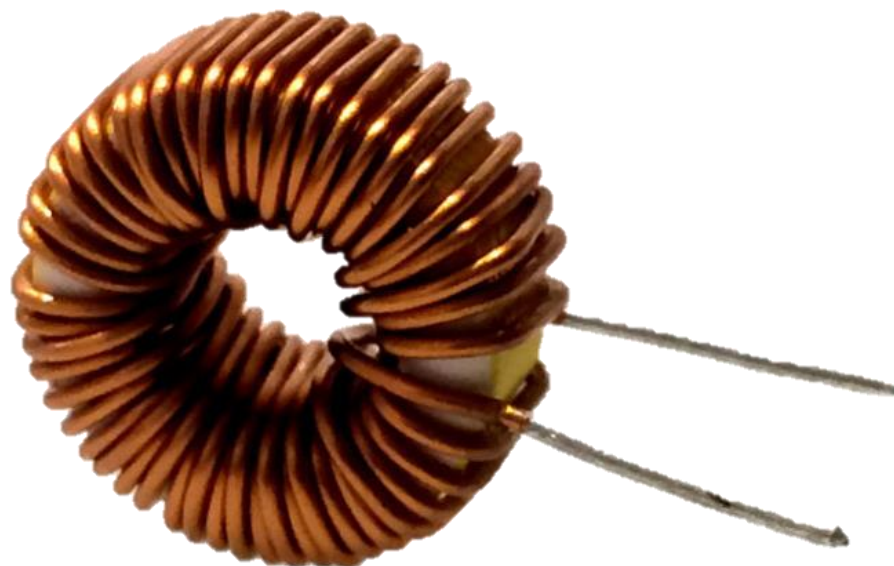

A coil of wire wound around a magnetic core like iron


They have a property called **Inductance** (SI unit: **Henry**, symbol **H**)

**Voltage** applied is proportional to **rate of change of Current** (unlike Ohm's law)

$$V \propto \frac{dI}{dt}$$
$$V = L \frac{dI}{dt}$$


Current in the coil (aided by the magnetic core) creates a magnetic field and hence magnetic flux

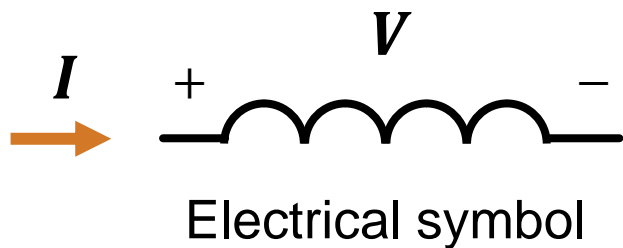Changing the magnetic flux in the coil induces a voltage that prevents the flux change






# Inductor

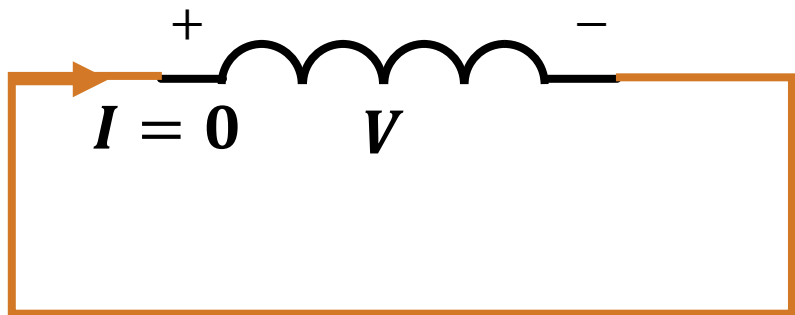

Inductor is discharged




Mass is stationary

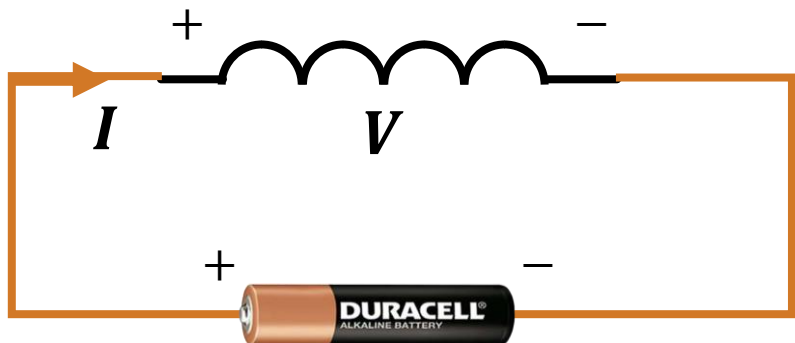

Voltage applied, Inductor current starts increasing



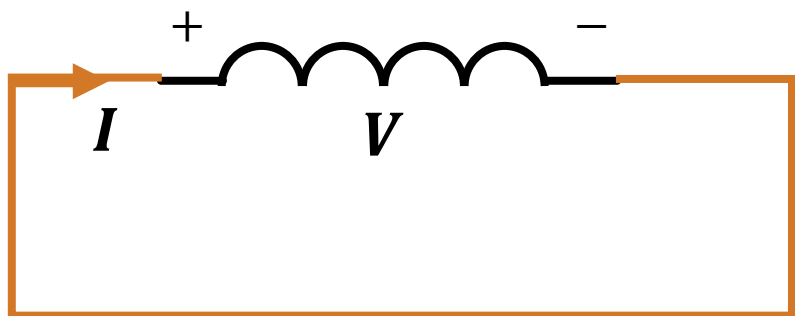Force applied, mass starts gaining velocity




Voltage removed, current starts declining and eventually stops due to magnetic leakage and tiny (but finite) resistance in copper wires



Force removed, mass slows down and stops eventually due to friction




# Inductor

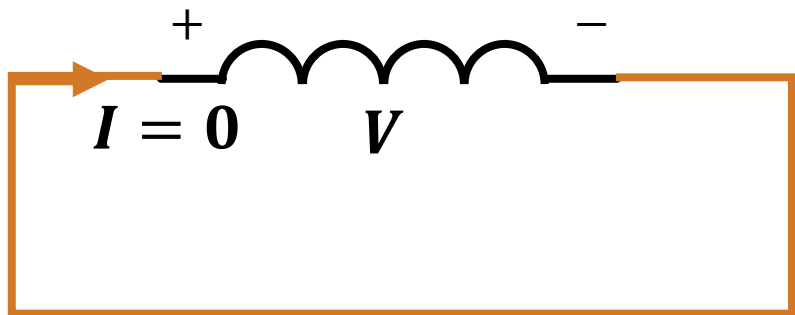

Inductor is discharged




Mass is stationary

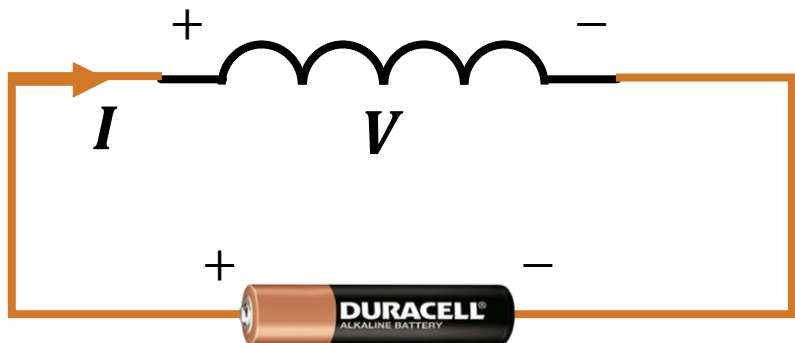


Voltage applied, Inductor current starts increasing



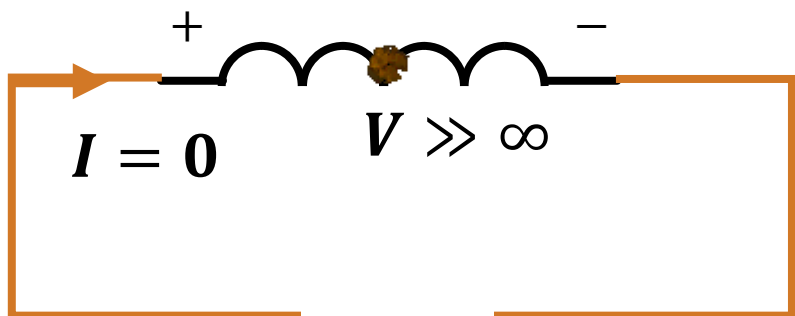Force applied, mass starts gaining velocity



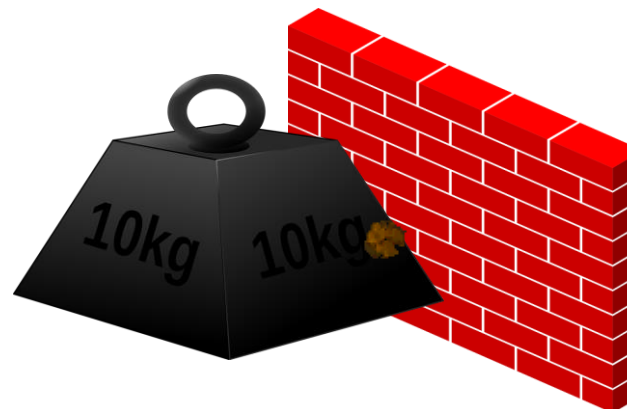Voltage removed and current path broken, i.e., open-circuit, near infinite voltage induced across coil to force current flow – **explosion** if high-enough energy was stored!






Unmovable brick wall
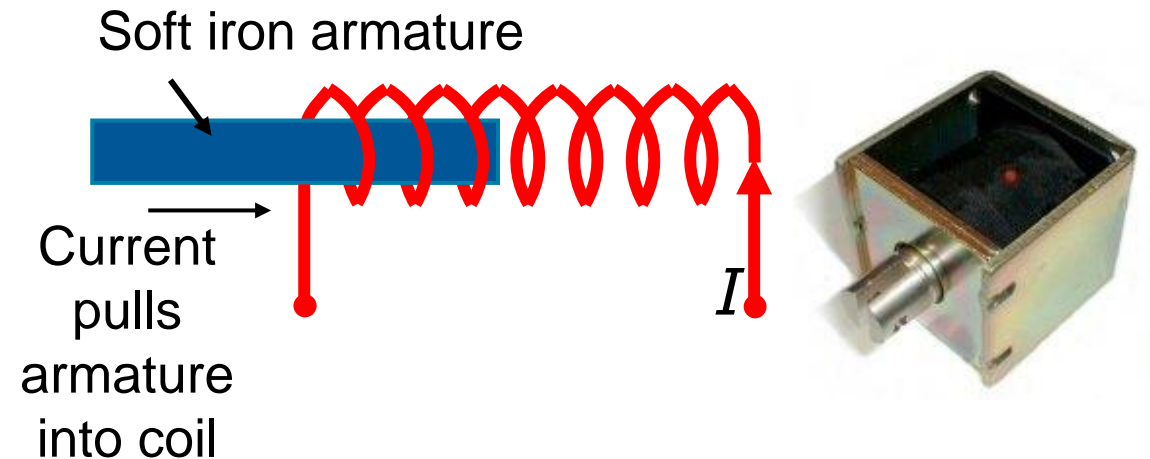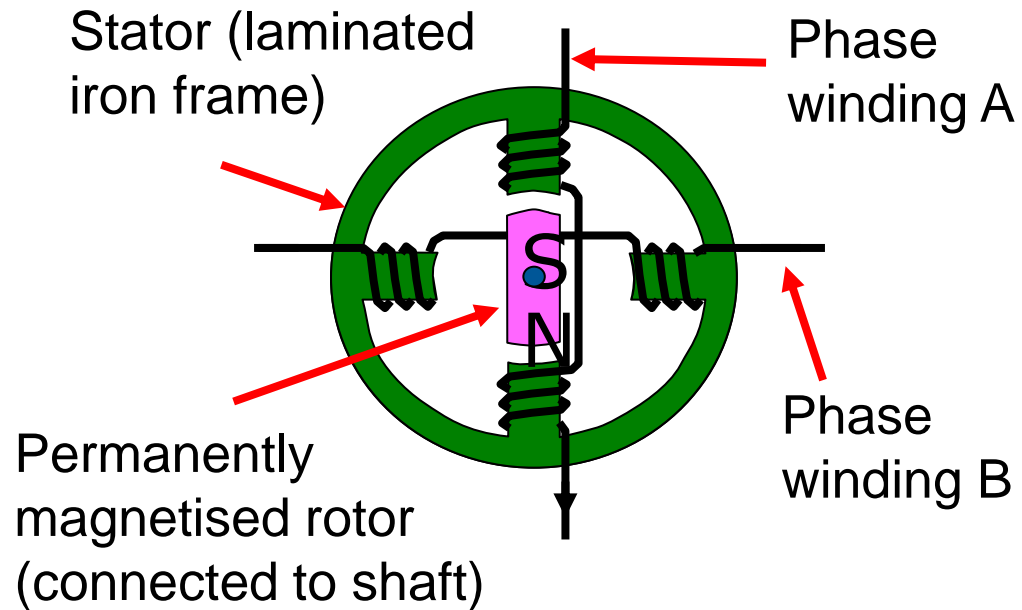
## Examples in real life



Filtering out rapidly-changing (high frequency signals) e.g., to stop unwanted noise going down power leads



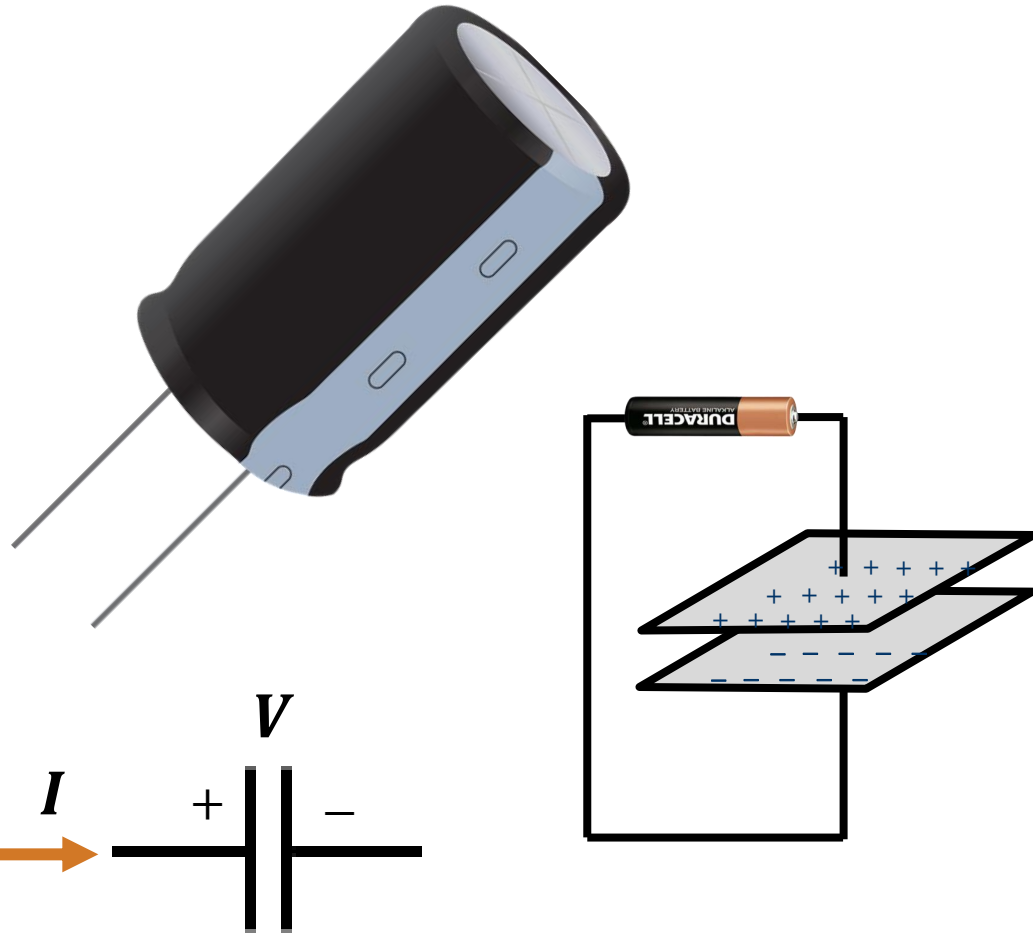

Electrical symbol

Two parallel plates with insulation (dielectric) in between


They have a property called **Capacitance** (SI unit: **Farad**, symbol **F**)

**Current** applied is proportional to **rate of change of Voltage** (unlike Ohm's law)

$$I \propto \frac{dV}{dt}$$
$$I = C \frac{dV}{dt}$$

Energy stored using electrostatic attraction: + and - charges in adjacent plates attract each other


# Capacitor

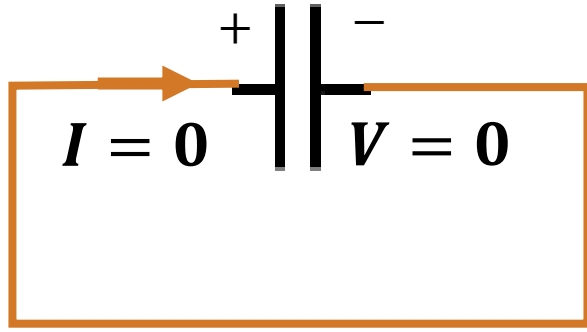

Capacitor is discharged




Mass is stationary

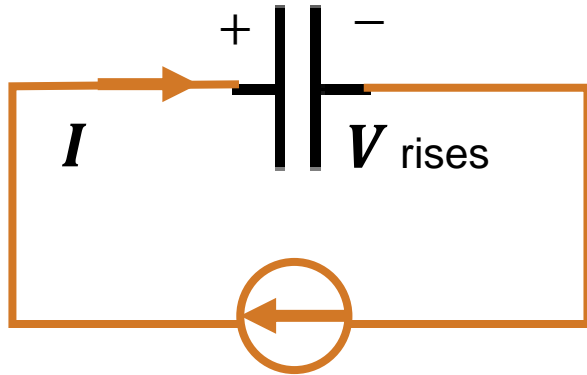

Current applied, Capacitor voltage starts increasing



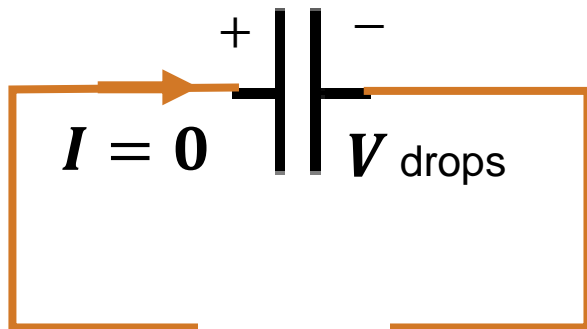Force applied, mass starts gaining velocity




Current removed, voltage starts declining and eventually goes to zero due to charge leakage



Force removed, mass slows down and stops eventually due to friction


# Capacitor

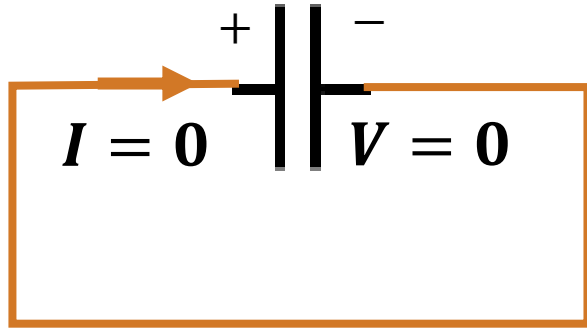

Capacitor is discharged




Mass is stationary

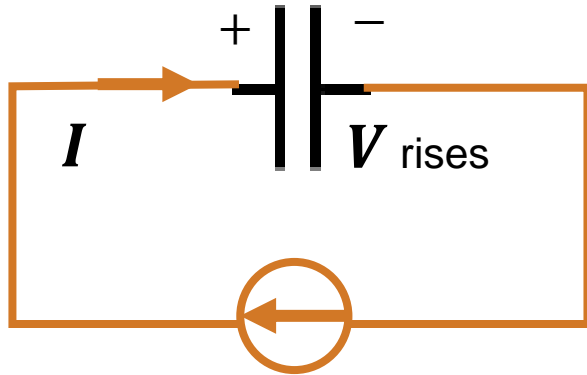


Current applied, Capacitor voltage starts increasing



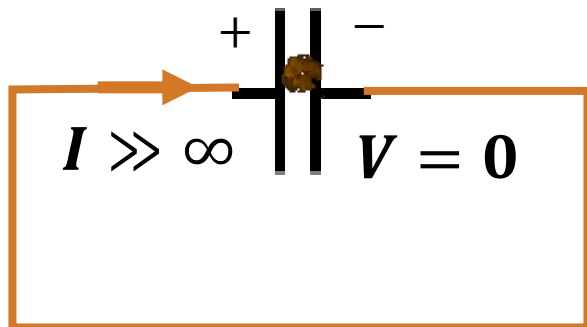Force applied, mass starts gaining velocity



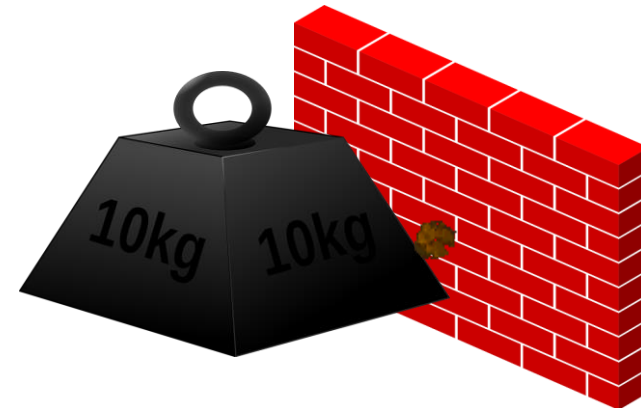Current removed and current path closed, i.e., short-circuit, near infinite current generated through capacitor to force non-zero voltage – **explosion** if high-enough energy was stored!



Unmovable brick wall

## Examples in real life




Stores charge to cause  
xenon spark for  
photographic flash

Practically all  
Electronics have small  
PCB-mount capacitors  
for voltage stabilization



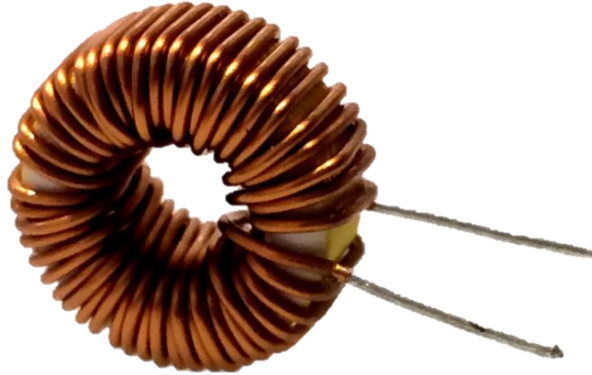All Electric Motors that are  
PWM-controlled  
(practically all in today's  
world)





Inductor **opposes sudden changes in current**

By **inducing** as much **voltage** is theoretically needed to **keep the current steady**



Capacitor **opposes sudden changes in voltage**

By **generating** as much **current** is theoretically needed to **keep the voltage steady**



- What is **Engineering**?
  - **Mechanical**
  - **Electrical** – sub-branch **Electronic engineering**
  - **Electromechanical**
  - **Computer/Software**
- Fundamentals of **Electrical Engineering**
  - **Charge, Current, Voltage** – concept of **Across & Through** variables
  - Resistance & **Ohm's Law**
  - Kirchhoff's Current Law (**KCL**) & Kirchhoff's Voltage Law (**KVL**)
  - **Power & Energy**
- Electrical **energy storing elements** – **Reactive** elements
  - **Capacitor**
  - **Inductor**



# Attendance

