



Electromechanical Devices MMME2051


Exercise Sheet 10 – Analog Electronics, Op Amps, Strain Gauge

- 10.1 Draw and explain how an accelerometer works.
- 10.2 Accelerometers are always used with an op-amp circuit – why is this?
- 10.3 Draw an amplifier circuit that could be used with a Wheatstone bridge. Write down the equation relating the potential developed across the Wheatstone bridge to the output of the amplifier circuit.
- 10.4 A Wheatstone bridge develops a potential of 0.01V, an amplifier circuit attached to the bridge has $R_1=R_2=10\text{k}\Omega$ and $R_f=R_g=100\text{k}\Omega$. What will the output voltage of the amplifier circuit be?
- 10.5 Calculate the resistance of an aluminum wire 50m long, 1mm diameter at 0°C and 50°C , given that $\rho=2.7 \times 10^{-8} \Omega\text{m}$ at 0°C and $\alpha=0.0038 \text{ K}^{-1}$.
- 10.6 The $10\text{k}\Omega$ potentiometer in Fig 7.2 has an active length l . A voltmeter with infinite internal resistance is connected between node B and the potentiometer wiper (node A).

1.72 Ω , 2.11 Ω

Calculate the voltmeter reading when the potentiometer wiper is set at a distance x measured from the earthed end of:

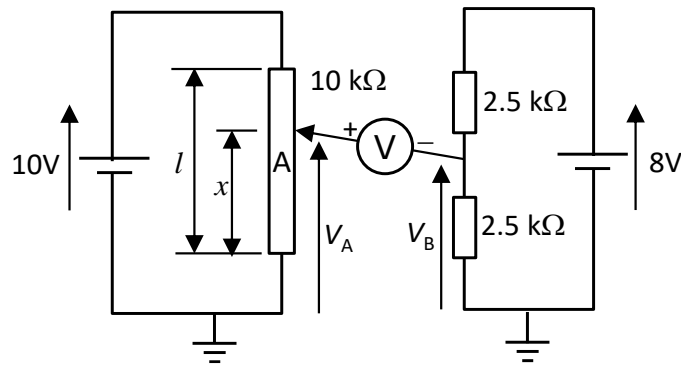- (i) $0.8 l$
- (ii) $0.5 l$
- (iii) $0.4 l$
- (iv) $0.2 l$



+4V, +1V, 0V, -2V.

10.7 A strain bridge comprises two 120Ω resistors, one active gauge and one unstrained gauge for temperature compensation. The two gauges have unstrained resistances of 120Ω and a strain gauge factor of 2.2. The bridge supply voltage is 5V. Calculate the strain when the voltmeter reading is 2mV.


$\varepsilon = 727 \text{ microstrain}$

10.8 A force, F of 10N is exerted at the centre of the steel beam shown in Fig 7.4a. Four identical strain gauges each with an unstrained resistance of 350Ω and a strain gauge factor, G of 2.4 are glued to the upper and lower surfaces of the beam, which is 400 mm long and 3 mm deep. The second moment of area of the beam, I is $3.6 \times 10^{-11} \text{ m}^4$ and Young's modulus for steel, E is $207 \times 10^9 \text{ Pa}$.

The four strain gauges are connected to a strain gauge bridge as shown in figure below:

- V_s is 10V.
- Bending moment at centre of beam, $M = \frac{FL}{2}$, where L =half the beam length.
- Stress adjacent to load $\sigma = \frac{My}{I}$ where y =half the depth of the beam.
- Strain, $\varepsilon = \frac{\sigma}{E}$

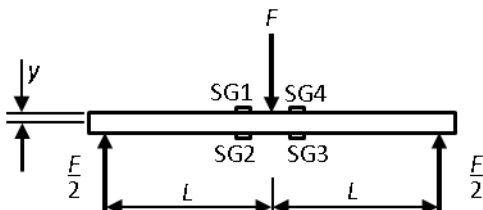Calculate the bridge output voltage, V_{bridge}



4.83 mV

