



University of
Nottingham

UK | CHINA | MALAYSIA

LECTURE 9

DC Motors & Boolean Algebra


Electromechanical Devices MMME2051

Module Convenor – Surojit Sen




- DC Motor
 - **Revision** of all motors studied so far – Induction, Stepper
 - **Operation** of a **Simple DC Motor**
 - **Why** use a DC Motor?
- **Boolean Algebra**
 - **Revision of Digital Electronics**
 - **Addition (OR), multiplication (AND), complement (NOT)**
 - **Laws**


INDUCTION MOTOR

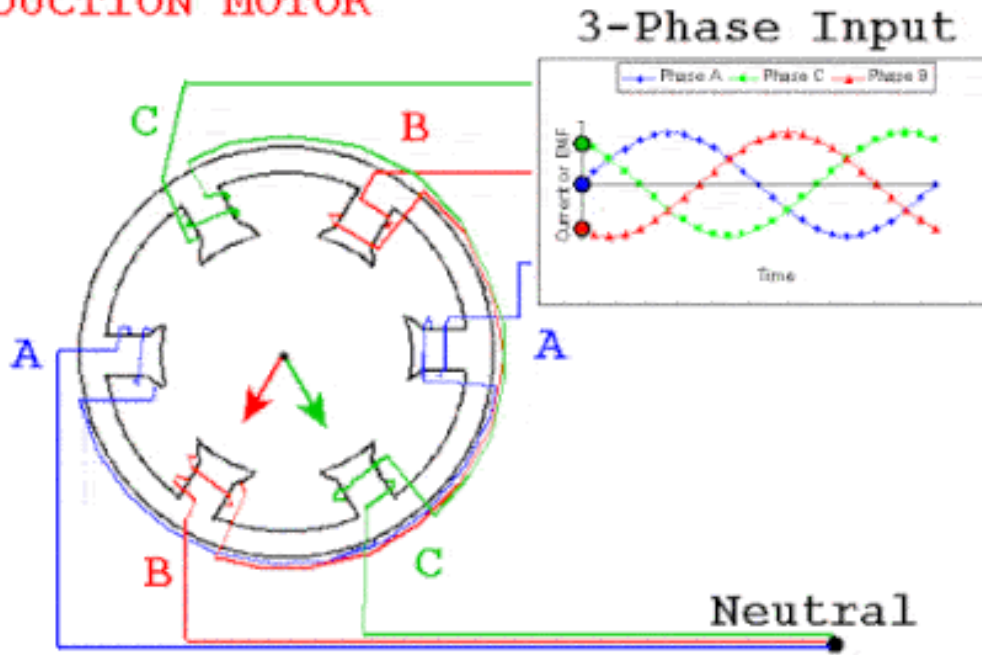
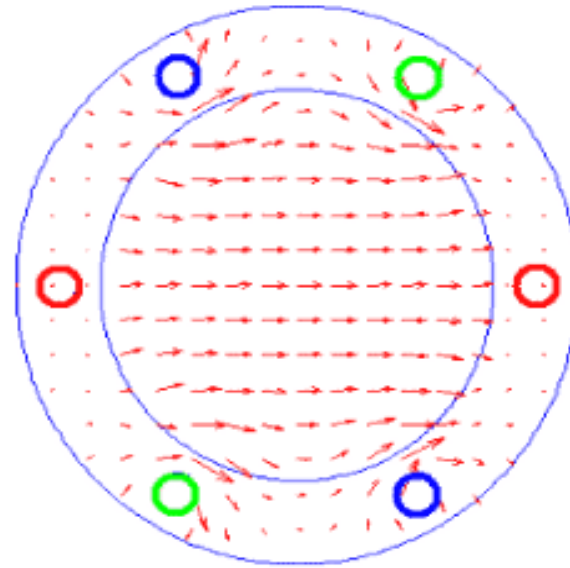
<https://axljoann.blogspot.com/2021/05/3-phase-induction-motor-hitachi-three.html>


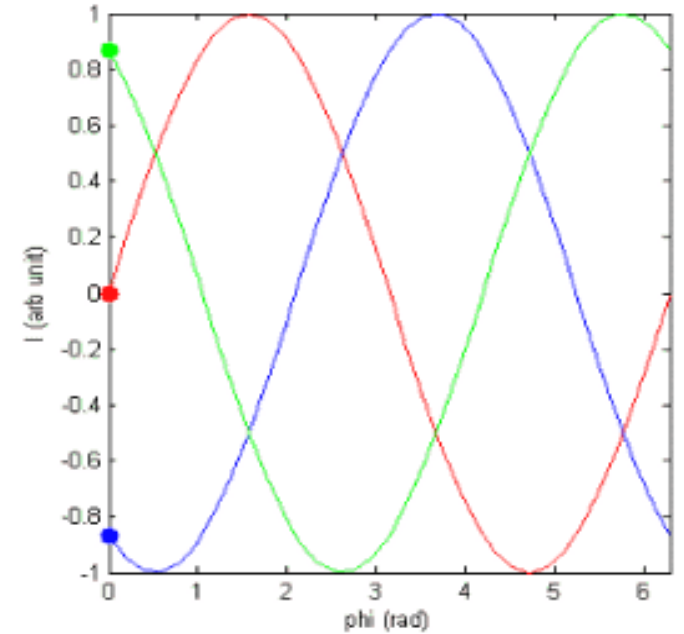
<https://medium.com/@abhisheksingh73017/how-an-induction-motor-starts-real-answer-from-an-engineer-65f2fd7fa5b1>





The speed of rotation is called “synchronous speed” which is nothing but the 3-phase AC frequency!

$$n_s(\text{Hz}) = f \text{ or } n_s(\text{RPM}) = 60 \times f$$



Induction Motor

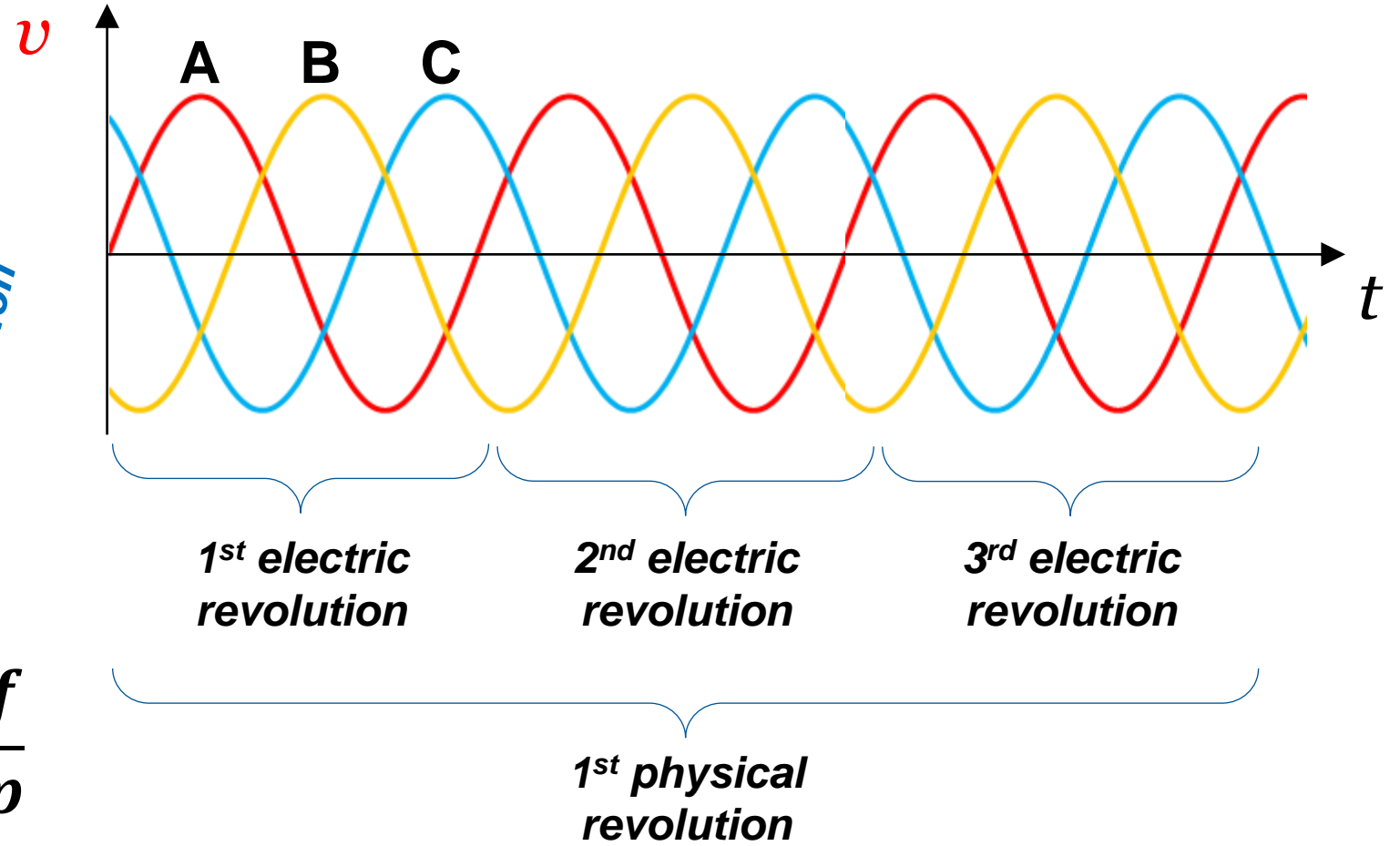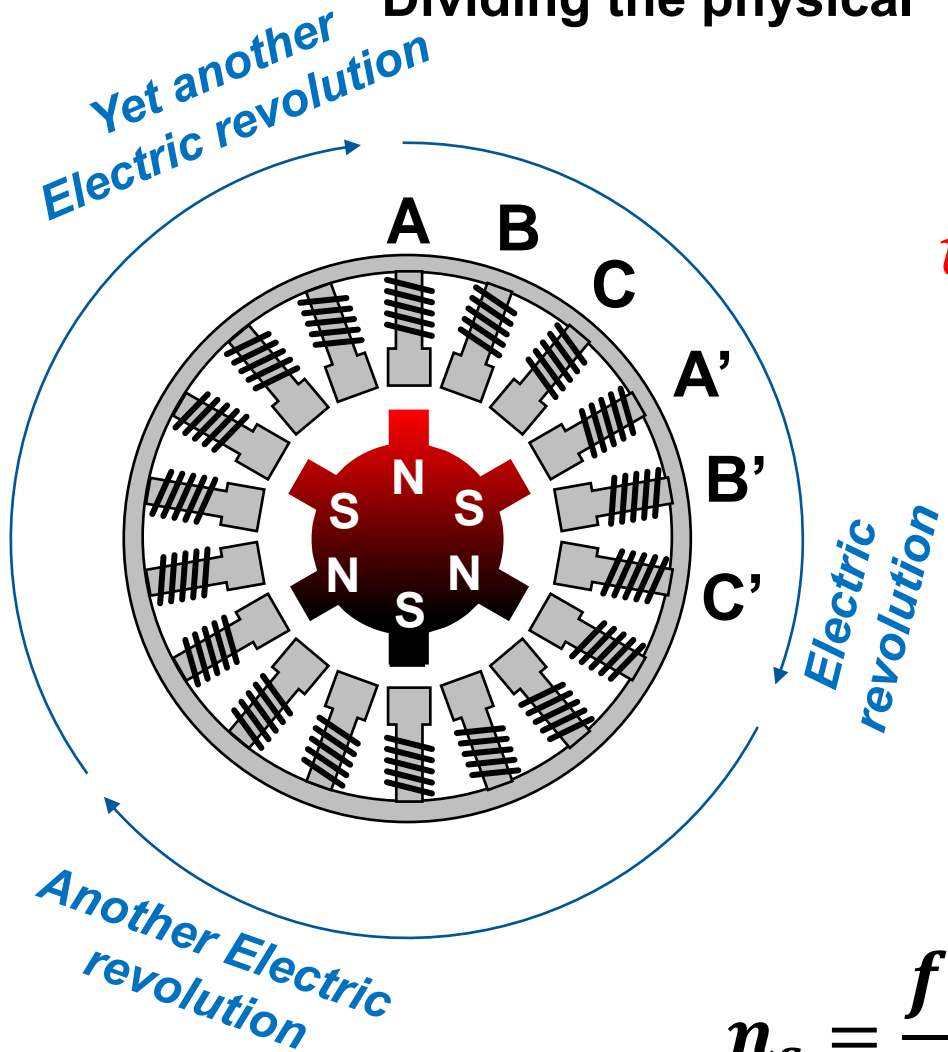Dividing the physical “angular space” into multiple sets of 3-phase





$$n_s = \frac{f}{p}$$

Left-Hand Rule (Motors)

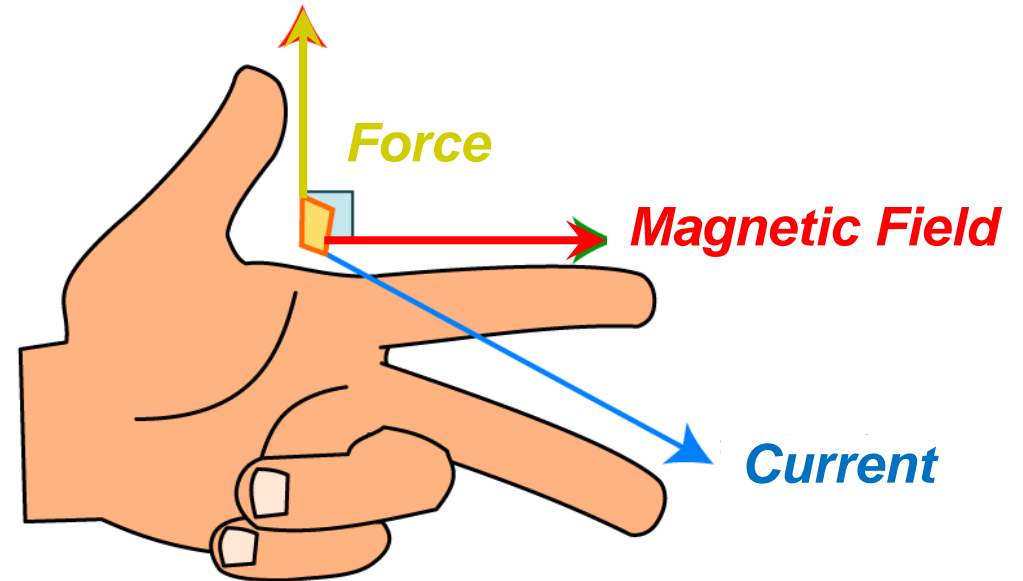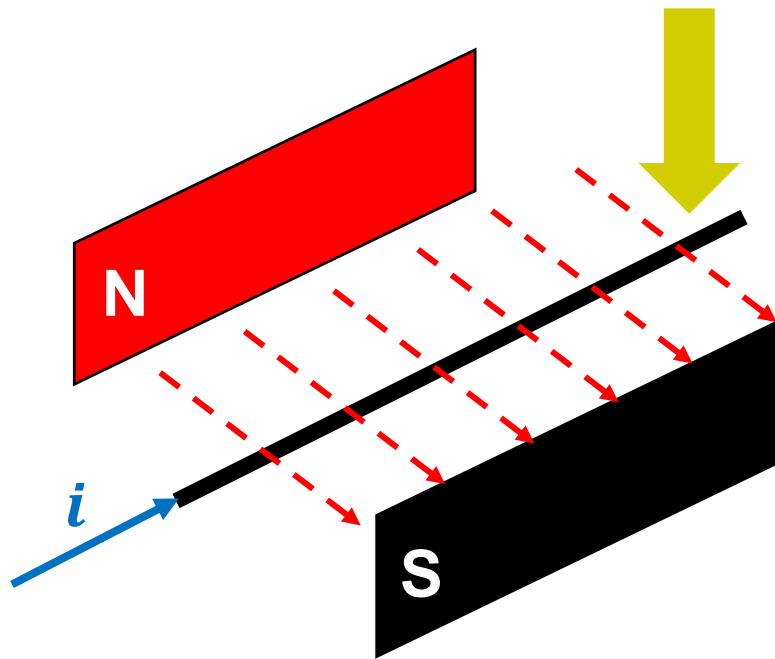

A current-carrying conductor in a magnetic field experiences a force/thrust


Right-Hand Rule (Generators)

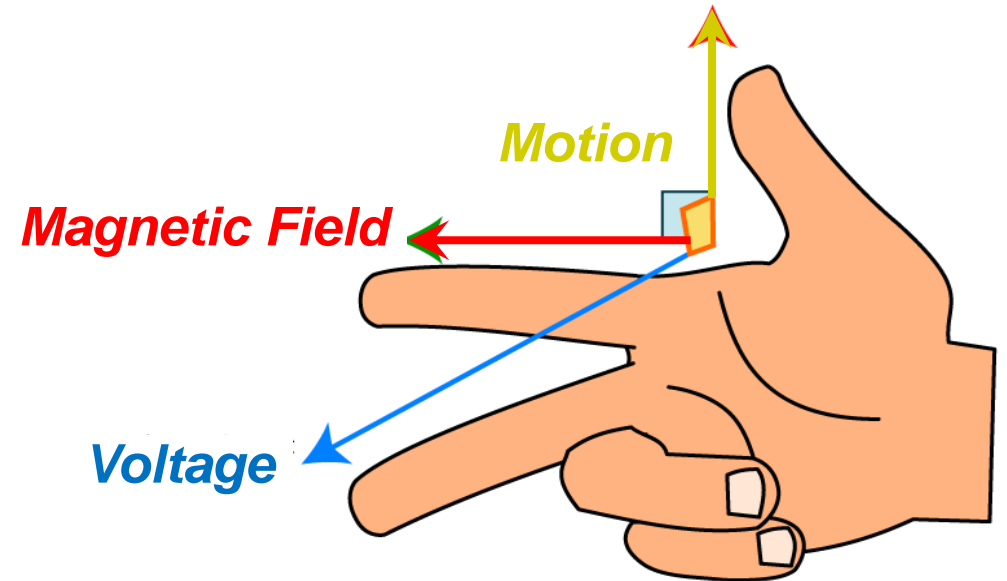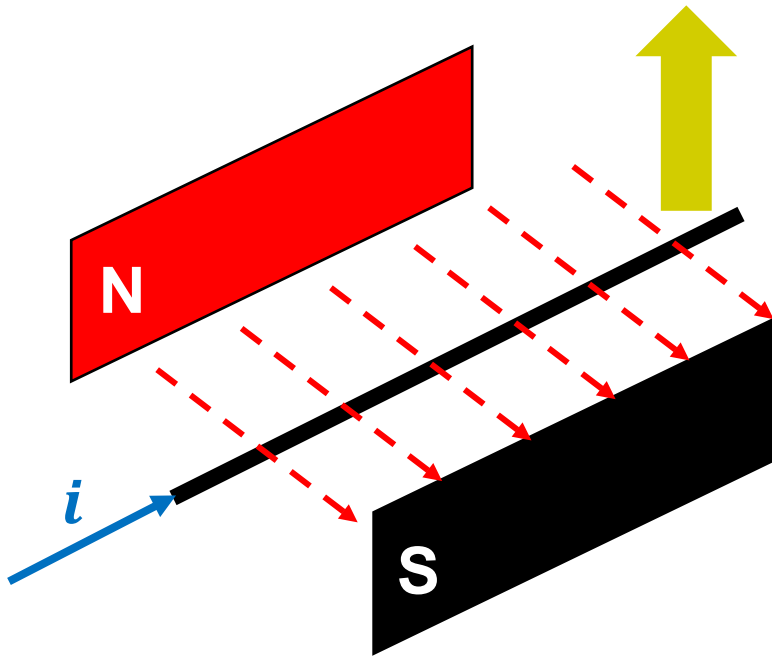

**A conductor moving in a magnetic field generates a voltage across itself
(current produced if circuit was to be completed)**




Induction Motor

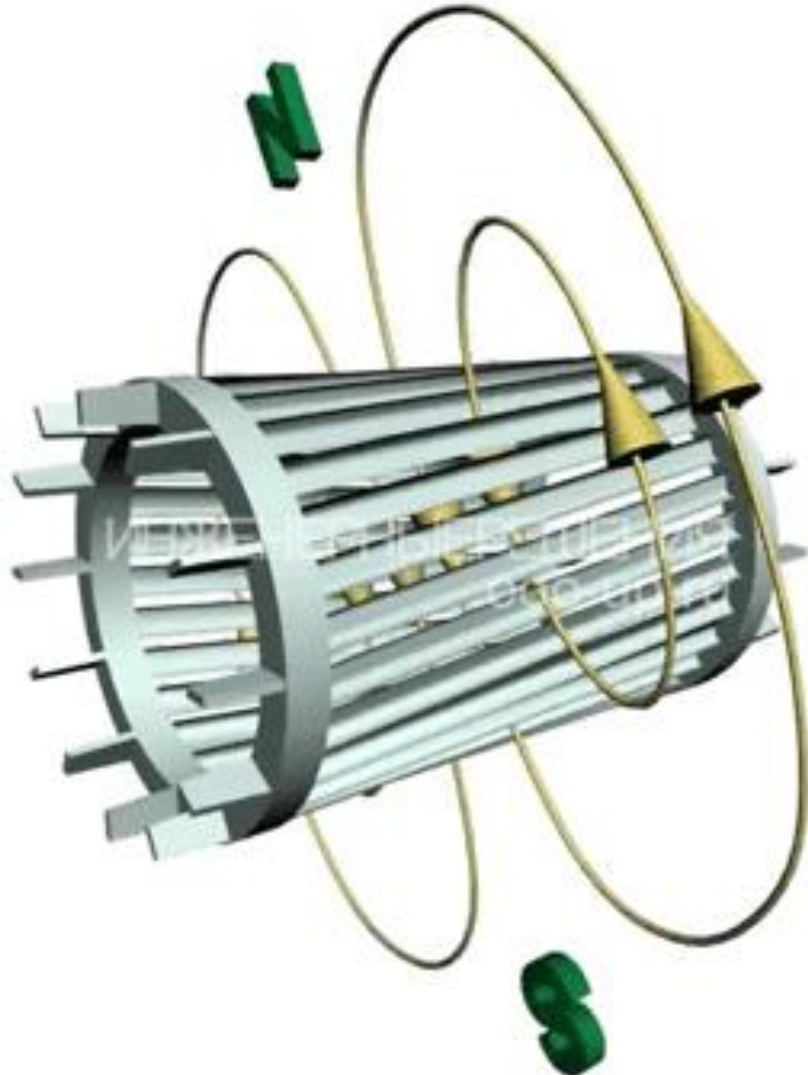

- Rotating **Magnetic Field** produced by the stator is continually **cutting a conductor**
- **Synchronous Speed** = Speed of the **rotating magnetic field**, i.e., **stator field**, i.e., **input supply**
- An **EMF gets generated** (RH Rule). In a squirrel cage rotor, everything is shorted! Hence, **current flows**
- Now the conductor is a **current-carrying** conductor. Current-carrying conductor experiences a **force** in the **magnetic field** (LH Rule)
- **Rotor needs to slip** (allowing the cutting) to produce any torque
- **Higher slip = higher torque**

$$T = \frac{3p}{2\pi f} \times \frac{V^2 a s}{X_R(a^2 + s^2)}$$

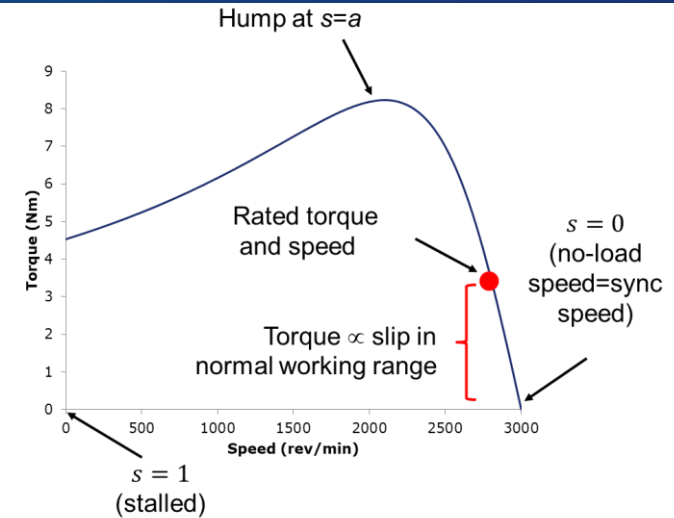
- T – Torque in star-connected motor
- p – Pole pairs per phase
- f – Supply frequency
- V – Supply phase voltage
- $a = \frac{R_R}{X_R}$ – Resistance-to-reactance ratio of rotor
- $s = \frac{n_s - n}{n_s}$ – Per-Unit slip (n_s – Sync Speed)
- n – Actual speed of rotor (same unit as sync speed)
- X_R – Reactance of Rotor (as seen from stator – referred impedance – remember Transformer?)



- No-load speed = synchronous speed
- Torque \propto slip (approx.) for small torques
- Torque-speed characteristic has “hump” at $s = \frac{R_R}{X_R} = a$
- Under running conditions slip is small e.g. 5%
- By setting $\frac{dT}{ds} = 0$, can show that maximum (“pull-out”) torque is


$$T_{max} = \frac{3p}{4\pi f} \frac{V^2}{X_R}$$

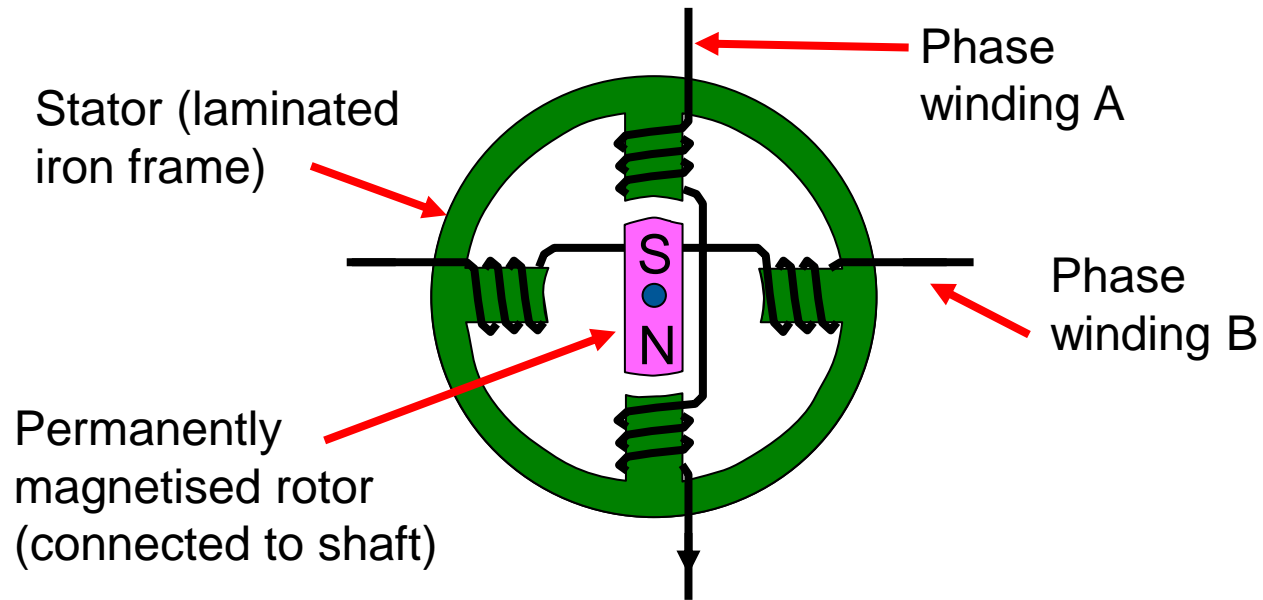- Motor stalls if load torque T reaches T_{max}








You can imagine, a motor design on left would make the motor spin in a **jerky** fashion. In real world, the motor looks like below. Each “**tooth**” is a magnet pole.

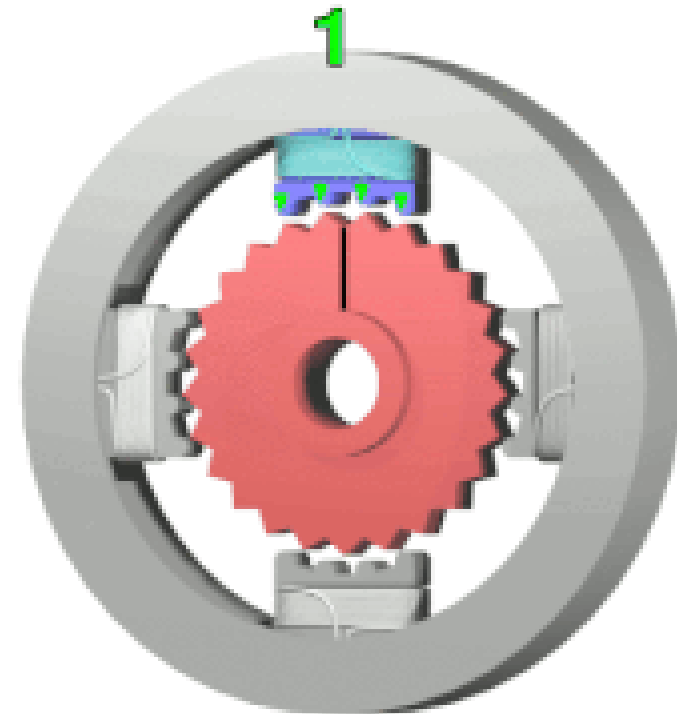- Rotor is (usually) **permanently magnetised**
- Attracted to a **different pair of poles at each step**
- Moves from **pole to pole** as each pair of poles is energised
- So it moves in a **series of steps**



Stepper Motor

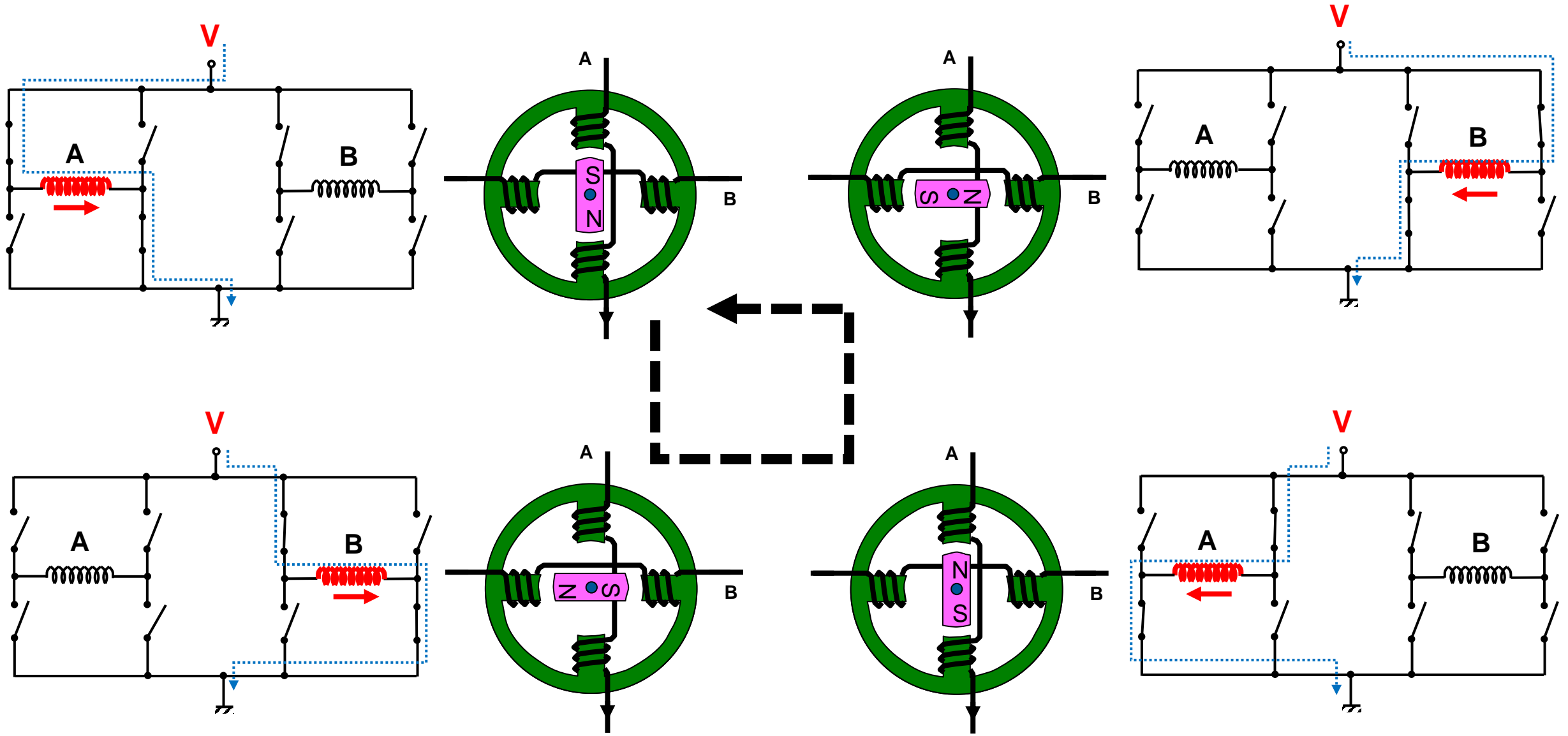

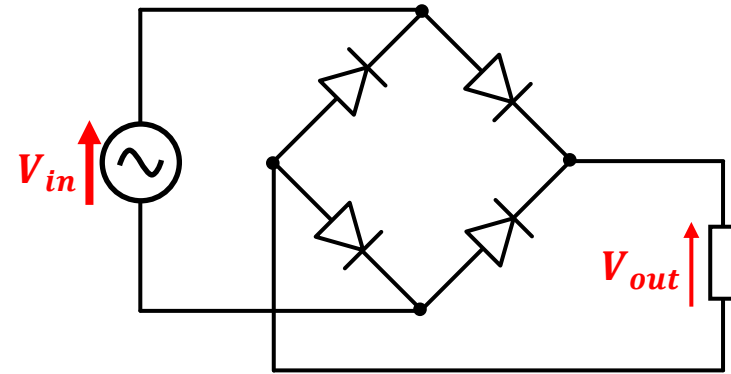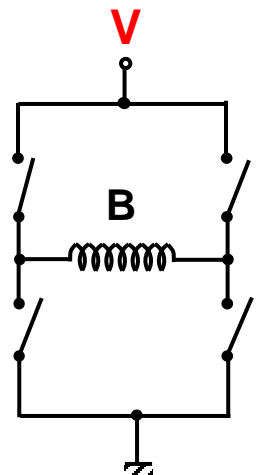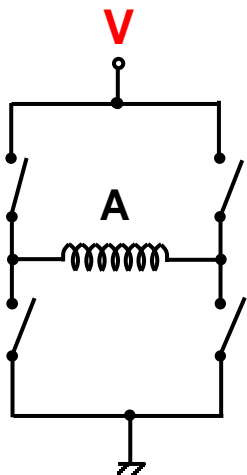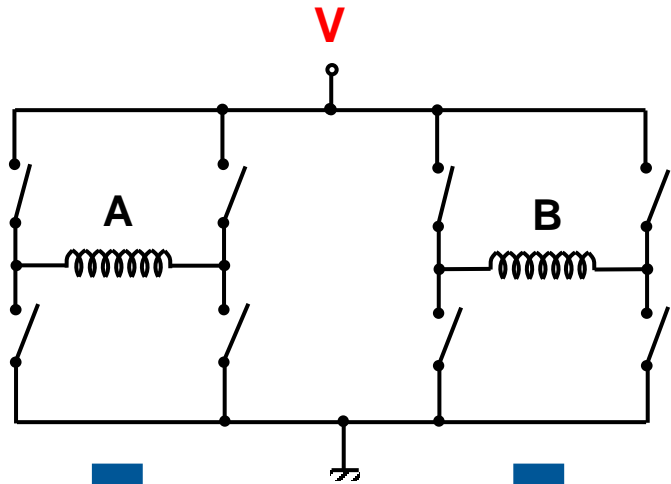


This circuit is more specifically called the **Diode Bridge**




H-Bridge

An H-Bridge is a circuit that allows polarity inversion across a load – basically allows current to flow in both direction by the application of switches (transistors) or diodes

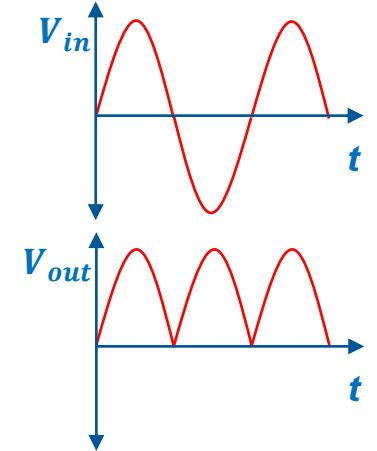
Universally used circuit for **Rectification** and **Motor Control**




Stepper Motor

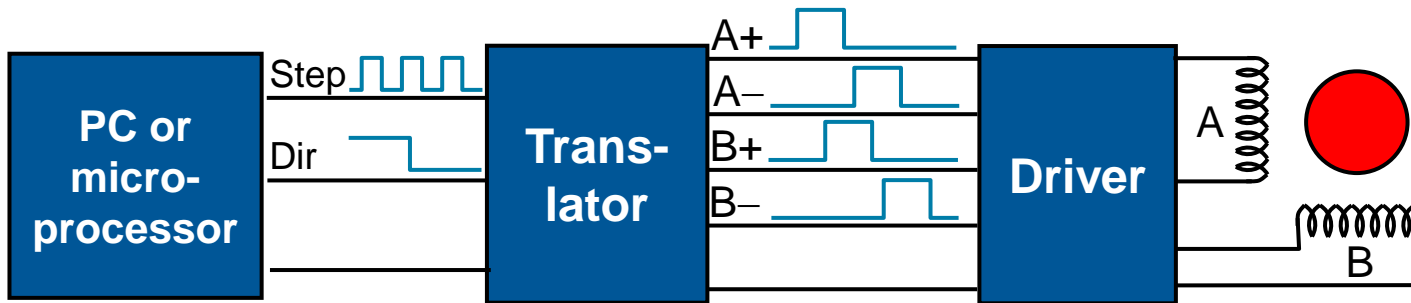

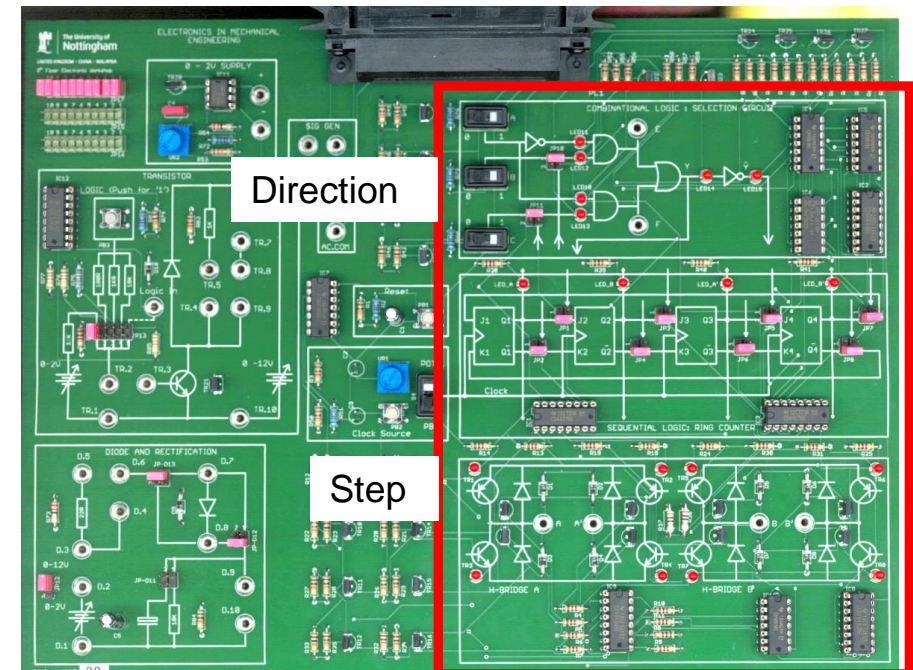- **Sequential logic** (interprets “step” signals)
- **Combinational logic** (interprets “direction”)
- **Transistors** (these are the switches which connect and disconnect the windings)




Stepper Motor

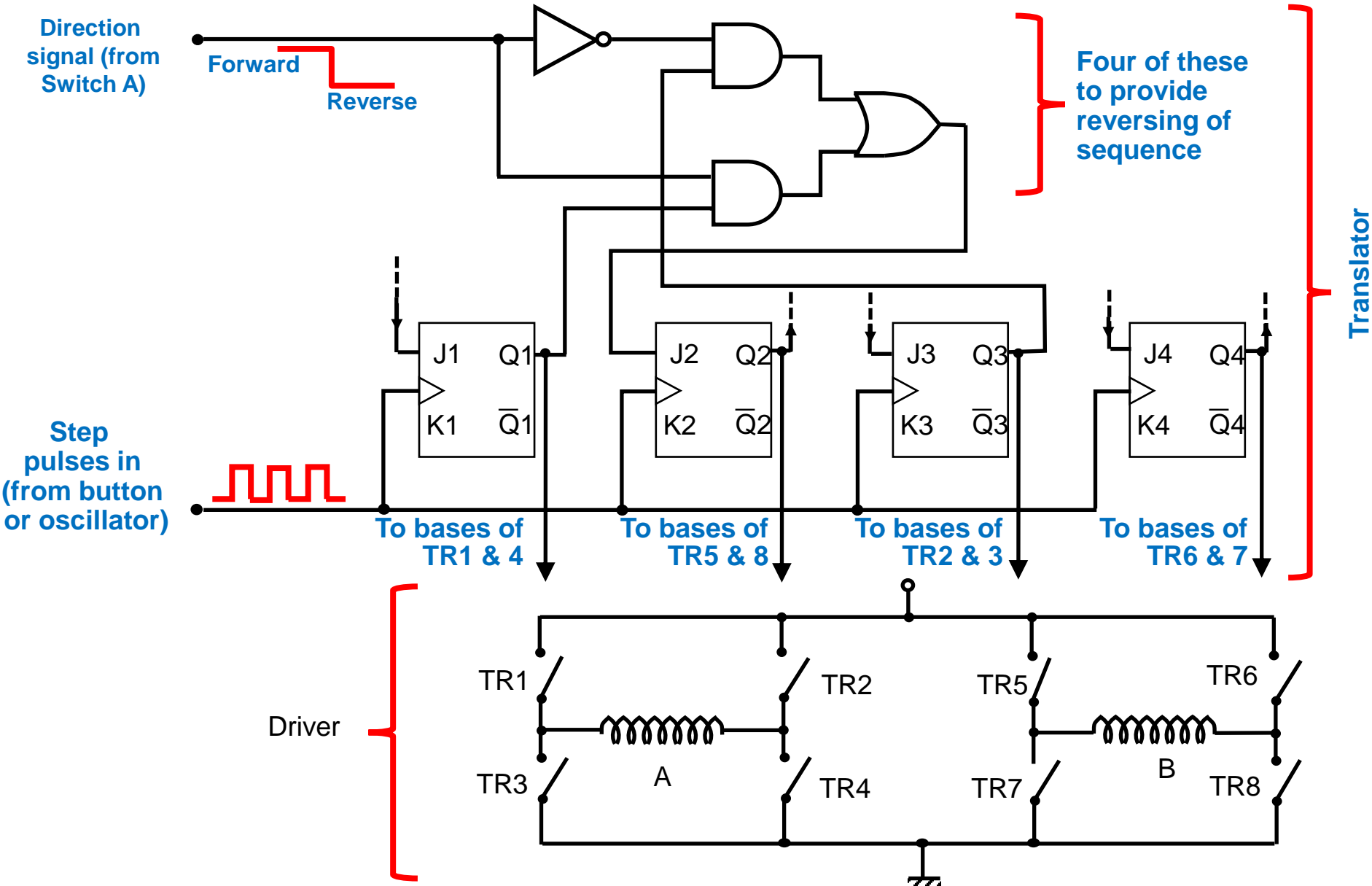

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



Stepper Motor

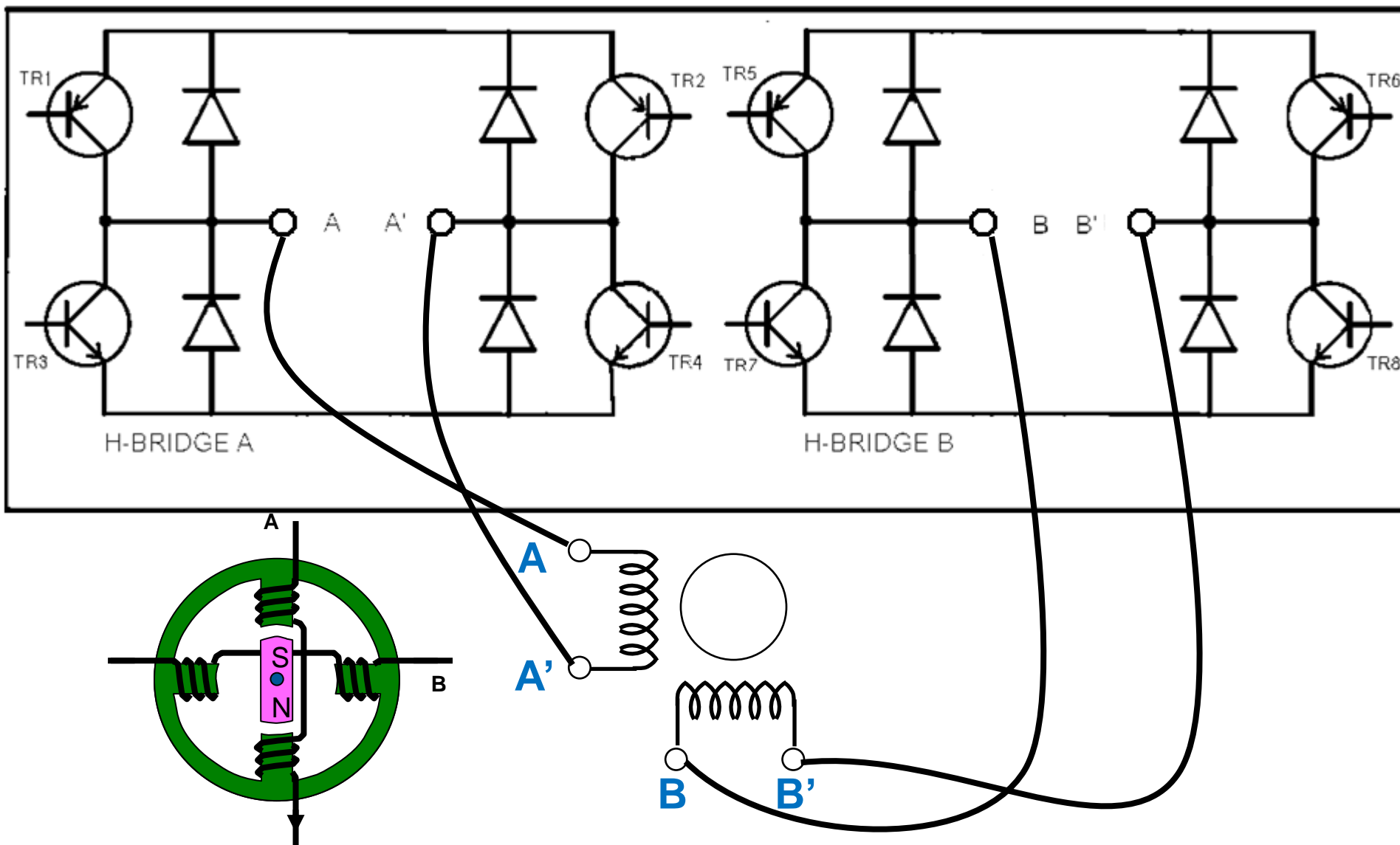



Simple DC Motor

“**Simple**” DC Motor are one of the oldest motor inventions that are still being used to this day – they are very simple from an engineering point of view

They are largely superseded now by “**electronically commutated**” DC Motors (hence the usage of “Simple” in this design)



Car Wiper Motor

<https://ladaworld.com/en/electric/68-lada-wiper-motor-2103-3730000.html>

Power Window Motor

<https://www.rendcarparts.com/saab/parts/4328415-5184874/rd5184874a>

Electric Wheelchair



https://www.karmamedical.com/featured_item/efl/



“Simple” DC Motor

The stator is either **permanent magnet** or **wire-wound with DC voltage applied**

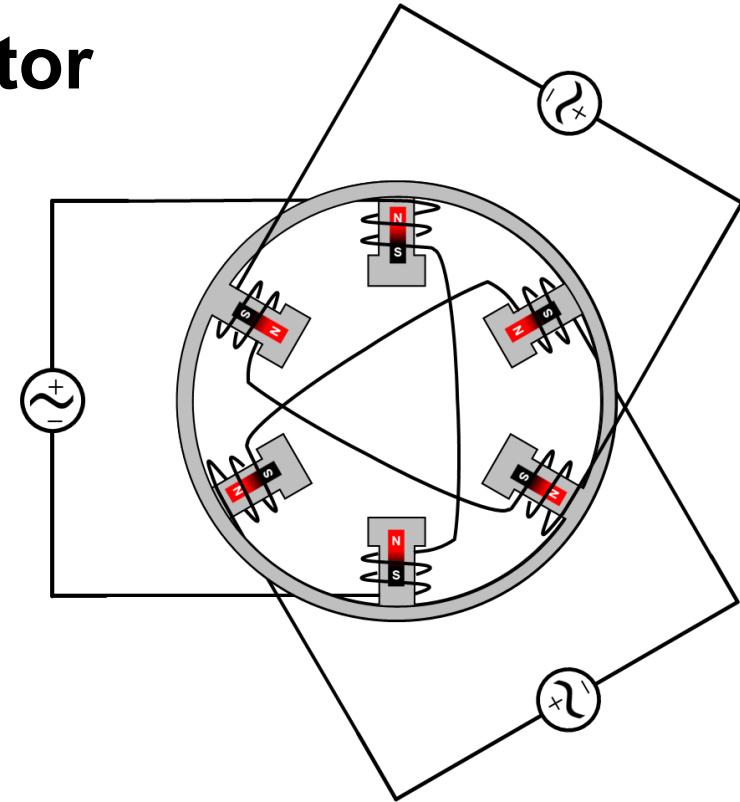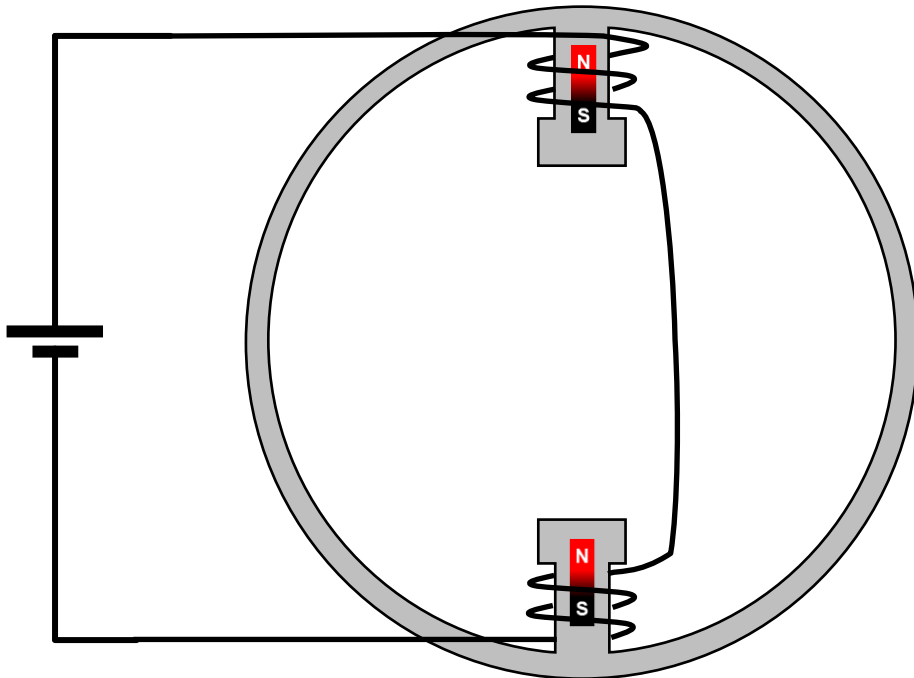Effect is the same – constant magnetic field



Remember Induction motor stator? It is very similar, but much simpler:

- **No AC**
- **Only single phase**

“Simple” DC Motor


The rotor is simply a **coil** with current flowing through it via **another** DC voltage supply

Interesting bit here is the **commutator/brush pair** – this allows to flip the voltage polarity every half revolution

Hence, the current flow direction also flips


Now let us see how the motor operates!

Hint: Fleming’s LH and RH Rules.

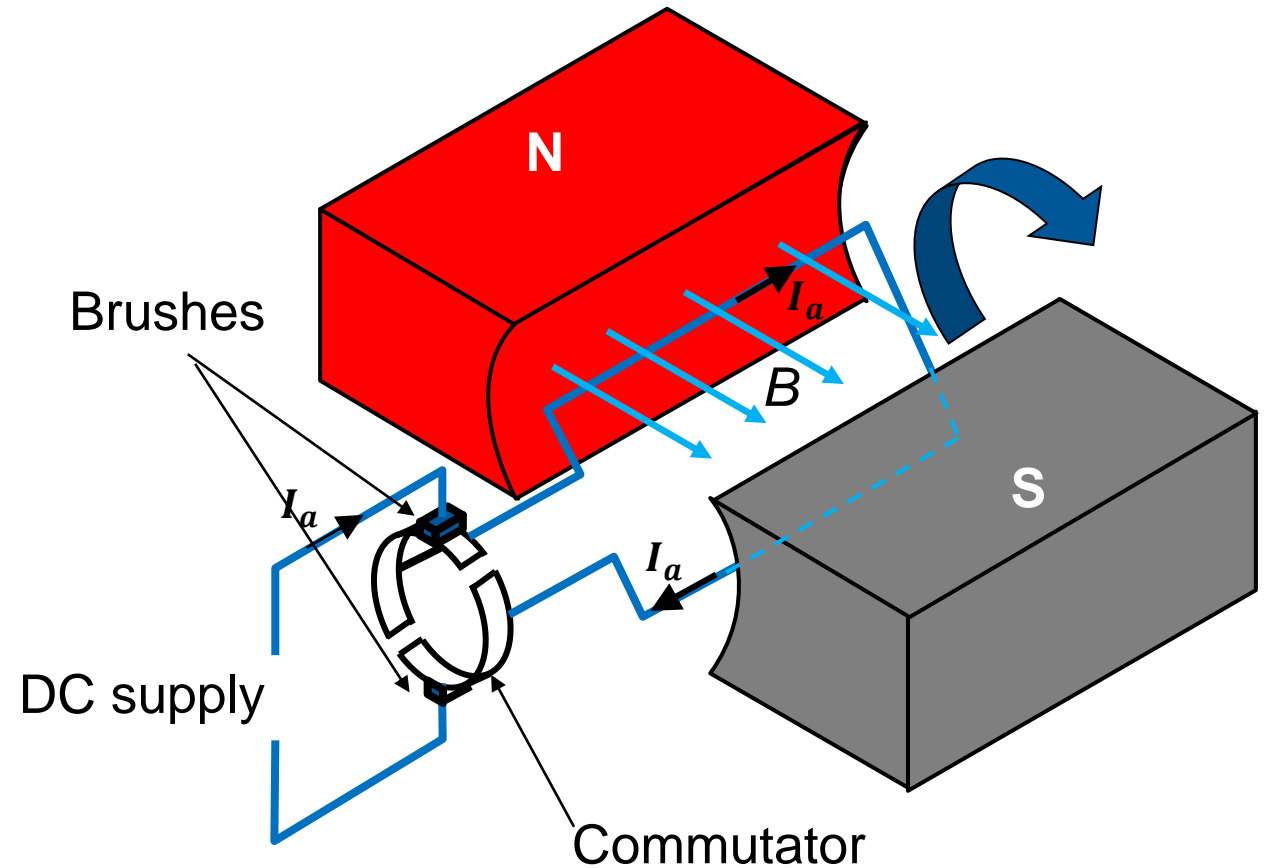



Simple DC Motor

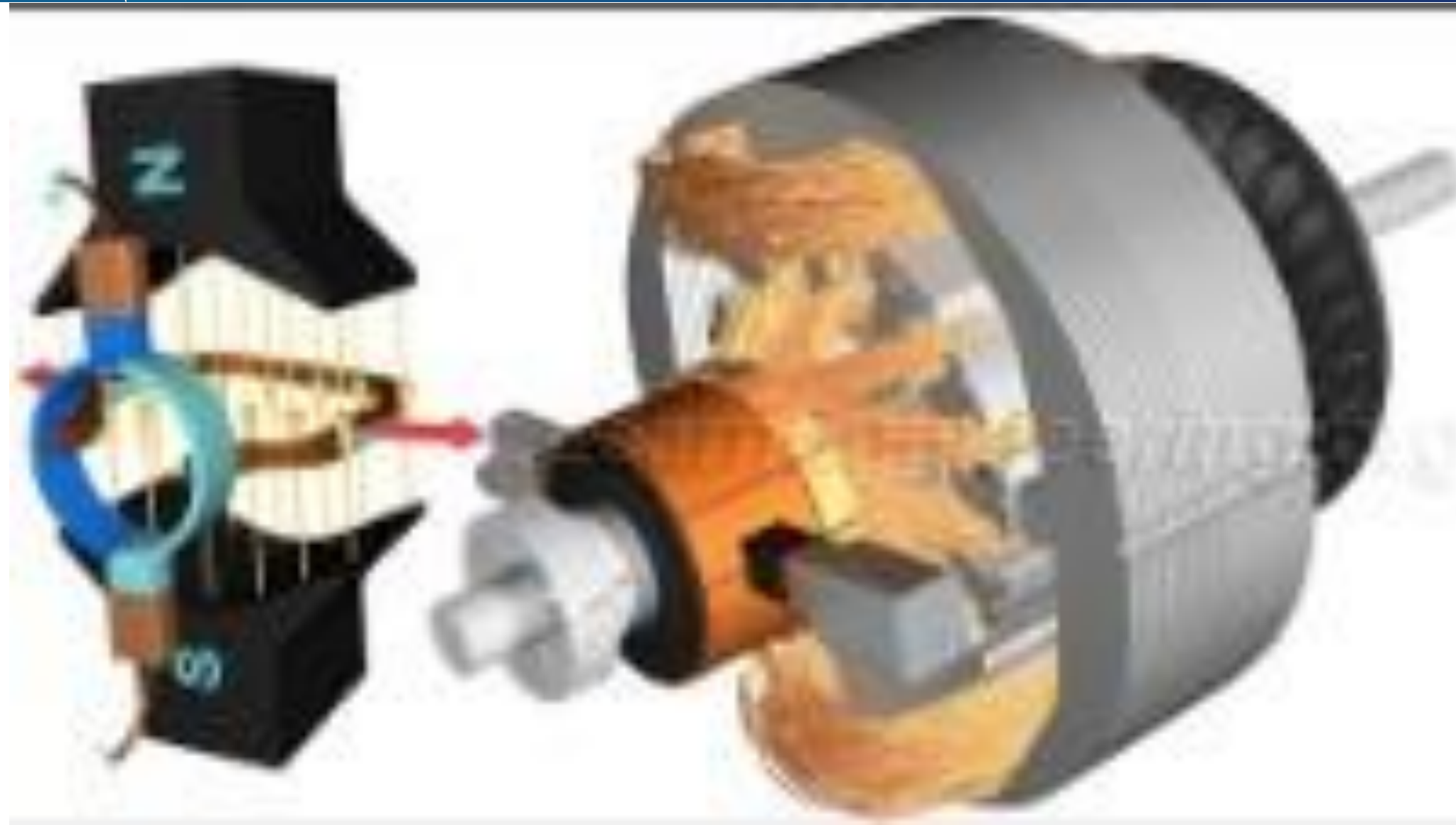

<https://www.youtube.com/watch?v=LAtPHANefQo>

“Simple” DC Motor

Fleming’s Left Hand Rule says a current-carrying conductor in a magnetic field experiences force/thrust

Lorentz Law says:


$$F = B \cdot I_a l$$

Torque is a function of the force and radius (which is fixed):

$$\tau = r \times F$$

Hence, Torque is linearly proportional to the Armature Current:

$$\tau = K I_a$$

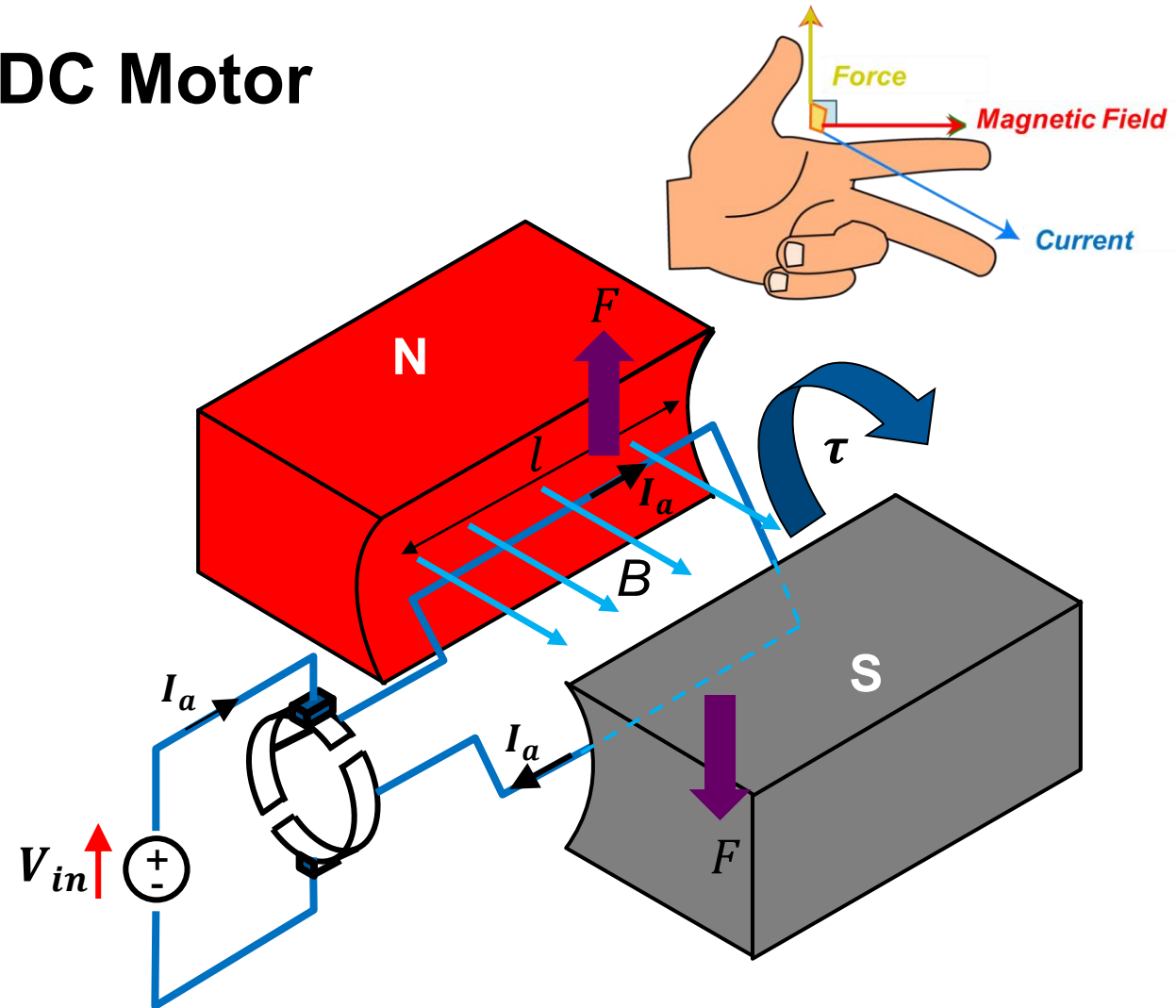

“Simple” DC Motor

Fleming’s Right Hand Rule says a moving conductor in a magnetic field generates a voltage across it

Lorentz Law says:


$$E_b = B \times vl$$

Angular velocity is linearly related to speed:

$$\omega = \frac{v}{r}$$

- Hence, Back EMF is linearly proportional to the Angular Speed:

$$E_b = K\omega$$

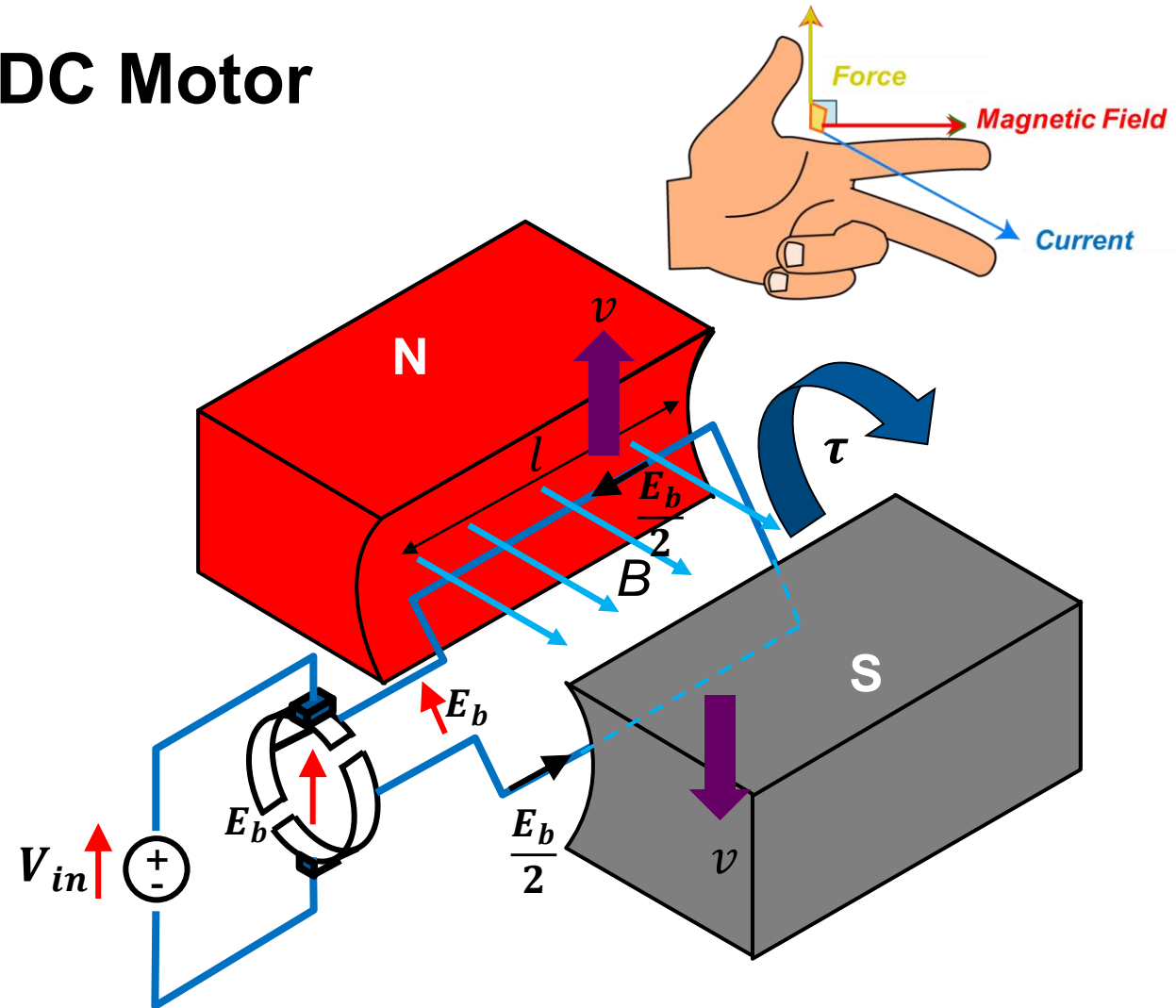

“Simple” DC Motor


So the two equations to pay heed to are:

$$\tau = KI_a$$

$$E_b = K\omega$$

You can find out mathematically (using the original equations in previous two slides) that the value of K is same in both equations!

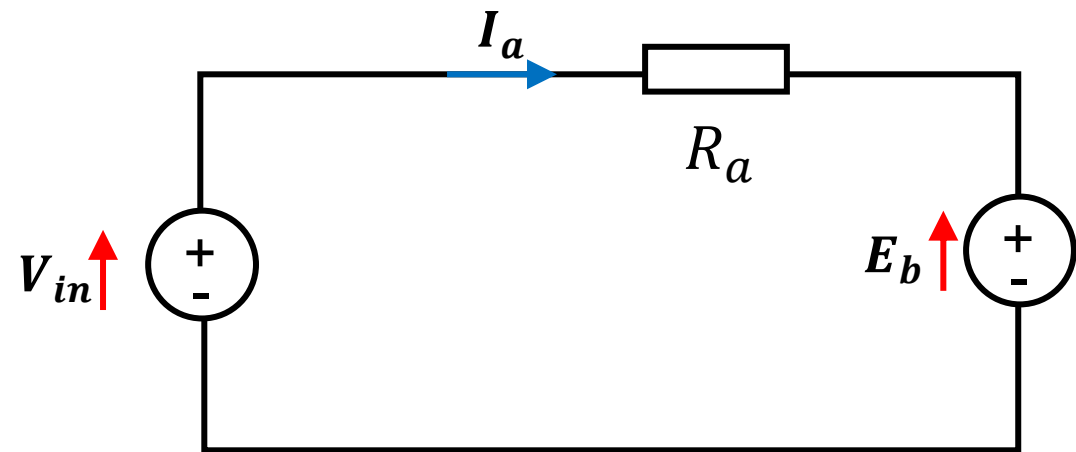Equivalent electrical circuit can be used to visualise how the motor works



$$V_{in} = E_b + I_a R_a$$

$$V_{in} = K\omega + \frac{\tau}{K} R_a$$



“Simple” DC Motor

We can also plot the Torque-Speed curve of the “Simple” DC motor using this equation

At zero speed (stall):


$$V_{in} = K(0) + \frac{\tau}{K} R_a$$

$$\tau = \frac{K}{R_a} V_{in}$$

At zero torque (no load):

$$V_{in} = K\omega + \frac{(0)}{K} R_a$$

$$\omega = \frac{V_{in}}{K}$$

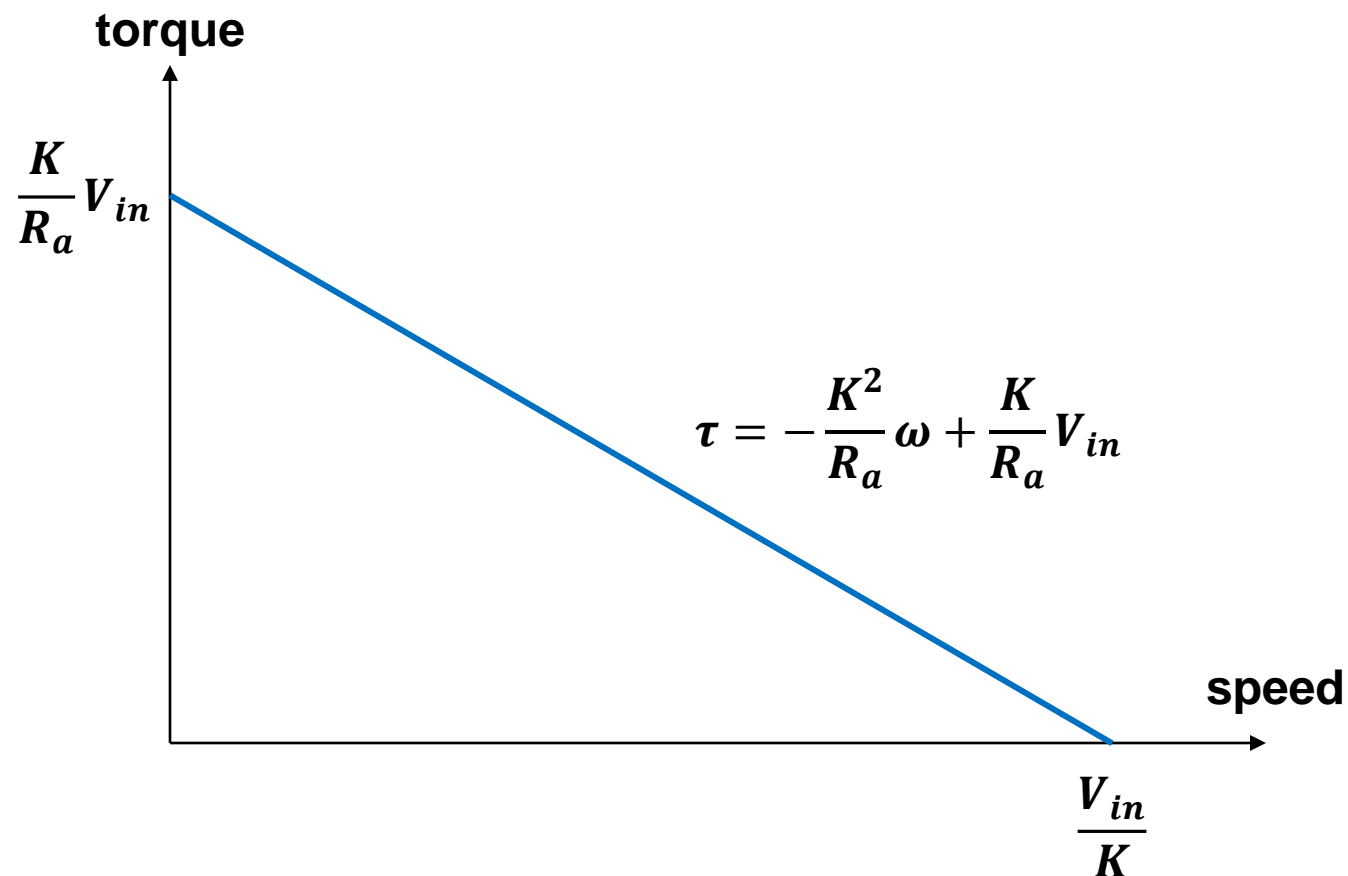

“Simple” DC Motor

We can also plot the Torque-Speed curve of the “Simple” DC motor using this equation

At zero speed (stall):


$$V_{in} = K(0) + \frac{\tau}{K} R_a$$

$$\tau = \frac{K}{R_a} V_{in}$$

At zero torque (no load):

$$V_{in} = K\omega + \frac{(0)}{K} R_a$$

$$\omega = \frac{V_{in}}{K}$$

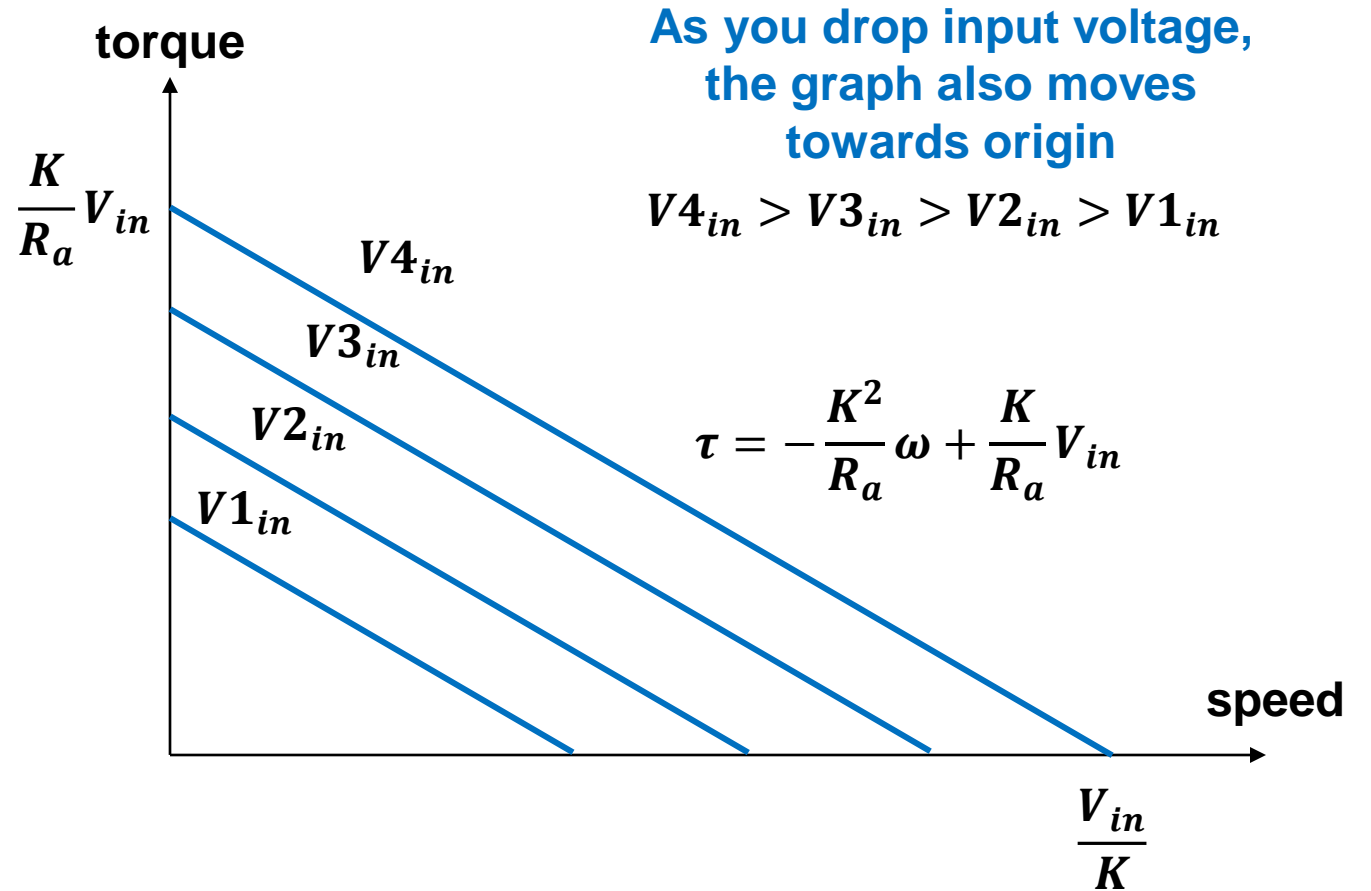

Worked Example 1

A motor has a constant of $0.025 \frac{Vs}{rad}$ and an armature resistance of 0.5Ω . Find the torque which is produced when supplying the motor from 16 V and running at a speed of 5000 RPM.

$$V_{in} = E_b + I_a R_a = K\omega + I_a R_a$$

$$I_a = \frac{V_{in} - K\omega}{R_a}$$

Here,

$$V_{in} = 16 V$$

$$K = 0.025$$

$$R_a = 0.5 \Omega$$

$$n = 5000 \text{ RPM}$$

So,

$$\omega = 2\pi \times \frac{5000}{60} = 523.6 \frac{rad}{s}$$

$$I_a = \frac{V_{in} - K\omega}{R_a}$$

$$I_a = \frac{16 - 0.025 \times 523.6}{0.5}$$

$$I_a = 5.82 A$$

And,

$$\tau = K \times I_a$$

$$\tau = 0.025 \times 5.82$$

$$\tau = 0.1455 \text{ Nm}$$

Worked Example 2

A DC motor (the “Torpedo 850”) is used for small electric drills and model boats. Its no-load speed (ignore frictional effects) is given as 9778 RPM when running from 12 V. It draws a current of 10.8 A at 12 V at a speed of 8311 RPM.

Find motor constant and armature resistance.

Find current, speed and mechanical power output at 12 V and torque of 0.05 Nm.

$$V_{in} = E_b + I_a R_a = K\omega + I_a R_a$$

Motor constant: assume that under no-load condition there really is no torque so current is zero, so:

$$V_{in} = E_b = K\omega$$

$$K = \frac{V_{in}}{\omega} = \frac{12}{2\pi \times \frac{9778}{60}}$$

$$K = 0.0117 \frac{Vs}{rad}$$

At 8311 RPM, current is 10.8 A

$$V_{in} = K\omega + I_a R_a$$

$$R_a = \frac{V_{in} - K\omega}{I_a}$$

$$R_a = \frac{12 - 0.0117 \times 2\pi \times \frac{8311}{60}}{10.8}$$

$$R_a = 0.168 \Omega$$

Worked Example 2

A DC motor (the “Torpedo 850”) is used for small electric drills and model boats. Its no-load speed (ignore frictional effects) is given as 9778 RPM when running from 12 V. It draws a current of 10.8 A at 12 V at a speed of 8311 RPM.

Find motor constant and armature resistance.

Find current, speed and mechanical power output at 12 V and torque of 0.05 Nm.

$$\tau = KI_a$$

$$I_a = \frac{\tau}{K}$$

$$I_a = \frac{0.05}{0.0117}$$

$$I_a = 4.27 \text{ A}$$

At 8311 RPM, current is 10.8 A

$$V_{in} = K\omega + I_a R_a$$

$$\omega = \frac{V_{in} - I_a R_a}{K}$$

$$\omega = \frac{12 - 4.27 \times 0.168}{0.0117}$$

$$\omega = 964 \frac{\text{rad}}{\text{s}}$$

$$\omega = 9205 \text{ RPM}$$

Mechanical output

$$W = \tau\omega = 0.05 \times 964 = 48.2 \text{ W}$$



- DC Motor
 - **Revision** of all motors studied so far – Induction, Stepper
 - **Operation** of a **Simple DC Motor**
 - **Why** use a DC Motor?
- **Boolean Algebra**
 - **Revision of Digital Electronics**
 - **Addition (OR), multiplication (AND), complement (NOT)**
 - **Laws**

Digital

Information in form of **discrete** symbols, or **levels**

Variable can be only 1 out of a **finite number of options**

Humans interpret physical values in discrete levels

- **Alphabets**
- **Binary number**
- **Logic state**
- **Answer to the question** – “*Are you enjoying this module?*”

Analog

Information in form of **continuous** and **real-valued levels**

Variable can be only 1 out of an **infinite number of options**

The physical values exist naturally in continuous spectrum levels

- **Air pressure in this room**
- **Volume of my voice**
- **Battery voltage in your laptop**
- **Answer to the question** – “*How much are you enjoying this module?*”

Language – using letters

There are 26 alphabets in the English language – digital!

Binary

e.g.,
11100100

Octal

e.g.,
344

Numbers

Every number that we use, uses a distinct number of symbols (including the decimal point)

Decimal

e.g.,
228


Hexadecimal

e.g.,
E4

How does this actually relate to “numbers”?

Let us look at a number in the “Decimal” number-format, the one that we have grown up with.

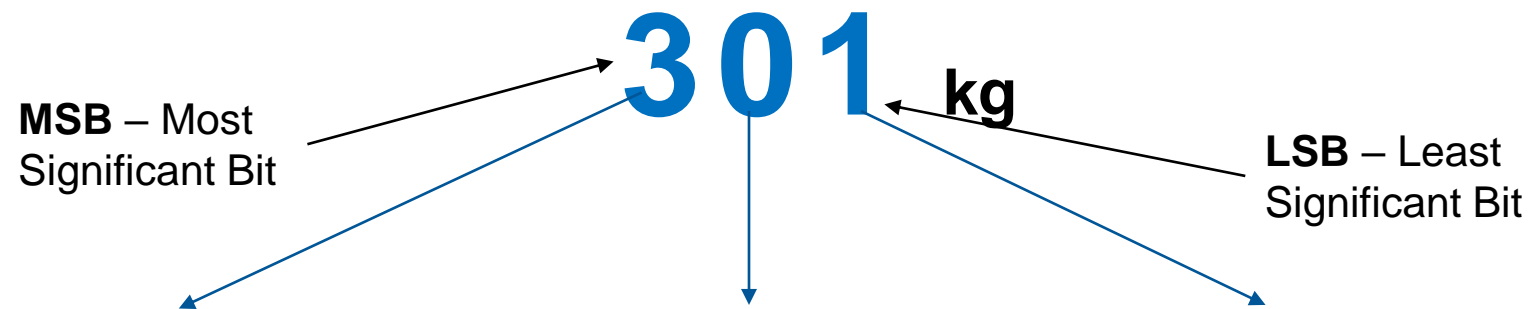Weight of the Formula Student 2021 car is



$$3 \times 10^2 = 300$$


$$0 \times 10^1 = 0$$

$$1 \times 10^0 = 1$$

How does this actually relate to “numbers”?

The same number in the Hexadecimal format will be

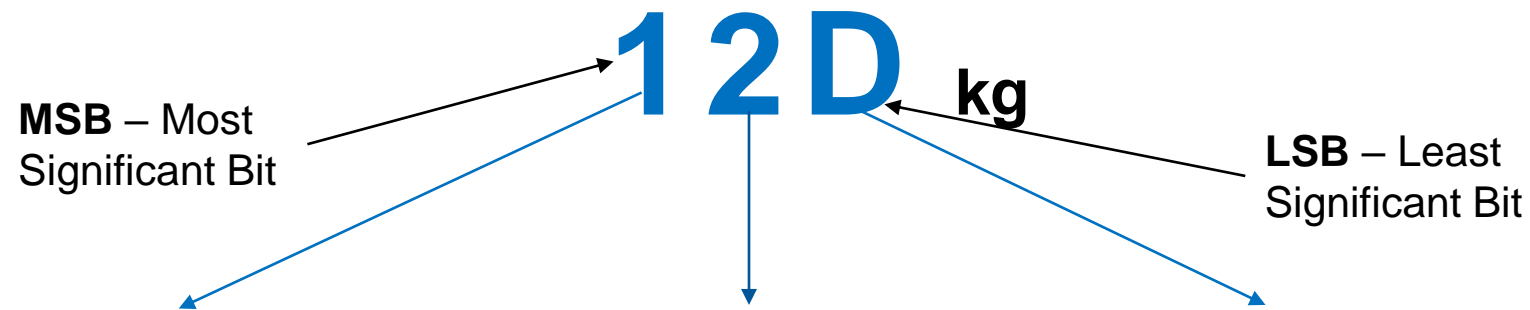Weight of the Formula Student 2021 car is



$$1 \times 16^2 = 256$$

$$2 \times 16^1 = 32$$

$$D \times 16^0 = 13$$

How does this actually relate to “numbers”?

How about in Binary?

Weight of the Formula Student 2021 car is

LSB – Least Significant Bit

MSB – Most Significant Bit

0001 0010 1101 kg

- $0 \times 2^{11} = 0$
- $0 \times 2^{10} = 0$
- $0 \times 2^9 = 0$
- $1 \times 2^8 = 256$

256

- $0 \times 2^7 = 0$
- $0 \times 2^6 = 0$
- $1 \times 2^5 = 32$
- $0 \times 2^4 = 0$

32

- $1 \times 2^3 = 8$
- $1 \times 2^2 = 4$
- $0 \times 2^1 = 0$
- $1 \times 2^0 = 1$

13

How to Add/Subtract Binary Numbers?

Just the same way you do for decimal numbers!

Decimal

$$\begin{array}{r}
 1 \\
 124 \\
 +229 \\
 \hline
 \mathbf{353}
 \end{array}$$

$$\begin{array}{r}
 124 \\
 - 47 \\
 \hline
 \mathbf{77}
 \end{array}$$

Binary

$$\begin{array}{r}
 1\ 1\ 1\ 1\ 1 \\
 0111\ 1100 \\
 +1110\ 0101 \\
 \hline
 \mathbf{1\ 0110\ 0001}
 \end{array}$$

$$\begin{array}{r}
 0111\ 1100 \\
 +0010\ 1111 \\
 \hline
 \mathbf{0100\ 1101}
 \end{array}$$

We don't normal do **multiplication** and **division** operations on binary numbers

We shall study **Binary Algebra** later



4-bit Binary Number Range

Decimal	B ₄	B ₂	B ₂	B ₁	Binary
0	0	0	0	0	0000
1	0	0	0	1	0001
2	0	0	1	0	0010
3	0	0	1	1	0011
4	0	1	0	0	0100
5	0	1	0	1	0101
6	0	1	1	0	0110
7	0	1	1	1	0111
8	1	0	0	0	1000
9	1	0	0	1	1001
10	1	0	1	0	1010
11	1	0	1	1	1011
12	1	1	0	0	1100
13	1	1	0	1	1101
14	1	1	1	0	1110
15	1	1	1	1	1111

We would call this a 4-bit binary number – it is made of 4 bits

Maximum number we can count up to for a binary number is given by $2^n - 1$


$$1 \text{ byte} = 8 \text{ bits}$$

Modern computers use **32-bit** or **64-bit** numbers in its operating system

Remember the numeric data types you learnt in MATLAB last year?

- **Single** – 4 bytes
- **Double** – 8 bytes
- **Int8** – 1 byte


AND

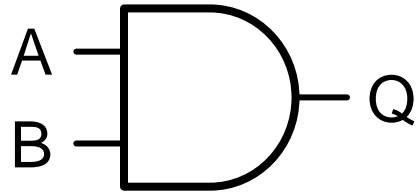

Truth Table


A	B	Q	Remark
0	0	0	HI if all inputs are HI
0	1	0	
1	0	0	
1	1	1	

OR

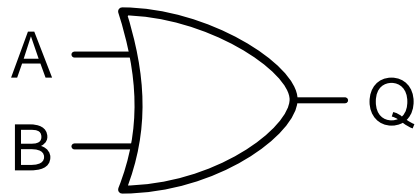



A	B	Q	Remark
0	0	0	HI if any input is HI
0	1	1	
1	0	1	
1	1	1	

NOT

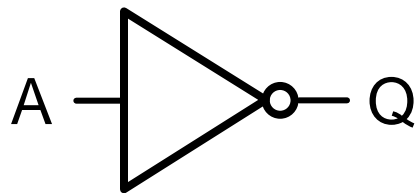


A	Q	Remark
0	1	Bit inversion
1	0	

This is an Integrated Circuit, or IC!

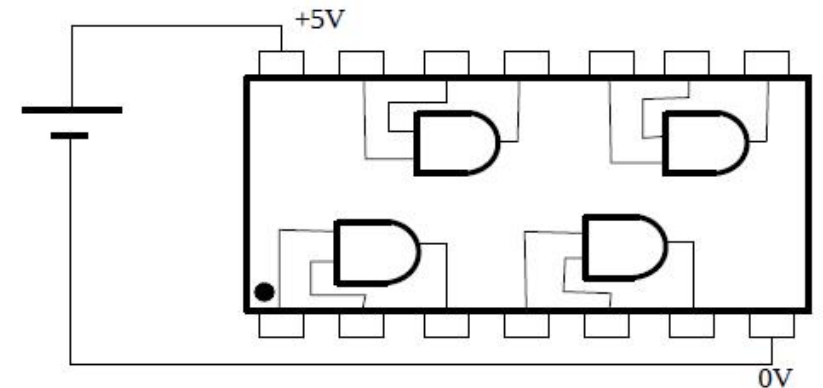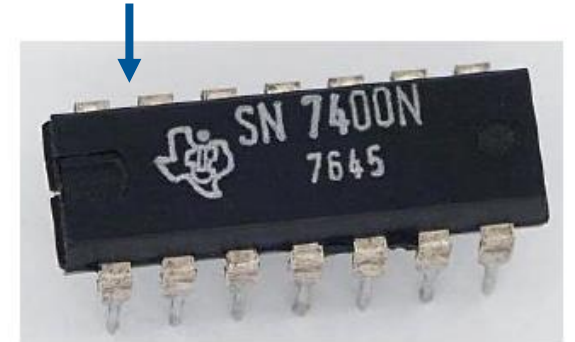


NAND

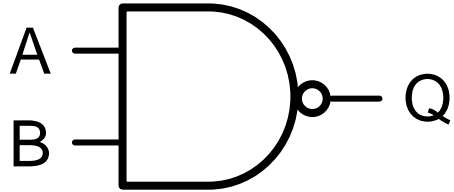

Truth Table


A	B	Q	Remark
0	0	1	LO if all inputs are HI
0	1	1	
1	0	1	
1	1	0	

NOR

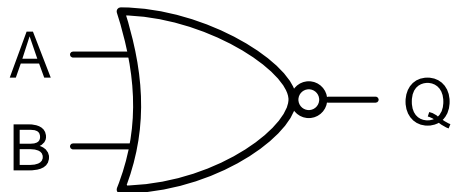



A	B	Q	Remark
0	0	1	LO if any input is HI
0	1	0	
1	0	0	
1	1	0	

XOR

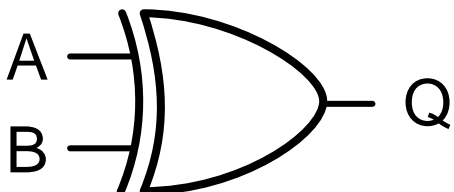


A	B	Q	Remark
0	0	0	HI if at least one input is HI and one is LO
0	1	1	
1	0	1	
1	1	0	

This is an Integrated Circuit, or IC!

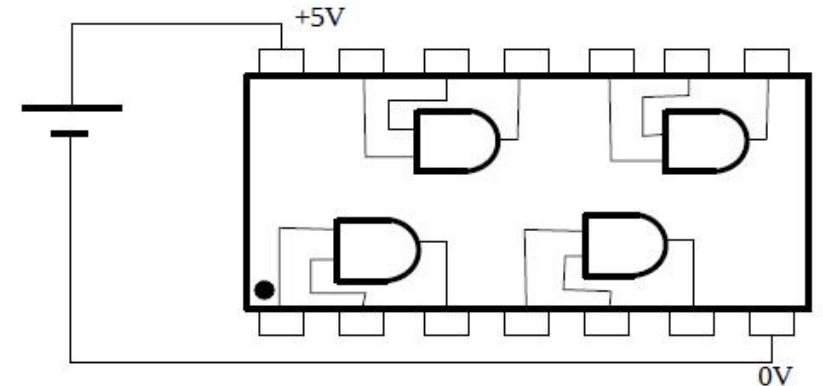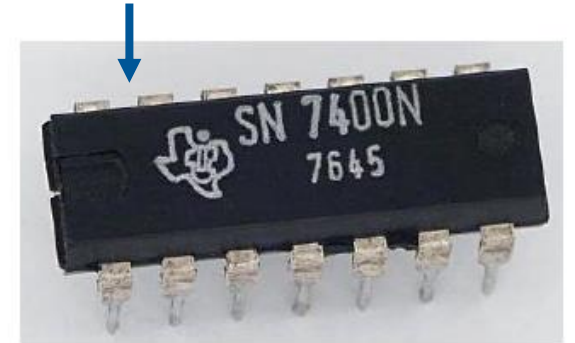

Don't need to study this for exam

Example 3

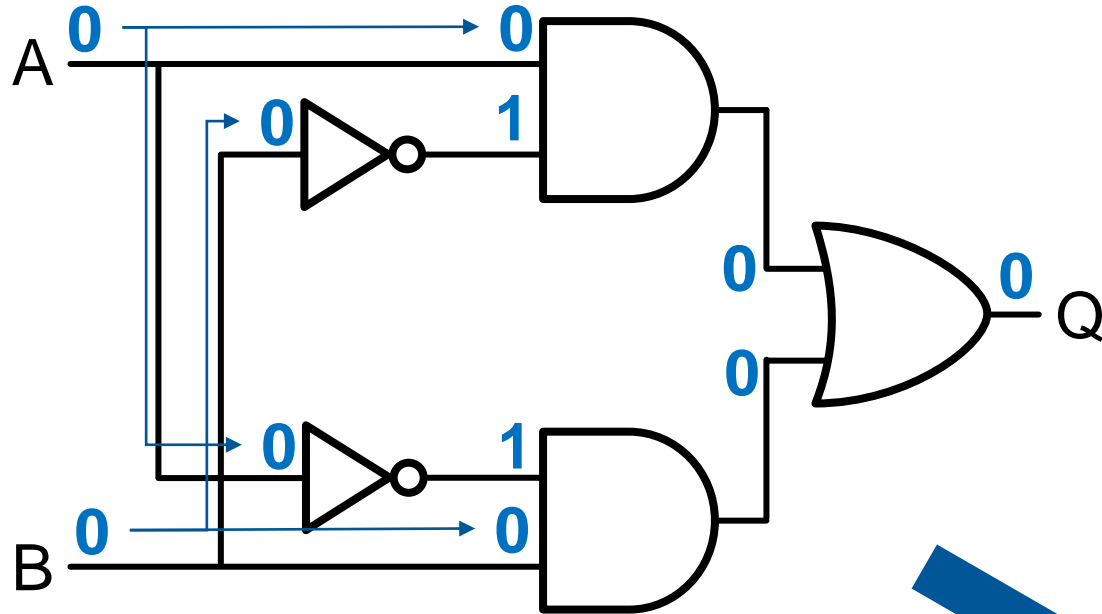

Total inputs = 2

Total combinations possible = $2^n = 4$

4 rows in truth table

A	B	Q	Remark
0	0	0	This is XOR gate
0	1	1	
1	0	1	
1	1	0	


~~Step 1 – Identify how many inputs there are~~

~~Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits~~

~~Step 3 – Try each input combination in the logic gate~~

~~Step 4 – Propagate the “logic” all the way to output~~

~~Step 5 – Fill the truth table row by row~~


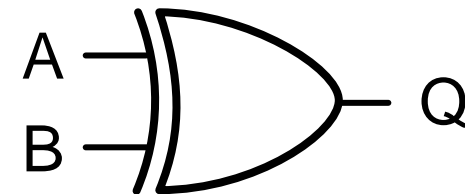


Example 4


- Imagine you are designing a circuit to monitor a digital thermometer embedded in a nuclear reactor
- You want to automatically shut off the reactor when the cooling fluid rises above 50°C
- It would also be bad if the coolant froze – shut down the reactor!
- Thermometer gives a 3-bit binary output in 10°C steps –
 - $2^3 = 8$ levels
 - Count from 0 to $2^3 - 1 = 7$
 - 0°C to 80°C range of output

$S=1$ (as we said solving for HI) if:


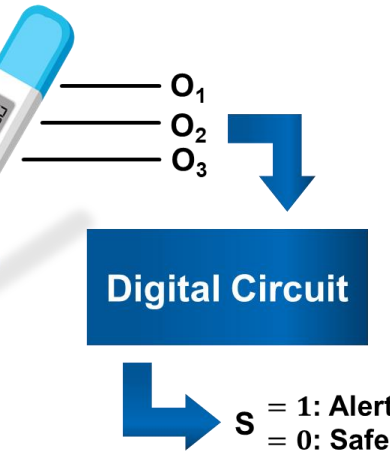
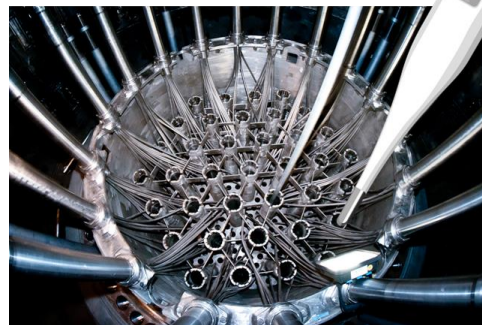
- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$



O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

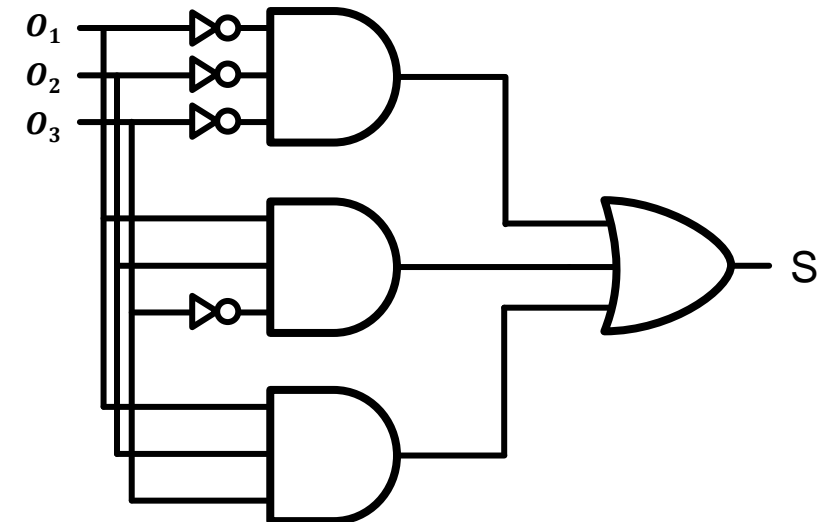

Example 5

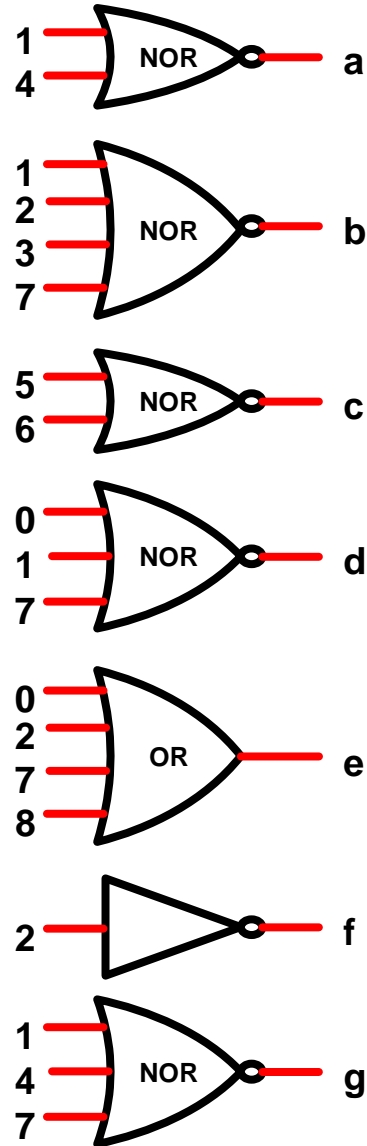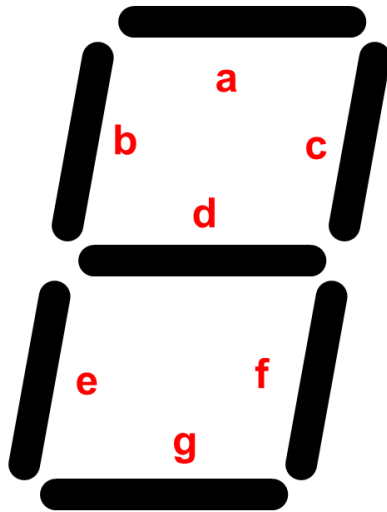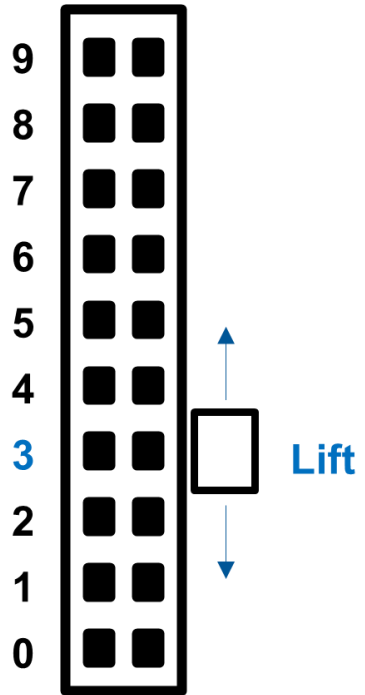


	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7	1	0	1	0	0	1	0
8	1	1	1	1	1	1	1
9	1	1	1	1	0	1	1

Boolean Algebra is like regular algebra – but instead of numbers, it operates with logical variables true and false, also denoted by 1 and 0 respectively

This is used to simplify logical circuits mathematically, i.e., instead of solving a complicated digital logic circuit via propagation of signal, you can simplify it mathematically using certain laws

There are three operators:

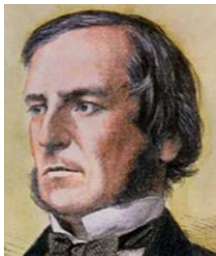


George Boole, self-taught English mathematician wrote the book *The Laws of Thoughts* (1854) and introduced Boolean Algebra

Operation	Symbol	Logic Gate
Conjunction	\wedge or $.$	AND
Disjunction	\vee or $+$	OR
Negation	\neg or $'$ or overhead bar	NOT

Truth Table


AND

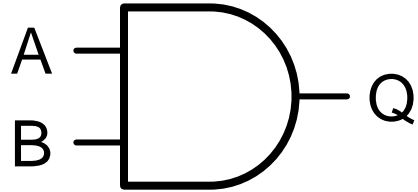

A	B	Q	Remark
0	0	0	HI if all inputs are HI
0	1	0	
1	0	0	
1	1	1	

$$Q = A \cdot B = A \wedge B$$


OR

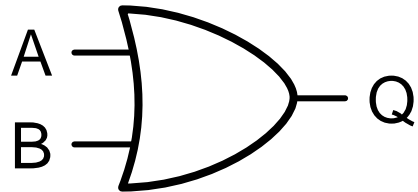

A	B	Q	Remark
0	0	0	HI if any input is HI
0	1	1	
1	0	1	
1	1	1	

$$Q = A + B = A \vee B$$

NOT

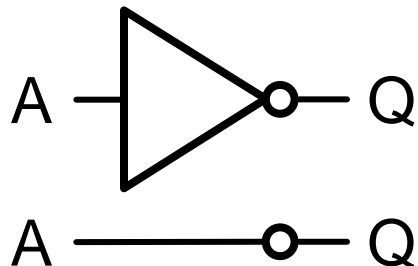


A	Q	Remark
0	1	Bit inversion
1	0	

$$Q = A' = \neg A = \bar{A}$$




Boolean Algebra

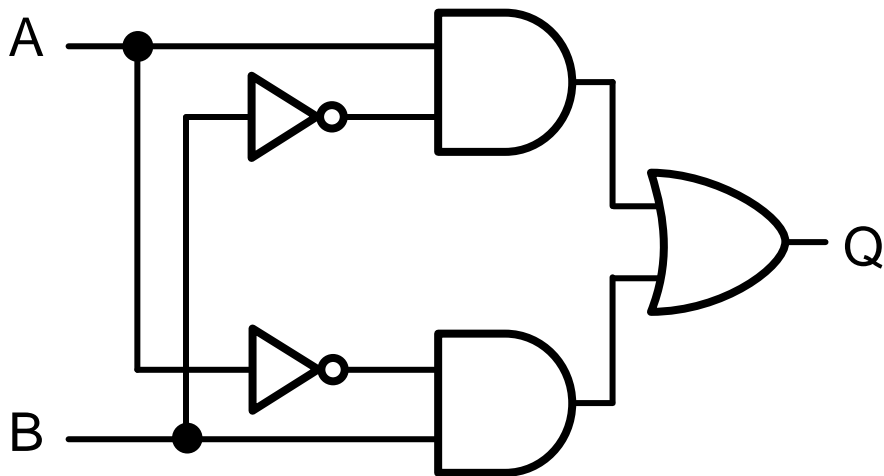

$$Q = A \cdot B' + A' \cdot B$$
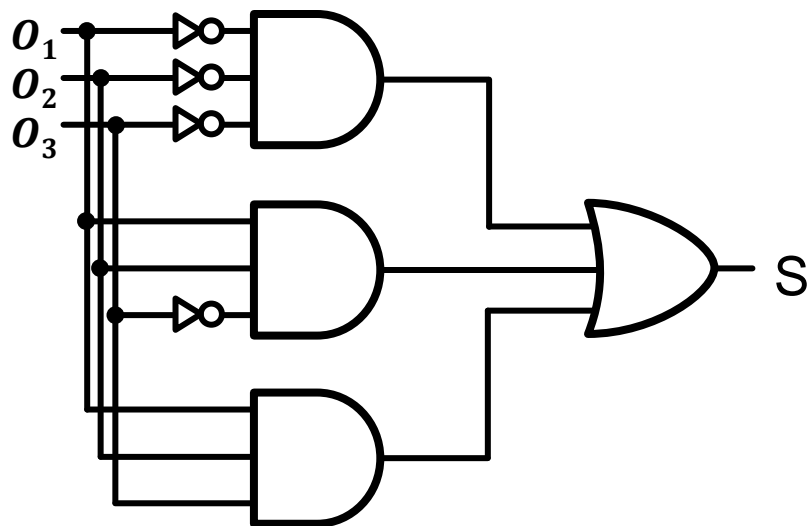
$$Q = A \cdot \bar{B} + \bar{A} \cdot B$$



$$S = O'_1 \cdot O'_2 \cdot O'_3 +$$

$$O_1 \cdot O_2 \cdot O'_3 + O_1 \cdot O_2 \cdot O_3$$



Boolean Law	Example 1	Example 2	Example 3
Annulment	$A \cdot 0 = 0$	$A + 1 = 1$	
Identity	$A \cdot 1 = A$	$A + 0 = A$	
Idempotent	$A \cdot A = A$	$A + A = A$	
Complement	$A \cdot A' = 0$	$A + A' = 1$	
Commutative	$A \cdot B = B \cdot A$	$A + B = B + A$	
Associative	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$	
Distributive	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$	$A + A' \cdot B = A + B$
Involution	$(A')' = A$		
De Morgan's	$(A + B)' = A' \cdot B'$	$(A \cdot B)' = A' + B'$	



- DC Motor
 - **Revision** of all motors studied so far – Induction, Stepper
 - **Operation** of a **Simple DC Motor**
 - **Why** use a DC Motor?
- **Boolean Algebra**
 - **Revision of Digital Electronics**
 - **Addition (OR), multiplication (AND), complement (NOT)**
 - **Laws**



Attendance



UP|PHY|B1-MMME2051EMD