



- Q1. There are 500 electrons flowing across the cross-sectional area of a copper wire every 5 seconds from A to B. What is the current in the copper wire from A to B?
- Q2. In the above situation, what is the current flowing from B to C?
- Q3. In the above situation, what is the current flowing from C to D?
- Q4. In the above situation, what is the current flowing from B to D?
- Q5. How many electrons would have to flow (and what direction) for there to be 5A of current flow from A to D?
- Q6. Say we had to apply 10V at A with respect to D to have 5A of current flow in the resistor. How much is the resistance of the resistor?
- Q7. The resistor is between B and C, the copper wire (between A and B, and between C and D) has zero resistance. What is the voltage between A and B?
- Q8. What is the voltage at B with respect to D?
- Q9. What is the power flow from C to B?
- Q10. Is voltage an across variable or through variable? Why?
- Q11. Is current an across variable or through variable? Why?



- Q12. You have been presented with an inductor (above). There is 10A of current flowing through it, i.e., $I = 10A$. As you have not been told how long the current has been flowing, you should assume it has been flowing a long time. What happens if you suddenly open-circuit the inductor, i.e., stop any current flow through the inductor?
- Q13. In the above situation (i.e., the moment when $I = 0A$ changed from $I = 10A$), would there be a voltage induced across the inductor? What would be the value of V (be careful about the polarity)?
- Q14. Say we had an identical situation, but with a capacitor instead of an inductor, and you open-circuited the capacitor while there was 10A current flowing through it, what would happen? What would be the new value of V across the capacitor?
- Q15. With the capacitor, what would have happened if you had short-circuited the capacitor (instead of open-circuit)?
- Q16. When we “open-circuit an element”, we are forcing (select option(s) from below) –
- Current flowing through it to be zero
 - Current flowing through it to be infinity
 - Voltage across it to be zero
 - Voltage across it to be infinity
- Q17. When we “short-circuit an element”, we are forcing (select option(s) from below) –
- Current flowing through it to be zero
 - Current flowing through it to be infinity
 - Voltage across it to be zero
 - Voltage across it to be infinity
- Q18. In an inductor, the voltage across it is proportional to (select option(s) from below) –
- Current through it
 - Rate of change of current through it
- Q19. In a capacitor, the current through it is proportional to (select option(s) from below) –
- Voltage across it
 - Rate of change of voltage across it