

## Electromechanical Devices MMME2051EMD

### Exercise Sheet 1 - Basic electrical principles and laws

- 1.1 For the circuit shown in Fig 1.1, calculate the current supplied by the battery, voltage across 2.2k $\Omega$  resistor, power dissipated in that resistor and power supplied by the battery. (Hint: start by finding the effective resistance of two of the resistors then the current in that pair of resistors).

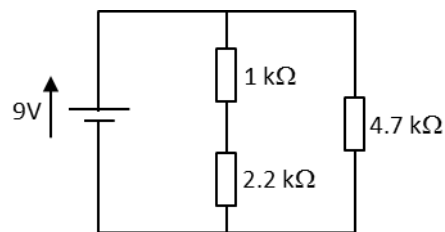


Fig 1.1

*4.72mA, 6.19V, 17.4mW, 42.5mW*

- 1.2 The digital outputs from an Arduino microcontroller give a voltage of 5V with respect to ground (Fig, 1.2). It is desired to drive an LED indicator, which needs a current of 13 mA and has a voltage drop of 2.1V across it. To avoid damage a resistor is put in series with the LED. What voltage drop is required across a resistor? What resistor is needed to get desired current?


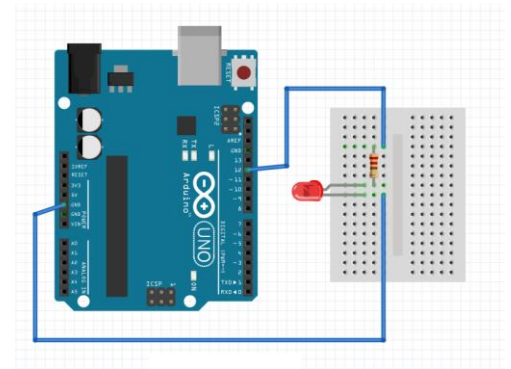


Fig. 1.2

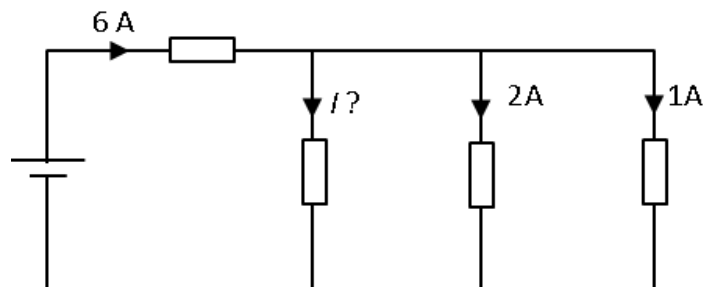- 1.3 What is the unknown current shown in Fig. 1.3?



*3A*

- 1.4 Fig. 1.4 shows a car battery connected to a lamp which is drawing 3A and a heater (shown as a resistor) which is drawing 8A. A generator is supplying 10A (via a resistor) to the circuit in an attempt to charge the battery. What is the current  $I$  and which direction is it in? Is the battery charging or discharging? (Hint: direction of  $I$  is not shown but you can choose convention for positive  $I$  arbitrarily then find actual direction from sign of answer).

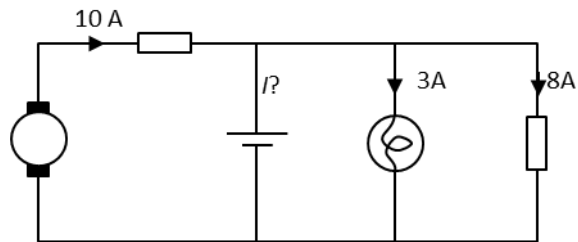


Fig. 1.4

*Current is 1A in an upward direction: battery is discharging.*

- 1.5 For the circuit shown in Fig 1.5, calculate the equivalent resistance across the battery, current  $I$ , voltage across 2.2k $\Omega$  resistor, power dissipated in 4.7k $\Omega$  resistor and power supplied by the battery.

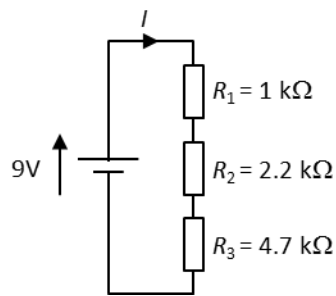


Fig 1.5

*7.9 k $\Omega$ , 1.14mA, 2.51V, 6.1mW, 10.3mW.*

- 1.7 For the circuit shown in Fig 1.7, calculate the equivalent resistance across the battery, the current supplied by the battery, current through 2.2k $\Omega$  resistor, power dissipated in 4.7k $\Omega$  resistor and power supplied by the battery.

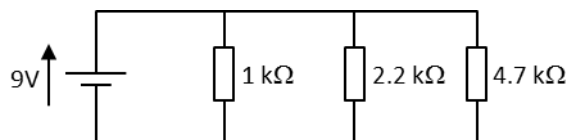


Fig 1.7

*0.6 k $\Omega$  or 600 $\Omega$ , 15mA, 4.1mA, 17.2mW, 135mW.*

- 1.8 A DC motor is fed with a current of 1.5 A from a 12 V battery via a diode with a voltage drop of 0.7 V and via wiring of resistance  $1.5 \Omega$  (Fig. 1.8). What is the potential difference  $V$  across the motor?

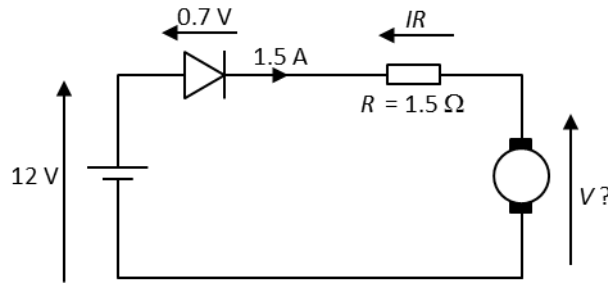


Fig. 1.8

9.05 V

**Consolidation/revision question**

- 1.9 For the circuit shown in Fig 1.5, the supply voltage is measured as 11.5V and the total current drawn is 2.5A. If the resistor is known to have a resistance of  $12 \Omega$ , what is the current  $I$  flowing in the lamp? (Hint: use Ohm's law followed by Kirchhoff's current law).

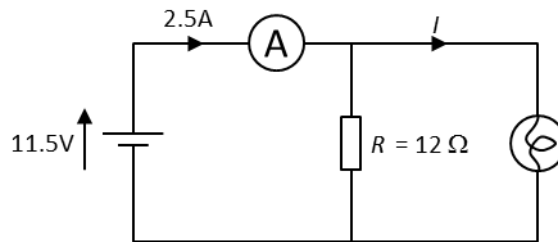


Fig 1.9

1.54 A.