



## Electromechanical Devices MMME2051

---

### Exercise Sheet 11 – Transformers

---

- 11.1 A 240V:12V 50Hz transformer supplies a secondary (low voltage) load comprising  $3\Omega$  resistor and 12.7mH inductor. Calculate the primary current in Cartesian notation and polar notation.

$$0.072 - j0.96A = 0.12A \angle -53.1^\circ$$

- 11.2 A transformer has a primary:secondary turns ratio of 20:1 and is supplied from a 240 V (rms) 50 Hz ac supply. If its load is a  $10\Omega$  resistor, what current does the transformer draw, and hence what is the resistance of the load referred to the primary? Ignore magnetisation current and assume the transformer is 100% efficient.

$$60 \text{ mA}; 4000 \Omega$$

- 11.3 A 240V:120V 60Hz transformer has its low voltage winding connected to 120V supply (so note the way around the transformer is connected!). Across the high voltage winding is a resistor in series with a capacitor. The supply current is  $(0.8 + j0.6)$  A. Calculate the current in the load in Cartesian and polar form, the impedance of the load and the resistance and capacitance.

$$0.4 + j0.3A, 0.5A \angle 36.9^\circ; 384 - j288\Omega; 384\Omega, 9.2\mu F$$

- 11.4 8.4 A 200V : 50V 60Hz transformer supplies a load comprising a  $10\Omega$  resistor in series with a 100mH inductor. Calculate the load impedance, secondary current, power dissipated in the load, equivalent impedance for the transformer and the load, primary current, and power supplied.

$$39\Omega \angle +75.1^\circ, 1.28A \angle -75.1^\circ, 16.5W, 624\Omega \angle +75.1^\circ, 0.32A \angle -75.1^\circ, 16.5W$$