



Electromechanical Devices MMME2051

Exercise Sheet 7 – Digital Electronics 2

- 7.1 Draw the truth table of a JK flip flop.
- 7.2 Explain in words why is it impractical to use a simple OR gate with a feedback loop as a latch.
- 7.3 Draw a Shift Register and name one application of this type of circuit.
- 7.4 Simplify the following expressions:

- a. $1 + 1 + 1$
- b. $1 + 0 + 0$
- c. $1' + 1' + 1'$
- d. $0 + 0 + 0$

Note: A single apostrophe (') after a binary variable is a way of denoting "complement/inverse" of the variable – NOT gate!

- 7.5 Simplify the following expressions:

- a. $A * 1$
- b. $A * 0$
- c. $A + 1$
- d. $A + A$
- e. $A * A$
- f. $A + A + B$
- g. $(A + B) * (A + C)$
- h. $(A + B) * (A + C) * (A' + C) * (B' + D)$

- 7.6 Now draw the circuits (using gate symbols) from above.
- 7.7 Given the following truth table, write the Boolean algebra expression to represent it. Can you simplify the answer?

A	B	C	Q
0	0	0	1
0	0	1	0
0	1	0	1

0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

- 7.8 Draw a diagram of a relay and explain how it works.
- 7.9 Why can't we supply large voltage and currents from microchips?
- 7.10 Draw a circuit diagram for a circuit that would use a small voltage/current signal to turn on a 20V light bulb using an NPN bipolar junction transistor.
- 7.11 What are the advantages/disadvantages of bipolar junction transistor?
- 7.12 What are the advantages/disadvantages of using a MOSFET? Why would you use a push-pull pair to drive a MOSFET?
- 7.13 Draw a circuit diagram showing how a push-pull pair would be used to drive a MOSFET and describe what the advantages of using a push-pull pair to drive a MOSFET are. Explain how the circuit works.