



University of
Nottingham

UK | CHINA | MALAYSIA

LECTURE 3A

Circuits Revision & AC Power

Electromechanical Devices MMME2051

Module Convenor – Surojit Sen



- Revision of circuits
 - **Sinusoidal** waveform – phase **angle v time?**
 - **Phasors**
 - Series/Parallel **clarification**
 - **Impedance**
 - **General Rule to solve circuits**
 - **Potential Divider Rule**
- Power in AC circuits
 - **Active v Reactive v Apparent Power**
 - **Power Factor**
 - **Resonance**

Sinusoid is a mathematical curve defined in terms of the **sine trigonometric function**

Sine and **Cosine** are both examples of sinusoid


Cosine function is simply the Sine function, but **90° advanced**

We will use the **Cosine** function to represent variables



$$y(t) = A \cos(\omega t + \phi)$$

Variable as function of time (points to $y(t)$)
 Amplitude (points to A)
 Frequency (points to ω)
 Phase Angle (points to ϕ)
 Phase offset (points to ϕ)
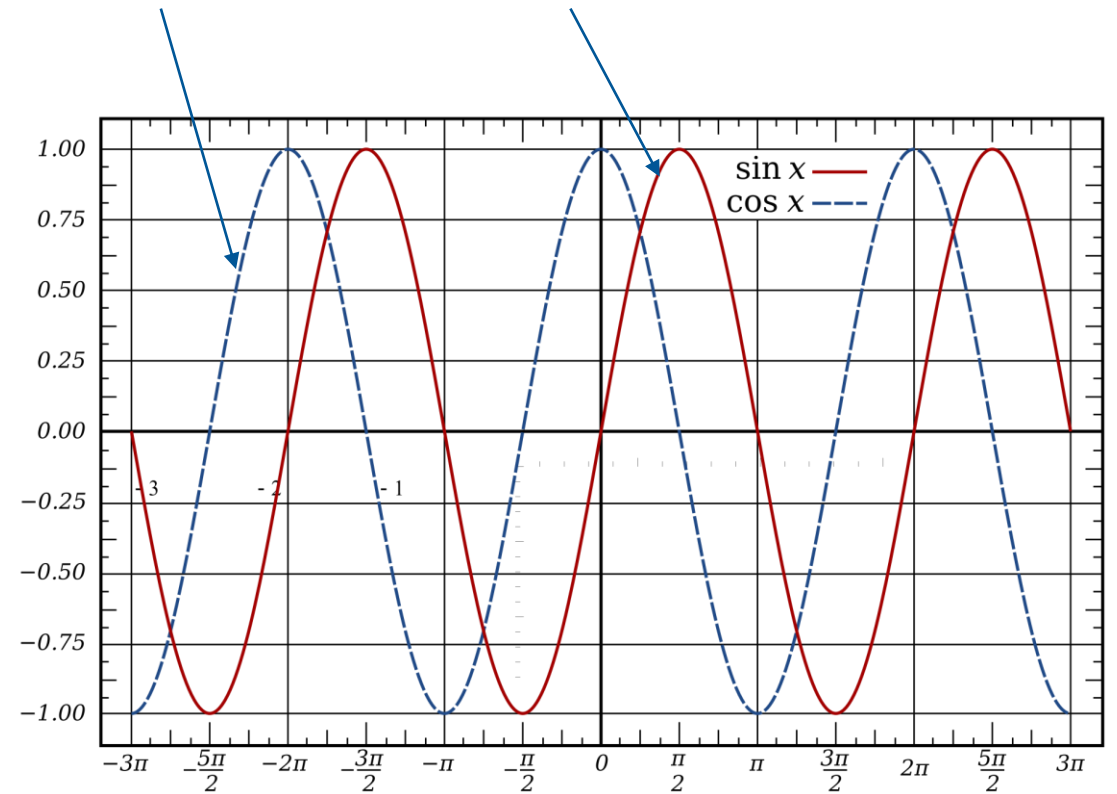
$$x_1(t) = \cos t \quad x_2(t) = \sin t$$




Sinusoid – Phase Angle

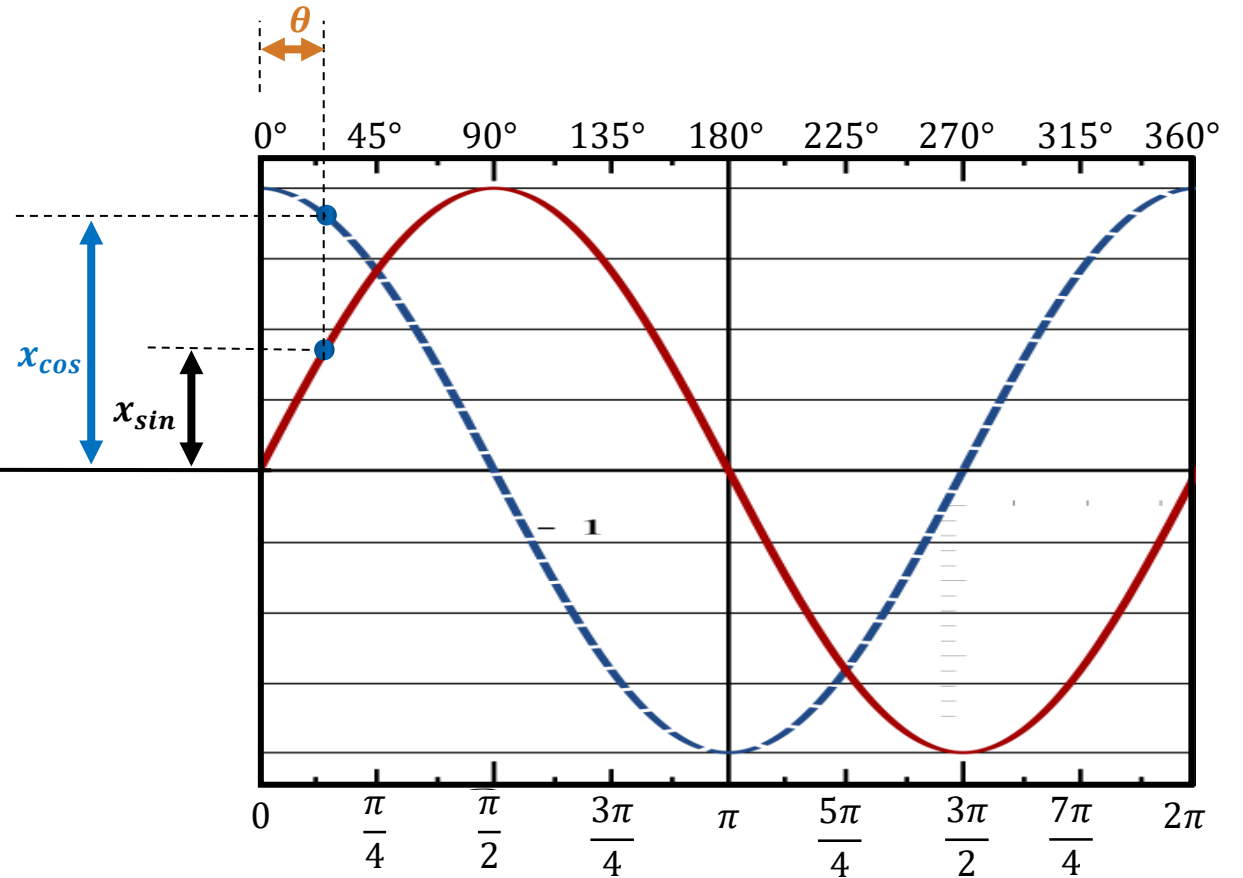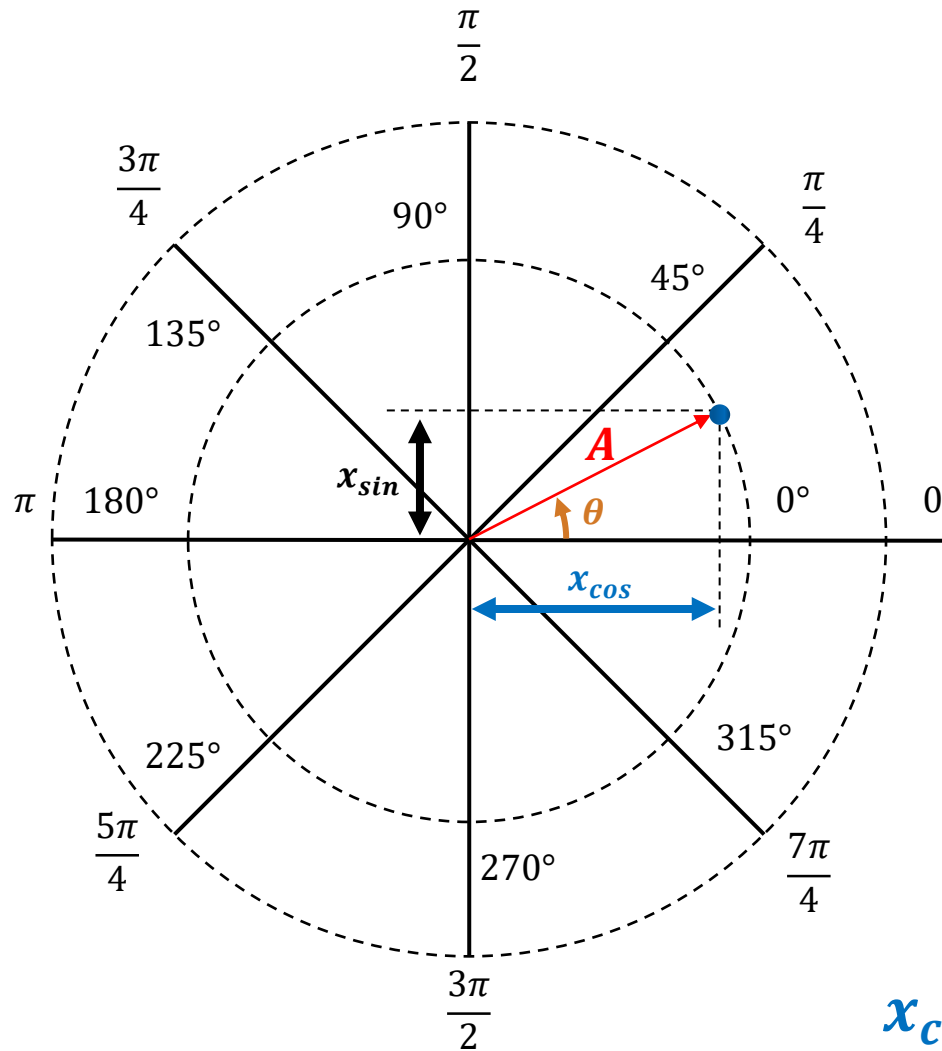

$$x_{cos} = A \cos(\theta)$$

$$x_{sin} = A \sin(\theta)$$

Sinusoid – Phase Angle

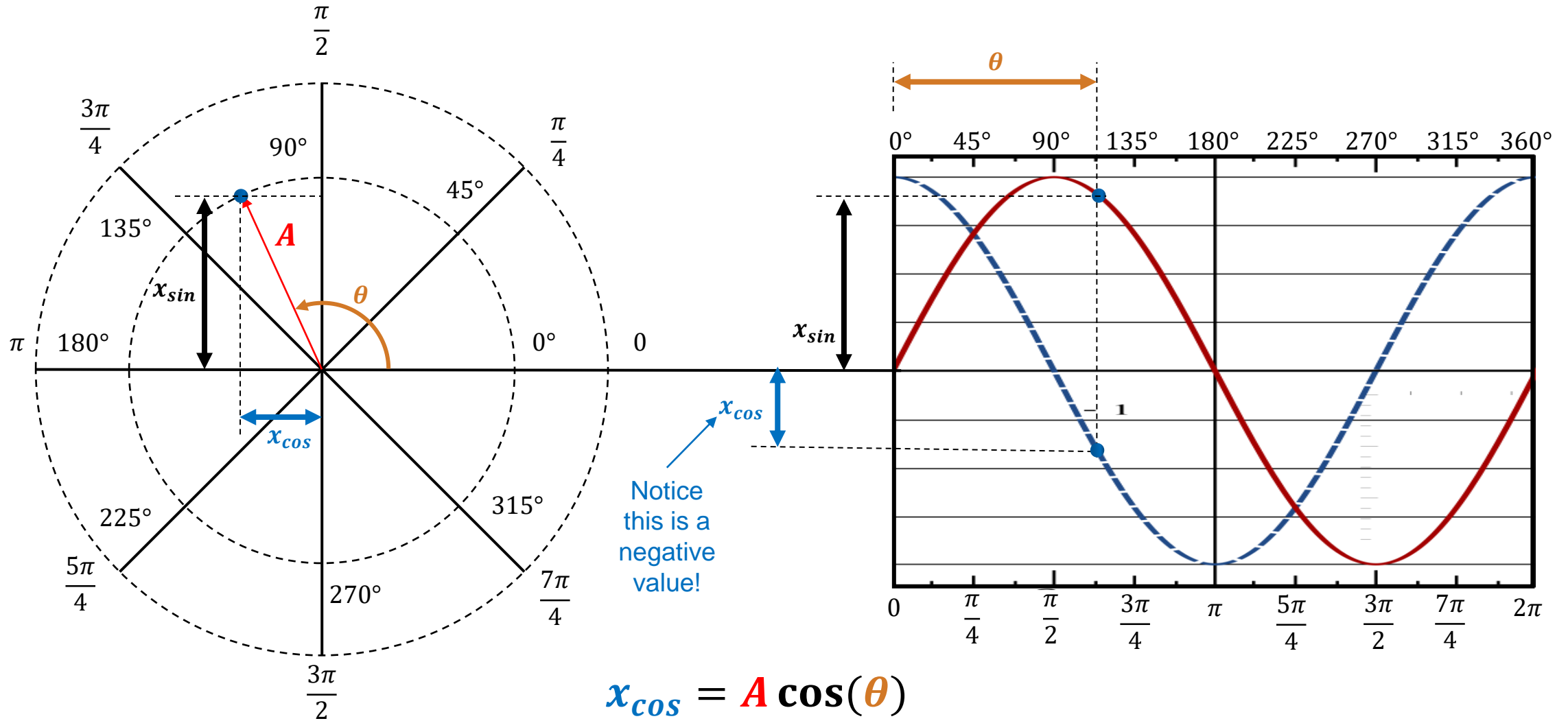


$$x_{cos} = A \cos(\theta)$$

$$x_{sin} = A \sin(\theta)$$



Sinusoid – Phase Angle

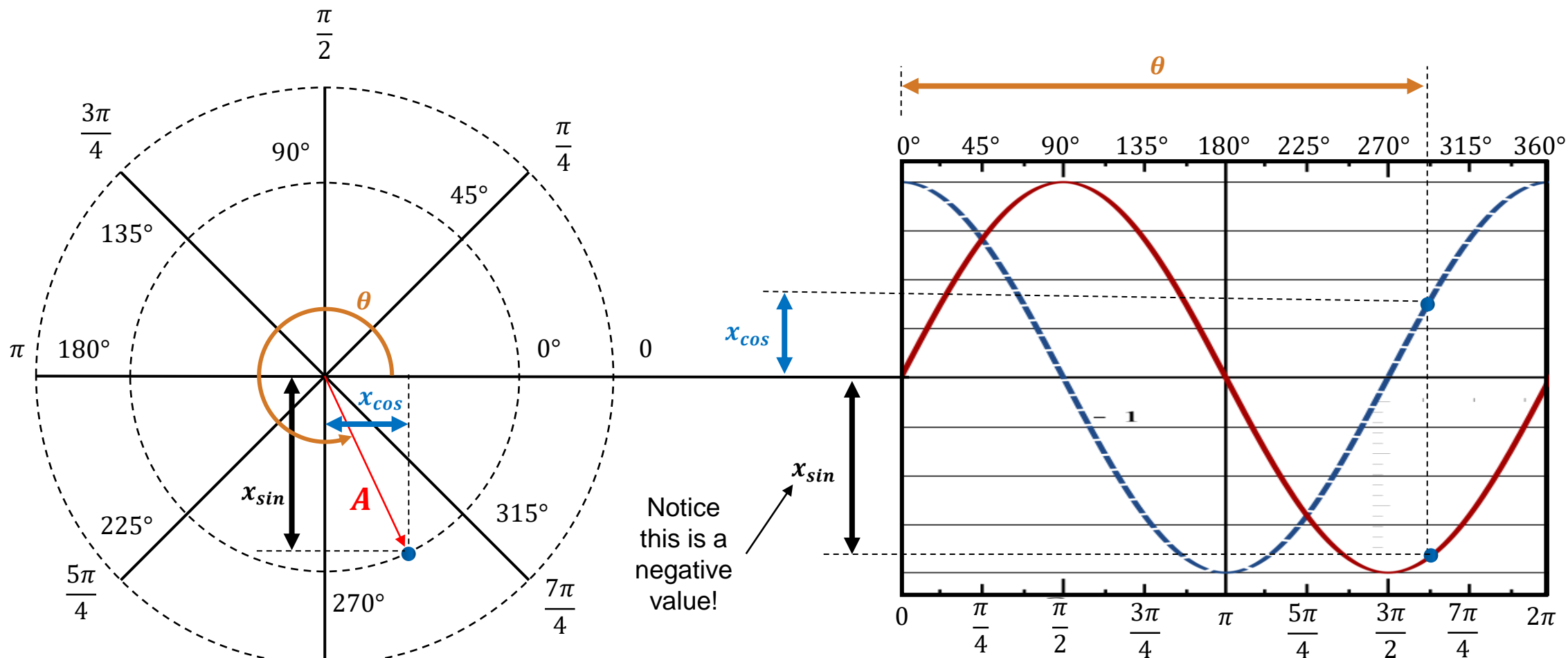

$$x_{cos} = A \cos(\theta)$$

$$x_{sin} = A \sin(\theta)$$

Sinusoid – Phase Angle v Time?

Why are we denoting points on the x-axis with angle values?

Shouldn't x-axis have values in seconds?

$$y(t) = A \cos(\omega t + \phi)$$

$$y(t) = A \cos \theta$$

$$\omega t + \phi = \theta$$


So let us say we are talking about a 50 Hz signal with 0° phase offset

$$2\pi f t + 0 = \theta$$

$$t = \frac{\theta}{2\pi \times 50} = \frac{\theta}{100\pi}$$

$$t = 0 \text{ when } \theta = 0$$
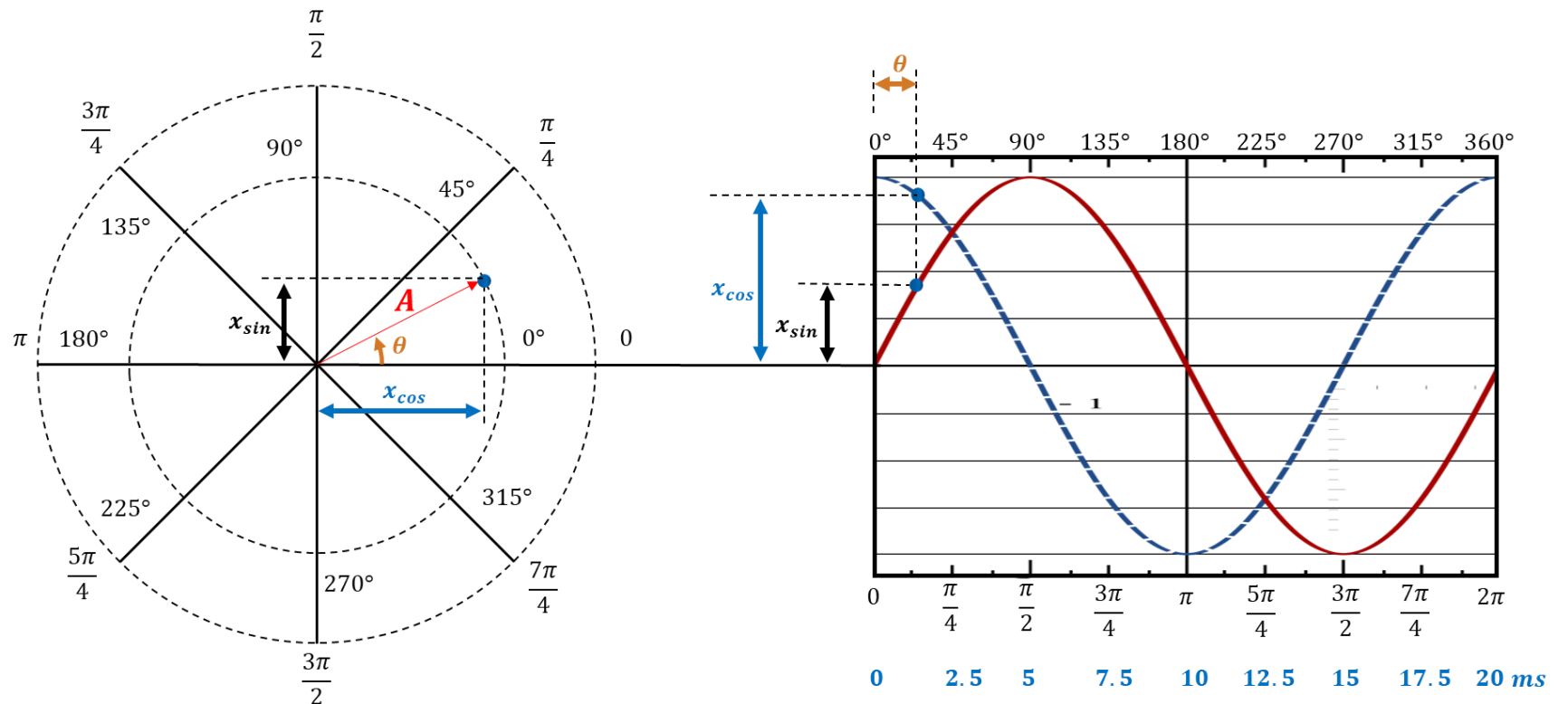
$$t = 20\text{ms} \text{ when } \theta = 2\pi$$



Sinusoid – Phase Angle v Time?

Let us try another example

$$y(t) = A \cos(\omega t + \phi)$$

$$y(t) = A \cos \theta$$

$$\omega t + \phi = \theta$$


So let us say we are talking about a 50 Hz signal with $\frac{\pi}{4}$ phase offset

$$2\pi f t + \frac{\pi}{4} = \theta$$

$$t = \frac{\theta - \frac{\pi}{4}}{2\pi \times 50} = \frac{\theta - \frac{\pi}{4}}{100\pi}$$


$$t = -2.5ms \text{ when } \theta = 0$$
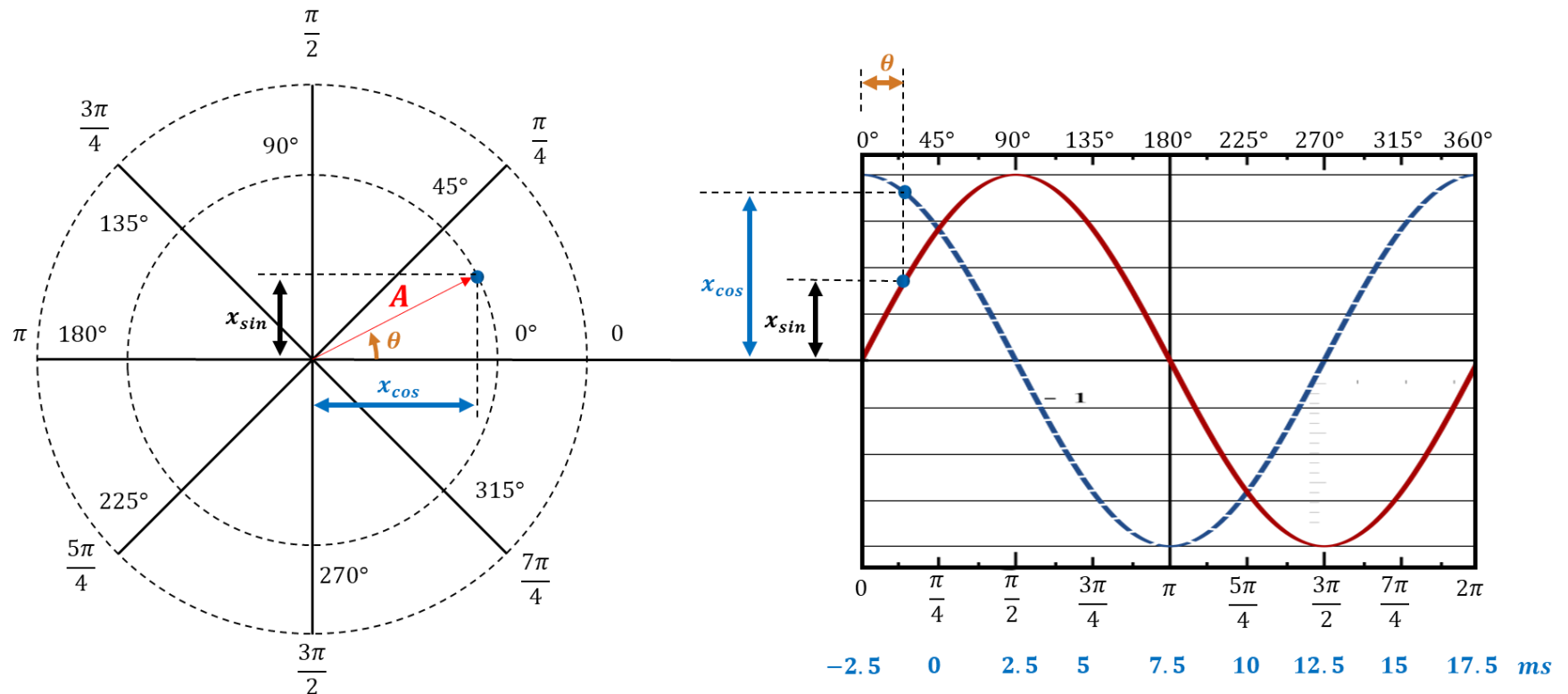
$$t = 17.5ms \text{ when } \theta = 2\pi$$




Sinusoid – Amplitude/Frequency/Phase Offset




Maximum magnitude of the variable

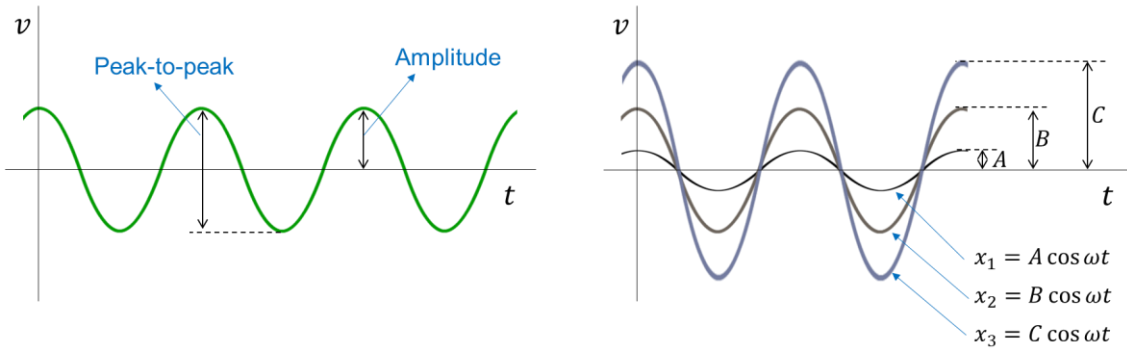

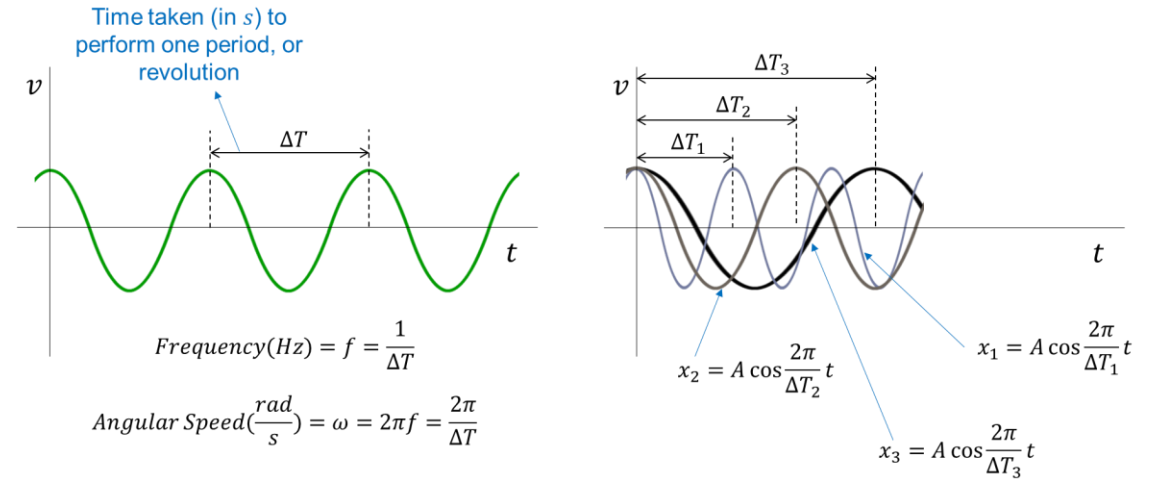Indicates how fast is the variable changing



Phase angle at $t = 0$

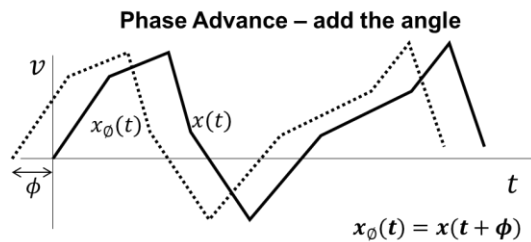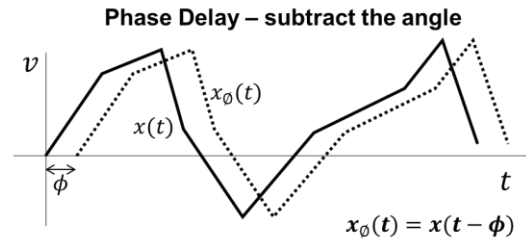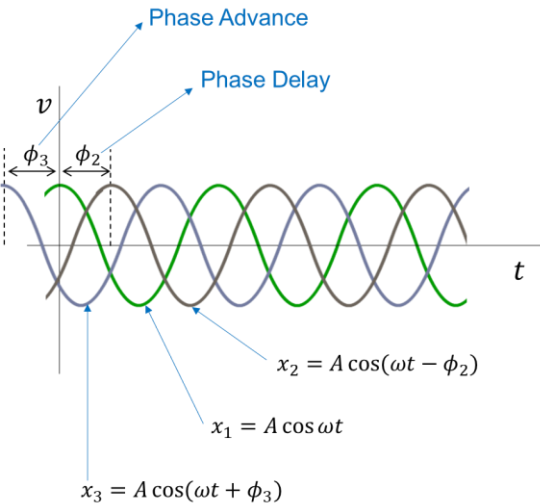

$$y(t) = A \cos(\omega t + \phi)$$

Variable as function of time (points to $y(t)$)
 Amplitude (points to A)
 Frequency (points to ω)
 Phase Angle (points to ϕ)
 Phase offset (points to ϕ)



Cartesian Form – Use the x & y coordinates to represent the complex number

$$4 + j3$$

$$x + jy \text{ (general form)}$$

Polar Form – Use the magnitude & angle to represent the complex number

$$5 \angle 37^\circ$$

$$|V| \angle \theta \text{ (general form)}$$

Exponential Form – Variation of Polar Form

$$Re[5e^{j37^\circ}]$$

$$Re[|V|e^{j\theta}] \text{ (general form)}$$

Cartesian to Polar Conversion

$$|V| = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$


Polar to Cartesian Conversion

$$x = |V| \cos \theta$$

$$y = |V| \sin \theta$$


Addition/Subtraction

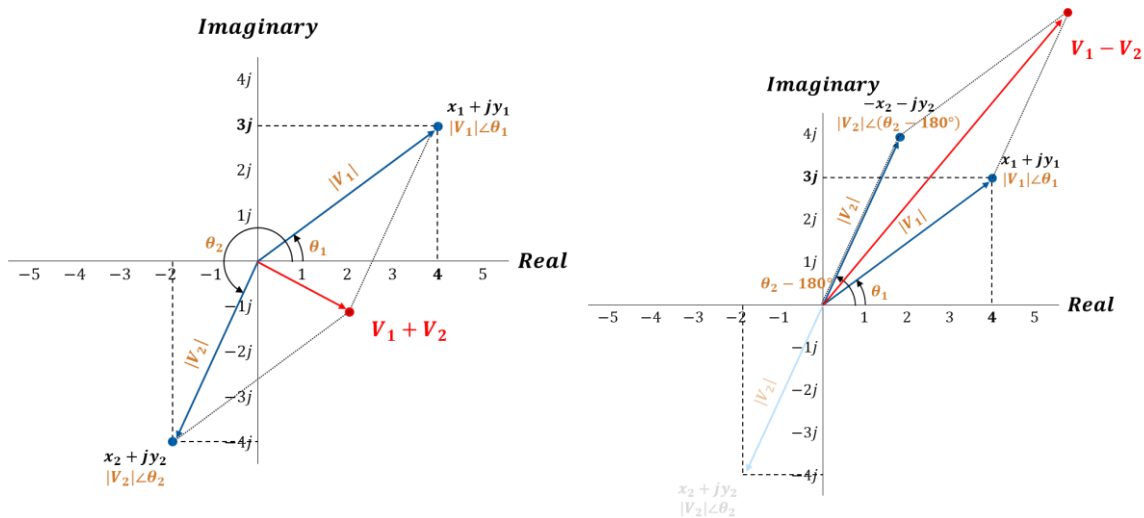- Convert to cartesian form
- Add/subtract the real terms
- Add/subtract the imaginary terms




Multiplication/Division

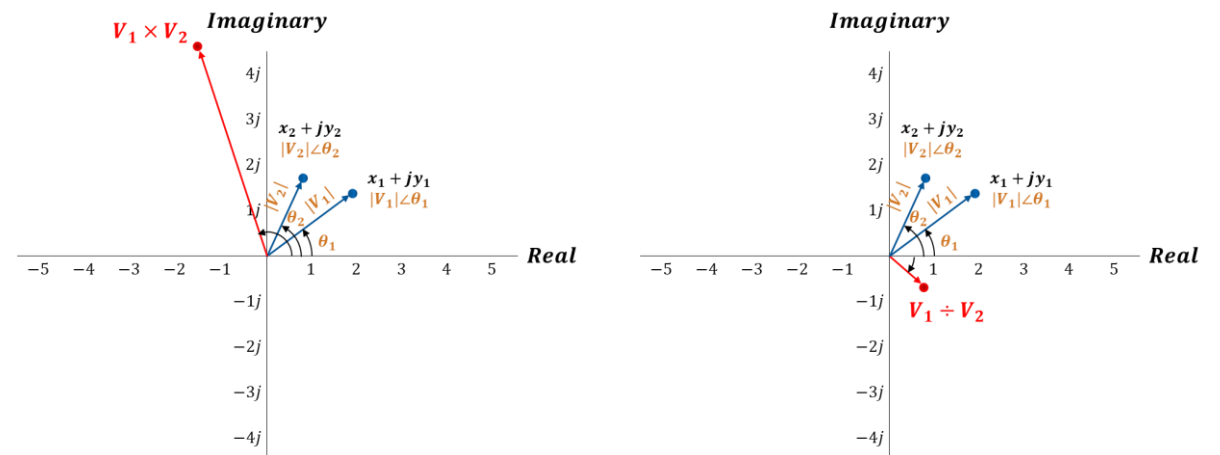- Convert to polar form
- Multiply/divide the magnitudes
- Add/subtract the angles



Phasor

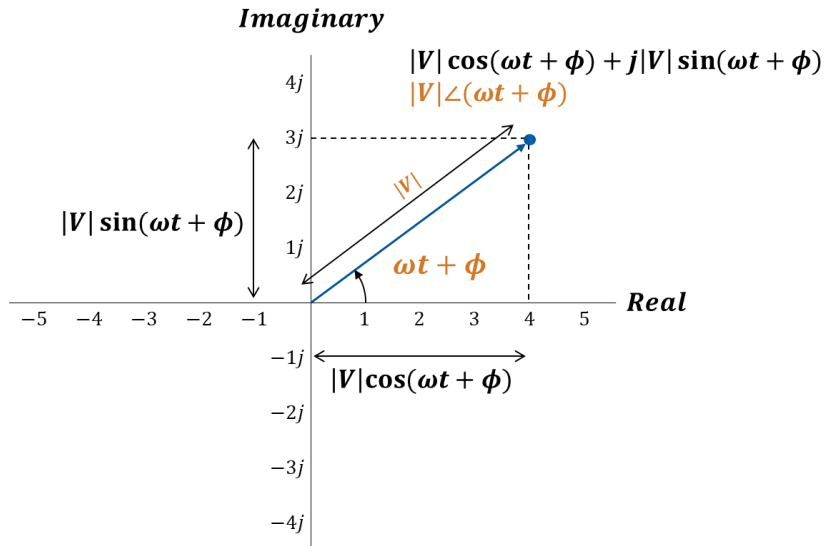


Say we have a voltage variable $v = |V|\cos(\omega t + \phi)$

We may represent it with a “phasor” which is nothing but a complex number that represents the initial position of the rotating vector (i.e., at $t = 0$), and say the “projection on positive real axis” is the value of the physical variable


For example, voltage $v = 150 \cos(50t + 25^\circ)$ may be represented in the phasor form as follows:

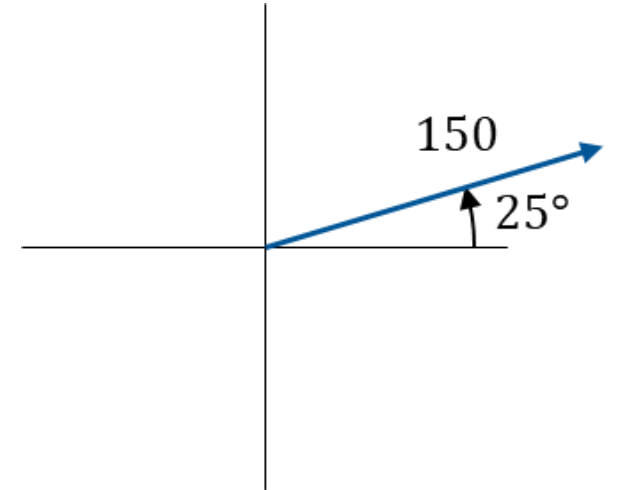Numeric Form – $150\angle 25^\circ$
Visual Form –




For example, current $i = 10 \cos(50t - \frac{\pi}{6})$ may be represented in the phasor form as follows:

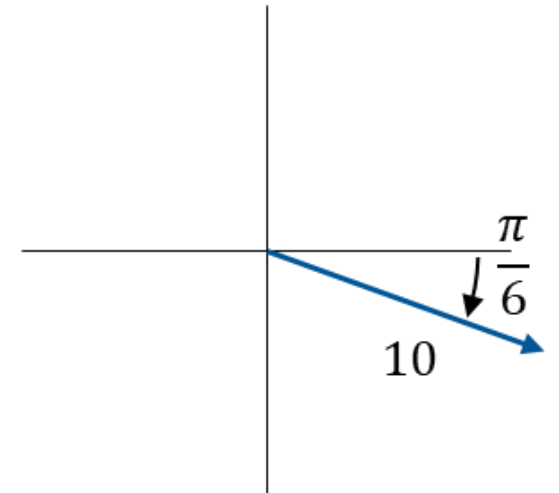Numeric Form – $10\angle \frac{\pi}{6}$
Visual Form –




Impedance


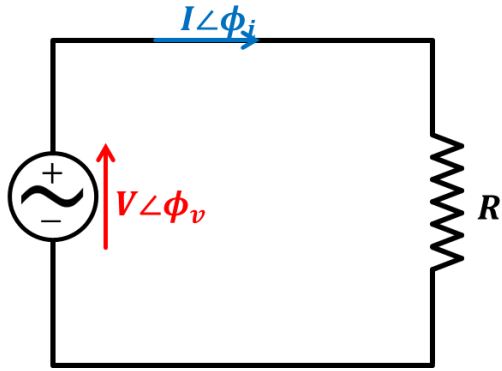


$$Z_R = R$$
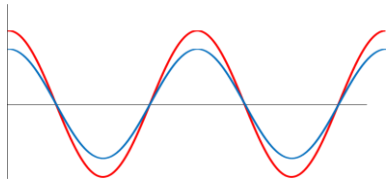
$$\frac{V}{R} \angle \phi_v = I \angle \phi_i$$




current in phase with voltage

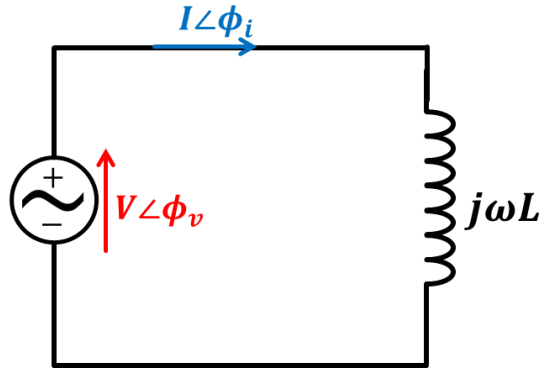
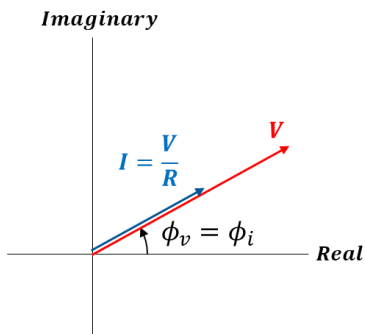


$$Z_L = j\omega L$$
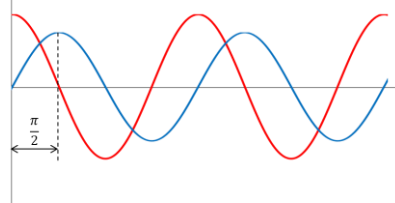
$$\frac{V}{\omega L} \angle (\phi_v - 90^\circ) = I \angle \phi_i$$




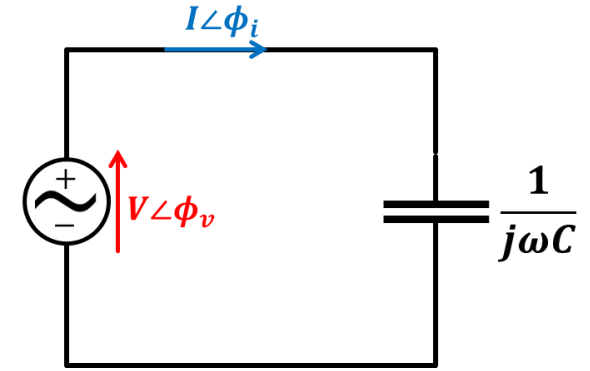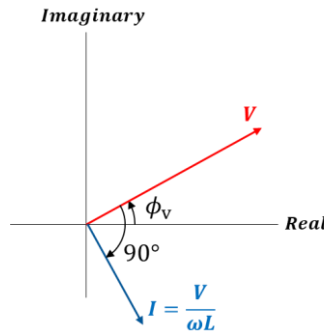current LAGS voltage by 90° or $\frac{\pi}{2}$ rad




$$Z_C = \frac{1}{j\omega C}$$
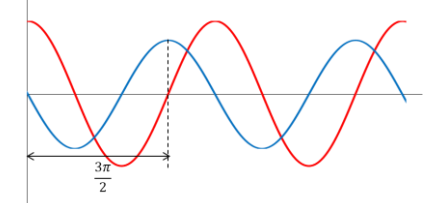
$$V\omega C \angle (\phi_v + 90^\circ) = I \angle \phi_i$$



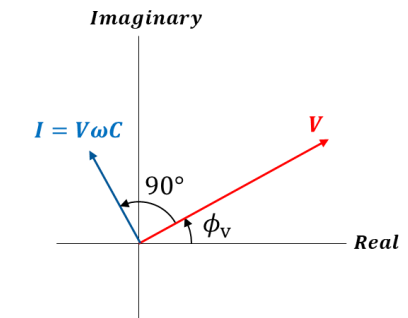current LEADS voltage by 90° or $\frac{\pi}{2}$ rad





General Rule to Solve Circuits

Step 1 – Convert voltage and current to phasor form

Step 2 – Convert R , L , C to impedance (Z_R , Z_L , Z_C)

Step 3 – Apply circuit simplification (series/parallel) depending on what is required to be solved

Step 3A – You may need to use the “loop current” & “branch current” method depending on the problem – however, most likely you can do without if you smartly apply the series/parallel rules of circuit simplification

Step 4 – Apply KVL to the required loop(s)


Step 5 – Apply Ohm’s Law

Step 6 – Solve the linear system of equations – you can solve for n unknowns with n equations

The Real Circuit (Resistive + Reactive)

Series

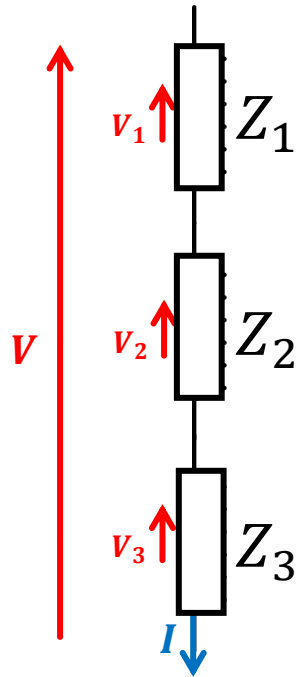
When two (or more) elements are connected together head-to-toe



$$Z = \sum Z_i$$

Parallel

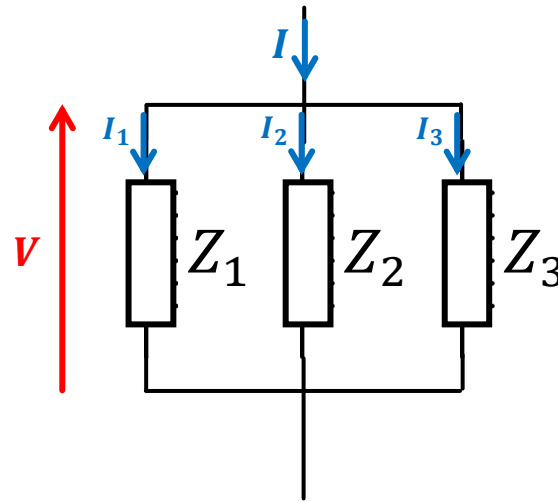
When two (or more) elements are connected head-to-head and toe-to-toe



$$\frac{1}{Z} = \sum \frac{1}{Z_i}$$


Series-Parallel

Combination of the both

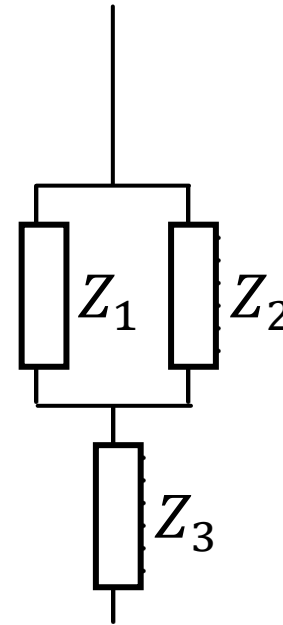

Break the circuit up into series and parallel and solve individually

Potential (& Current) Divider Rule

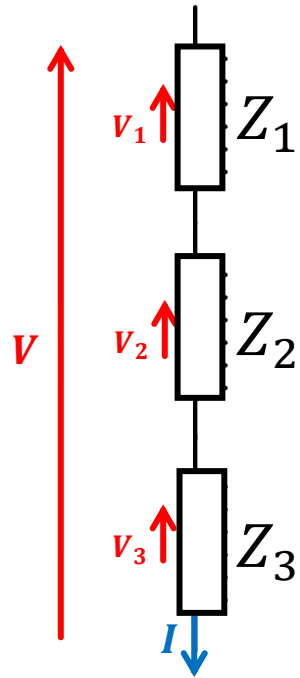

$$V_1 = \frac{Z_1}{Z_1 + Z_2 + Z_3} V$$

$$V = V_1 + V_2 + V_3$$

$$V = IZ_1 + IZ_2 + IZ_3$$


$$V = I(Z_1 + Z_2 + Z_3)$$

$$V_1 = IZ_1$$

$$I = \frac{V_1}{Z_1}$$

$$V = \frac{V_1}{Z_1} (Z_1 + Z_2 + Z_3)$$

$$V_1 = \frac{Z_1}{Z_1 + Z_2 + Z_3} V$$

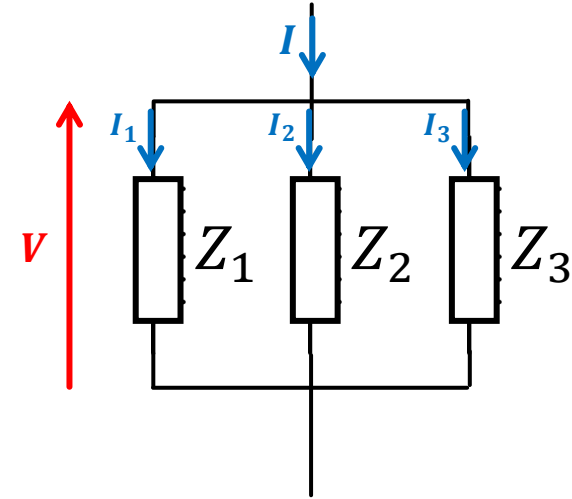


$$I_1 = \frac{\frac{1}{Z_1}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} I$$


$$I_1 = \frac{Y_1}{Y_1 + Y_2 + Y_3} I$$

Admittance (symbol Y unit mho or \bar{U}) is the reciprocal of Impedance

Example of Real Circuit

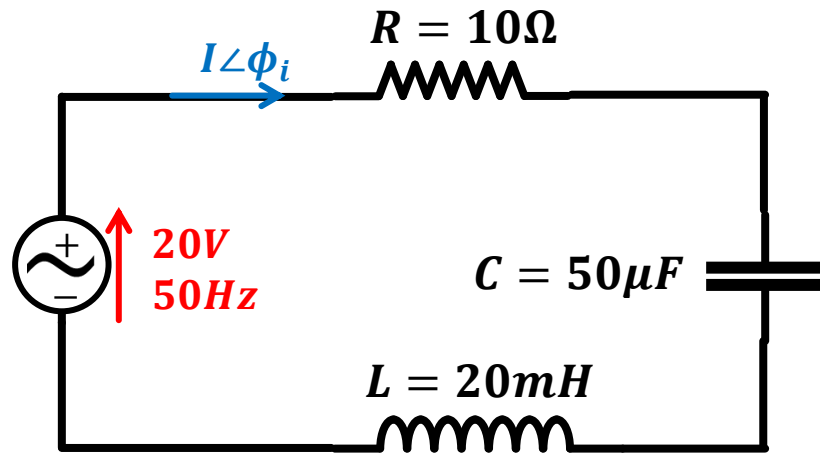

Imaginary

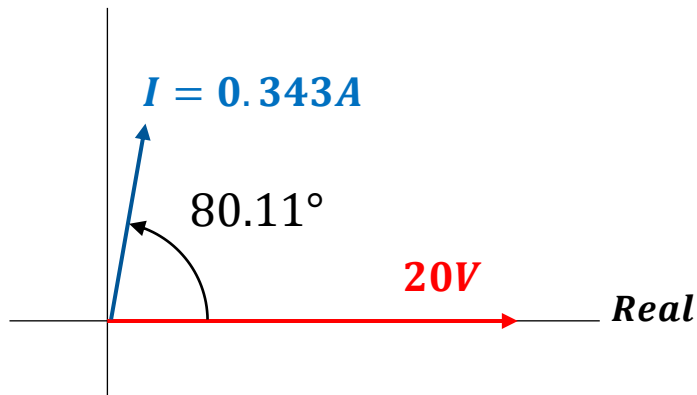

$$Z_R = 10\Omega$$

$$Z_L = j\omega L = j2\pi fL = j2 \times 3.14 \times 50 \times 20 \times 10^{-3} = j6.28\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2\pi fC} = \frac{-j}{2 \times 3.14 \times 50 \times 50 \times 10^{-6}} = -j63.66\Omega$$

The **three elements** are clearly in **series**

$$Z = Z_R + Z_L + Z_C = 10 + j(6.28 - 63.69) = 10 - j57.38$$

Applying **Ohm's Law**, we need to divide V by Z, remember, for division, we need complex numbers in **polar form**

$$|Z| = \sqrt{10^2 + 57.41^2} = \sqrt{3395.91} = 58.24$$

$$\angle Z = \tan^{-1} \frac{-57.41}{10} = -80.11^\circ$$

Applying **Ohm's Law**

$$I = \frac{V}{Z} = \frac{20\angle 0^\circ}{58.24\angle -80.11^\circ} = 0.343\angle 80.11^\circ$$

When no info on phase offset for voltage provided, no harm in setting it to 0°, makes calculations easier!



- Revision of circuits
 - **Sinusoidal** waveform – phase **angle v time?**
 - **Phasors**
 - Series/Parallel **clarification**
 - **Impedance**
 - **General Rule to solve circuits**
 - **Potential Divider Rule**
- Power in AC circuits
 - **Active v Reactive v Apparent Power**
 - **Power Factor**
 - **Resonance**

Root Mean Square (RMS)


- In mathematics, the **root-mean-square** (or **RMS**) of a set of numbers x_i is defined as the square root of the arithmetic mean of the squares of the set

$$\underline{x} = \sqrt{\frac{x_1^2 + x_2^2 + x_3^2 + \dots + x_n^2}{n}} = \sqrt{\frac{\sum x_i^2}{n}}$$

- When dealing with AC applications, the amplitude of voltage or current is seldom used (we will see shortly why – power)
- Hence, AC ammeters/voltmeters are invariably calibrated for RMS value – not peak/amplitude
- For all **sinusoidal waves**, the RMS value is $\frac{1}{\sqrt{2}} = 0.707$ times the amplitude
- It is much more convenient to make the **length of phasors** represent **RMS** instead of amplitude
- Going forward, we will deal with **only RMS values** when studying AC

$$\text{RMS value of } V = V_{rms} = \frac{|V|}{\sqrt{2}} = 0.707V$$

Power in Resistive Circuit

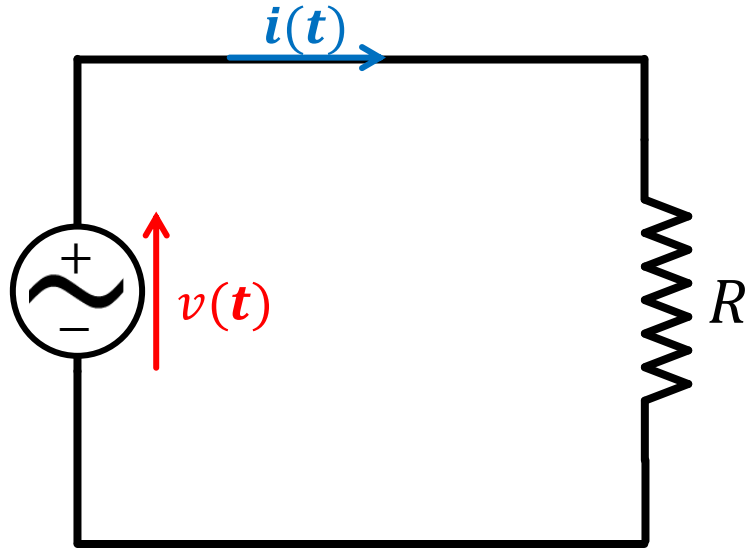

$$v(t) = V \cos \omega t$$


$$i(t) = I \cos \omega t$$

Instantaneous power

$$p(t) = v(t) \times i(t)$$

$$p(t) = V \cos \omega t \times I \cos \omega t$$
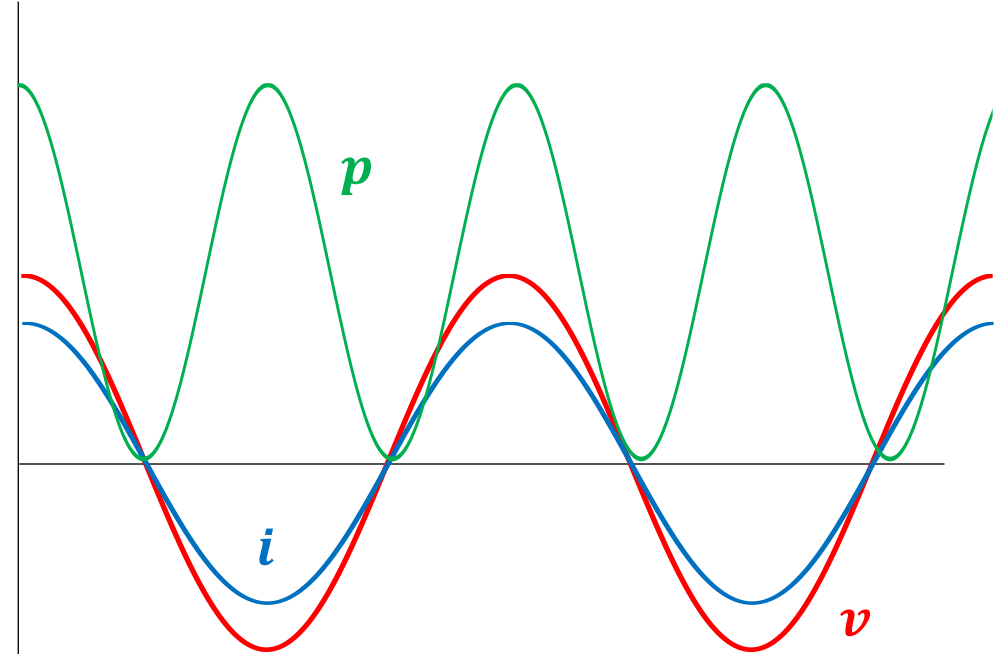
$$p(t) = \frac{VI}{2} (1 + \cos 2\omega t) = \frac{I^2 R}{2} (1 + \cos 2\omega t) = \frac{V^2}{2R} (1 + \cos 2\omega t)$$



Average power – integrate over full cycle

$$P_{avg} = \int \frac{VI}{2} (1 + \cos 2\omega t)$$

$$P_{avg} = \frac{VI}{2} + 0$$

$$P_{avg} = \frac{V_m I_m}{\sqrt{2} \sqrt{2}} = V_{rms} I_{rms}$$



Proof (don't learn)

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T p(t) dt \\ &= \frac{1}{T} \int_0^T v(t)i(t) dt \\ &= \frac{1}{T} \int_0^T V \cos(\omega t)I \cos(\omega t) dt \\ &= \frac{1}{T} \int_0^T \frac{VI}{2} \{1 + \cos(2\omega t)\} dt \\ &= \frac{1}{T} \int_0^T \frac{VI}{2} dt + \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \{\cos(2\omega t)\} dt \\ &= \frac{VI}{2} - \frac{1}{\omega T} \int_0^{2\pi} \frac{V_m I_m}{2} \{\cos(2\omega t)\} d\omega t \\ &= \frac{VI}{2} = V_{rms} I_{rms} \end{aligned}$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$

Remember that power in DC circuits


$$P = V_{dc} \times I_{dc}$$

Equivalently, the AC counterparts for

V_{dc} is V_{rms} and I_{dc} is I_{rms}

**That is why we always use the RMS
value of voltage and current**

Power in Inductive Circuit

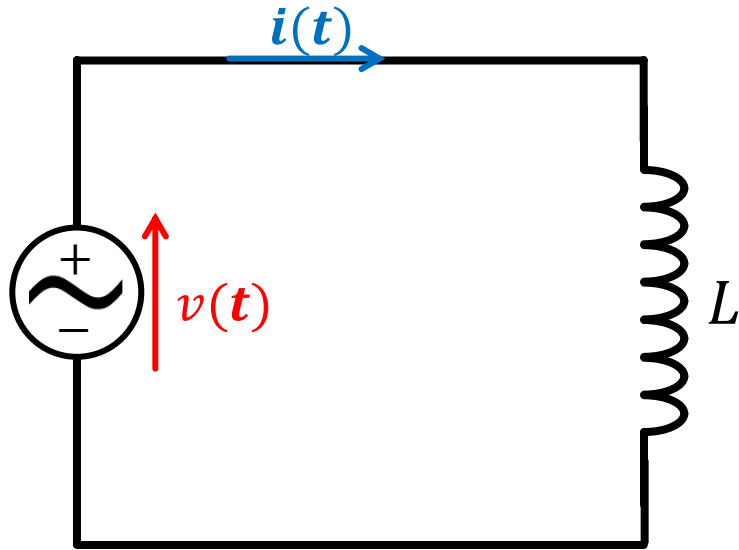

$$v(t) = V \cos \omega t$$

$$i(t) = I \sin \omega t$$


Do you know why?

Instantaneous power

$$p(t) = v(t) \times i(t)$$

$$p(t) = V \cos \omega t \times I \sin \omega t$$
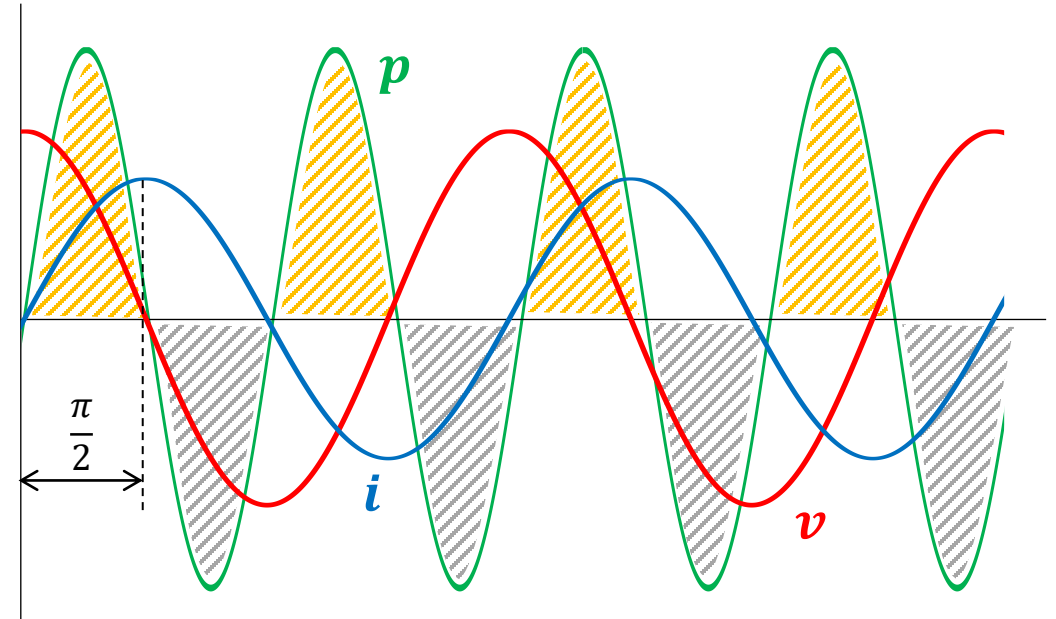
$$p(t) = \frac{VI}{2} \sin 2\omega t = \frac{\omega LI^2}{2} \sin 2\omega t = \frac{V^2}{2\omega L} \sin 2\omega t$$




Energy absorbed from the source



Energy released to the source

Average power is ZERO!

Power in Capacitive Circuit

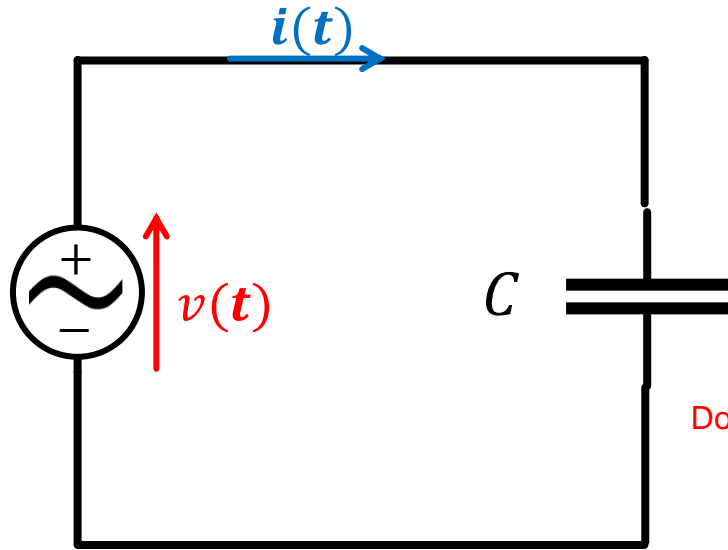

$$v(t) = V \cos \omega t$$

$$i(t) = -I \sin \omega t$$

Do you know why?


Do you know why?

Instantaneous power

$$p(t) = v(t) \times i(t)$$

$$p(t) = -V \cos \omega t \times I \sin \omega t$$
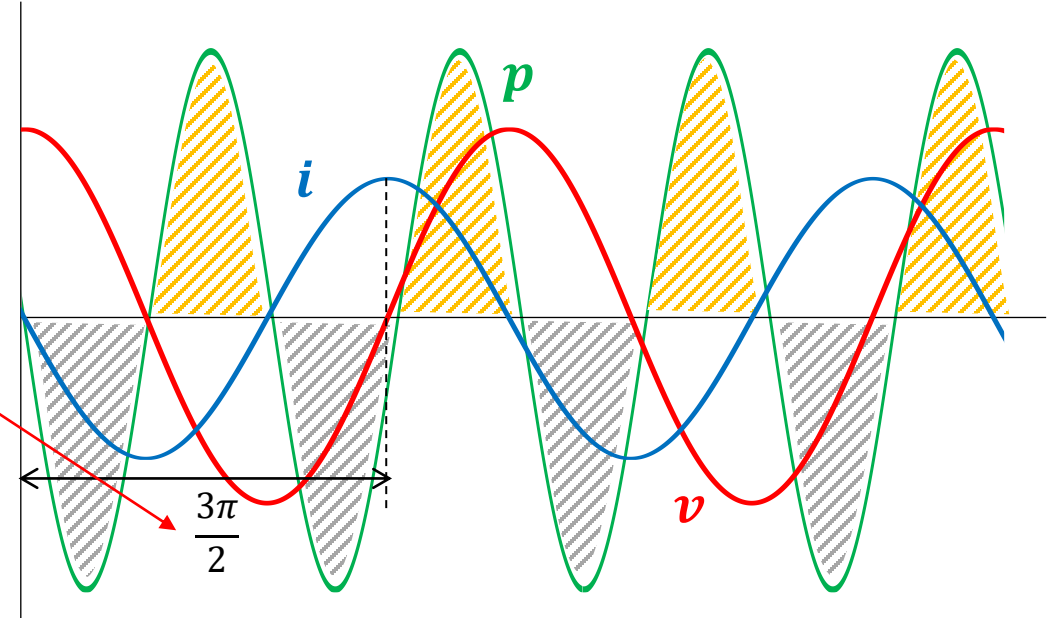
$$p(t) = \frac{-VI}{2} \sin 2\omega t = \frac{I^2}{2\omega C} \sin 2\omega t = \frac{\omega CV^2}{2} \sin 2\omega t$$




Energy absorbed from the source



Energy released to the source

Average power is ZERO!

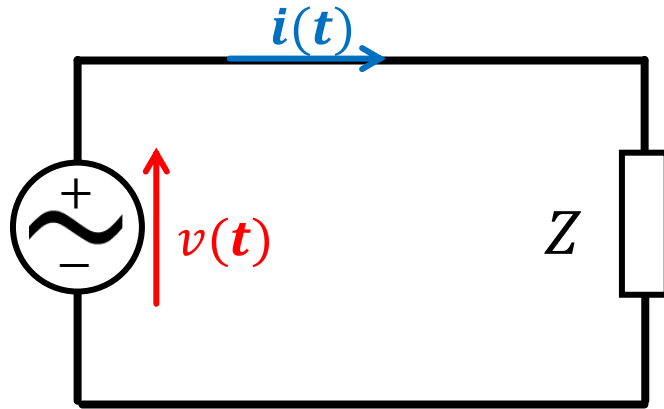Power in Real Circuit (Resistive + Reactive)



$$v(t) = V \cos \omega t$$

$$i(t) = I \cos(\omega t + \gamma)$$

Instantaneous power

$$p(t) = v(t) \times i(t)$$


$$p(t) = V \cos \omega t \times I \cos(\omega t + \gamma)$$

$$p(t) = \frac{VI}{2} \{ \cos(\omega t - \omega t - \gamma) + \cos(\omega t + \omega t + \gamma) \}$$

$$p(t) = V_{rms} I_{rms} \cos \gamma + V_{rms} I_{rms} \cos(2\omega t + \gamma)$$

Average Power

This term averages to zero over a cycle

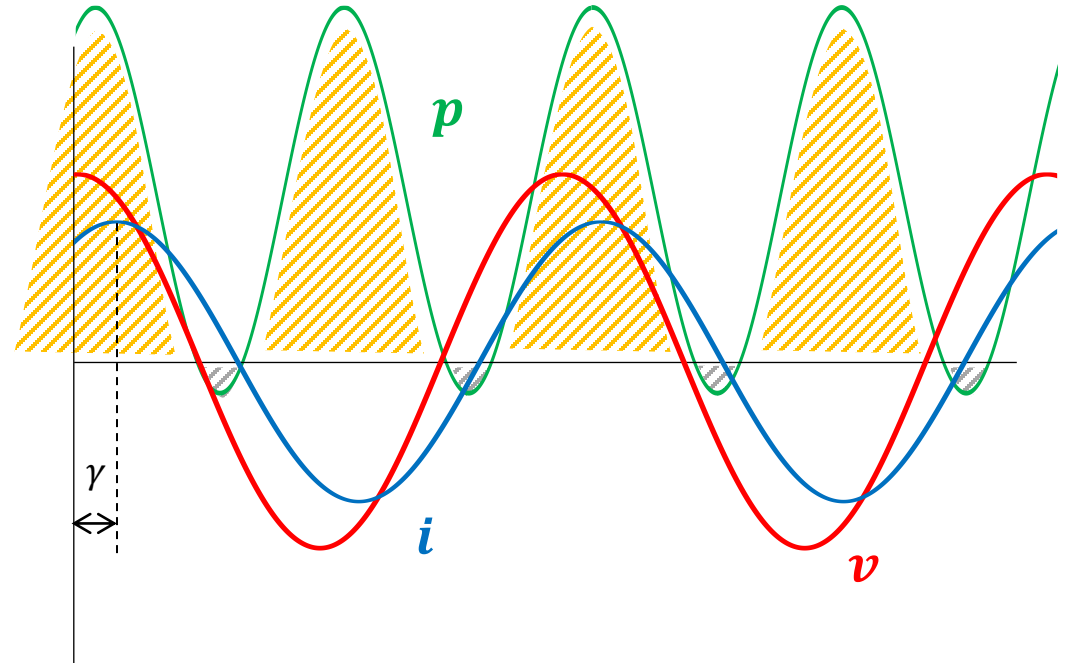


Energy absorbed from the source



Energy released to the source

Average power is $V_{rms} I_{rms} \cos \gamma$ **Power Factor**

Power Factor

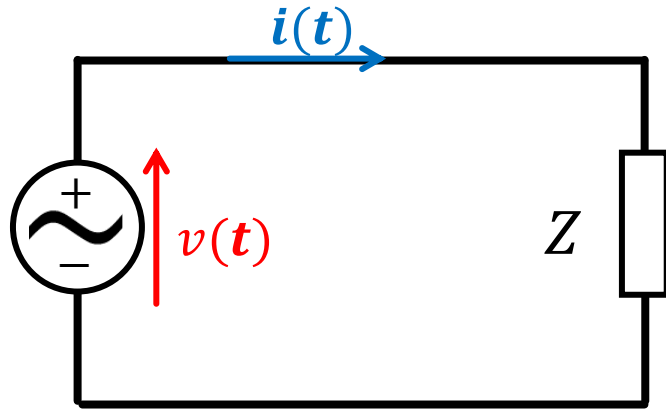


$$P_{avg} = V_{rms} I_{rms} \cos \gamma$$

$$\cos \gamma = \text{Power Factor} = PF$$

γ is the **phase deviation** between voltage & current

PF tells us **what fraction of the current does useful work**

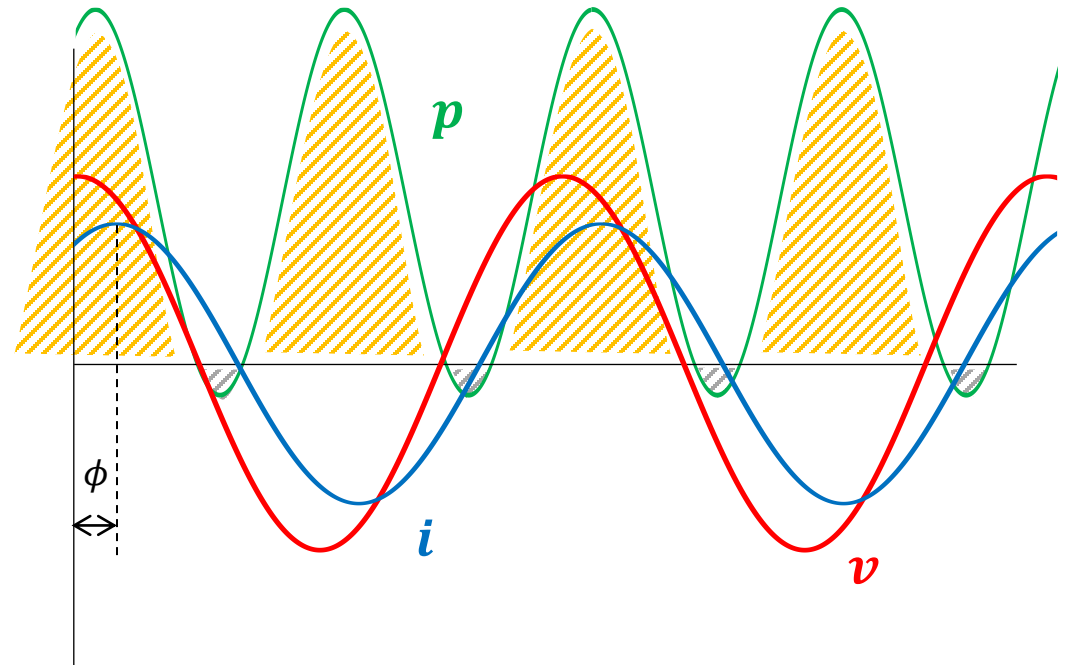Is it phase **advance/delay**? *Does it matter?*



Energy absorbed from the source



Energy released to the source



Power Factor

Purely Resistive Load R	$\gamma = 0^\circ$ $\cos \gamma = 1$	All power consumed
Purely Reactive Load L or C	$\gamma = \pm 90^\circ$ $\cos \gamma = 0$	No real power consumed
Real Inductive Load RL or RLC	$-90^\circ < \gamma < 0^\circ$ $0 < \cos \gamma < 1$	Part of apparent power consumed
Real Capacitive Load RC or RLC	$0^\circ < \gamma < 90^\circ$ $0 < \cos \gamma < 1$	

Apparent Power (symbol **S** unit **VA**)

$$S = V_{rms}I_{rms}$$

- As the name suggests, this is the amount of power that appears to be flowing from source to load
- This is not the case as over a cycle, some (or all) of this power gets returned back to source
- As the power still flows (even if it is simply thrown back-forth between source and load), losses still occur
- A good circuit should have PF very close to unity
- However, AC equipment are rated for Apparent Power as it handles both used and unused power

Active Power (symbol **P** unit **W**)

$$P = V_{rms}I_{rms} \cos \gamma = V_{rms}I_{rms}PF = S \times PF$$



- This is the real power transferred to the load


Reactive Power (symbol **Q** unit **VAR**)

$$P = V_{rms}I_{rms} \sin \gamma = V_{rms}I_{rms} \sin \gamma = S \sin \gamma$$


- This is the purely unused power exchanged between the source and load

Active v Reactive v Apparent Power

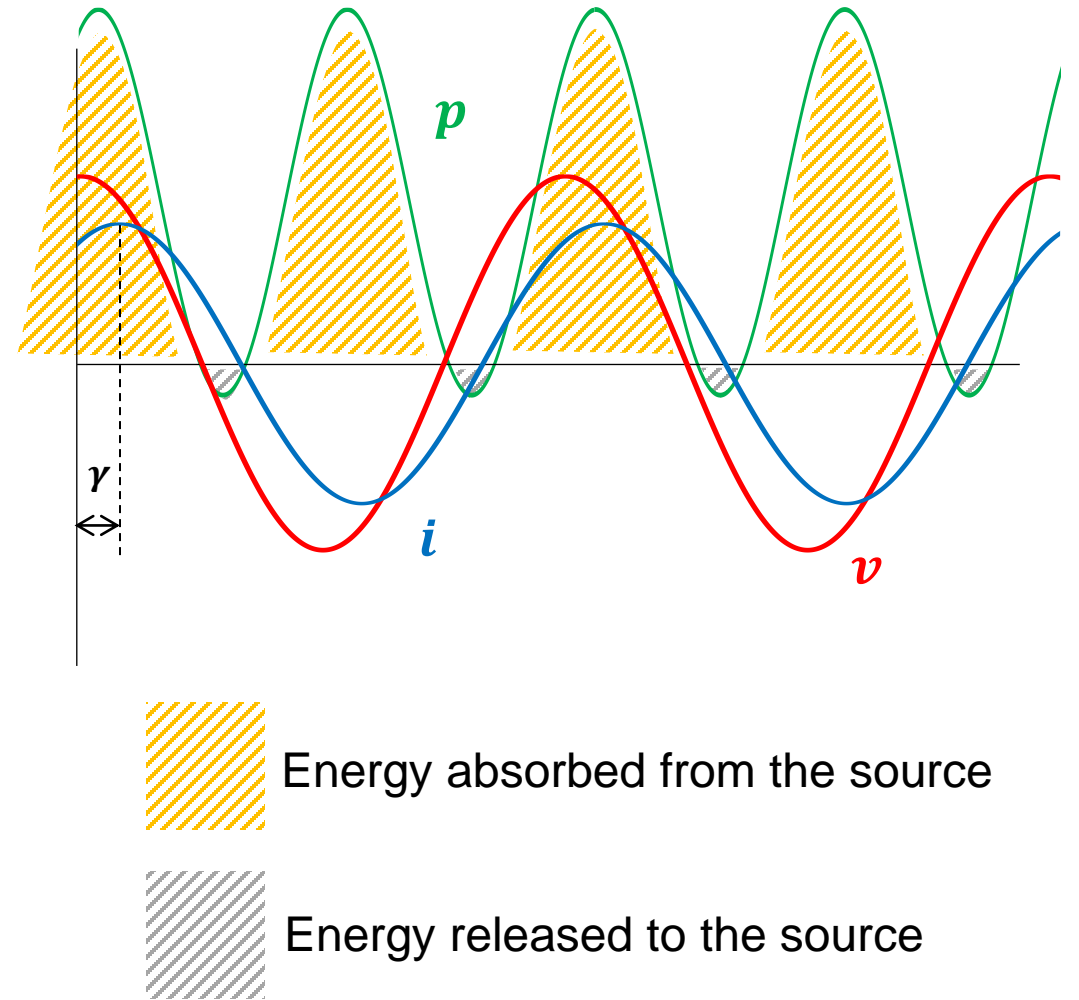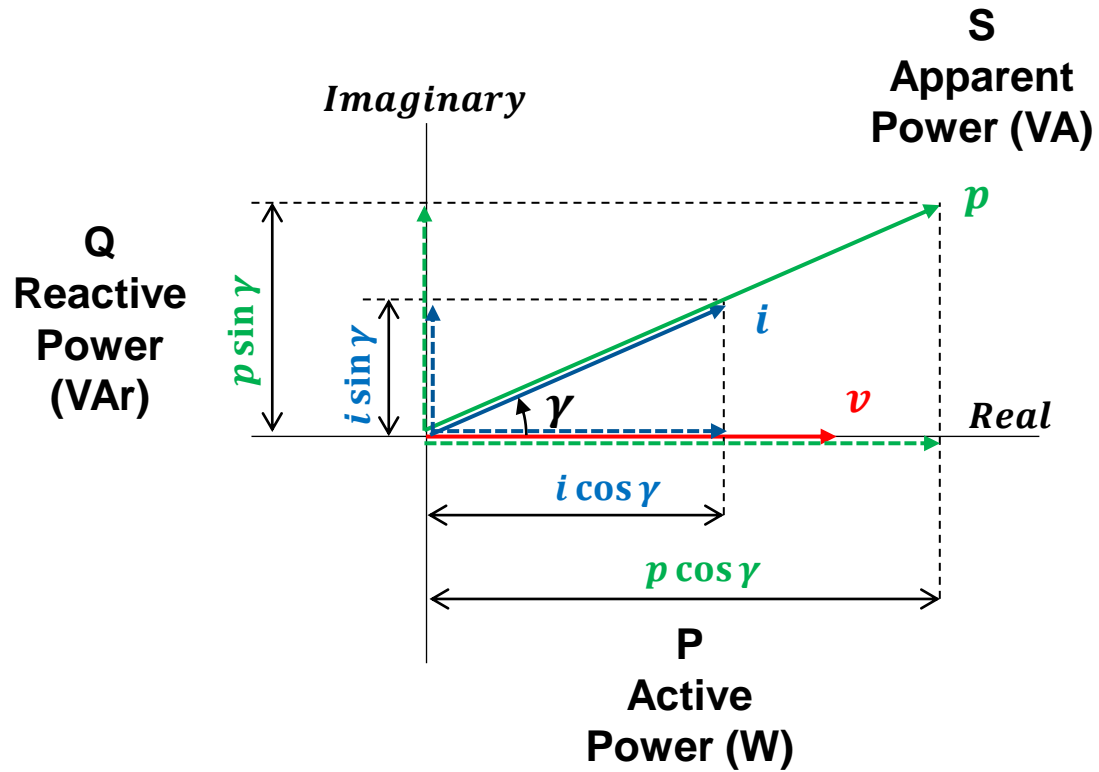

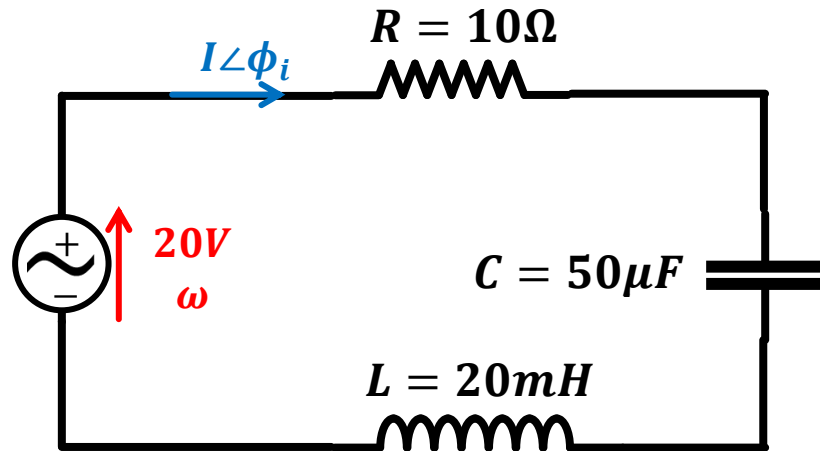

- We have seen that inductor and capacitor **individually contribute** to delaying and advancing (respectively) the current waveform w/r/t the voltage
 - When the inductance and capacitance value are equal (and opposite, inherently) they **nullify** each other – **Resonance**
 - $Z_L = j\omega L$ **increases** with **increasing frequency**
 - $Z_C = \frac{1}{j\omega C}$ **decreases** with **increasing frequency**
- We did this example earlier with frequency (50 Hz), we saw that the **overall circuit was capacitive** (i.e., capacitance was overpowering inductance and resultant current was 80° leading)
 - What happens if we **increase the frequency**?
 - There will come a frequency when **inductance just matches capacitance** – this is **resonance**
 - When this happens, you will be left with a **purely resistive circuit**, i.e., **overall impedance drops!**
 - As you increase the frequency (from 50 Hz), you would see current rising gradually, then sharply at resonance, then again start falling

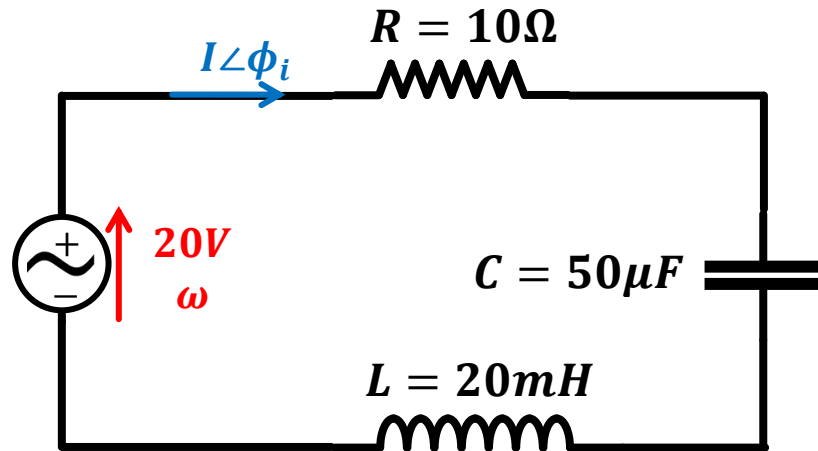

$$Z_L = Z_C$$

$$j\omega L = \frac{1}{j\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{20 \times 10^{-3} \times 50 \times 10^{-6}}} = \frac{1}{\sqrt{10^{-6}}}$$

$$\omega_{res} = 1000 \frac{rad}{s}$$

Lets find out the current at resonant frequency and plot the phasor diagram

$$Z_L = j\omega_{res}L = j \times 1000 \times 20 \times 10^{-3} = j20\Omega$$

$$Z_C = \frac{1}{j\omega_{res}C} = \frac{-j}{1000 \times 50 \times 10^{-6}} = -j20\Omega$$

The three elements are clearly in series

$$Z = Z_R + Z_L + Z_C = 10 + j(20 - 20) = 10\Omega$$

Applying Ohm's Law

$$I = \frac{V}{Z} = \frac{20 \angle 0^\circ}{10 \angle 0^\circ} = 2 \angle 0^\circ A$$

2 A is significantly higher than 343 mA that we calculated at 50 Hz frequency

This is because the at resonance, inductive and capacitive impedances nullify each other

Example 1

A coil is connected to a 50 V AC supply at 400 Hz. If the current supplied to the coil is 200 mA and the coil has a resistance of 60 Ω , determine the value of inductance.

Like most practical forms of inductor, the coil in this example has both resistance *and* reactance. We can find the impedance of the coil from:

$$|Z| = \frac{V}{I} = \frac{50}{0.2} = 250\Omega$$

Since

$$|Z| = \sqrt{R^2 + X^2}$$

$$X = \sqrt{|Z|^2 - R^2}$$

$$X = \sqrt{250^2 - 60^2} = 243\Omega$$

Now since $XL = 2\pi fL$,

$$L = \frac{X}{2\pi f} = \frac{243}{100\pi} = 0.097H$$

Example 2

An AC load has a power factor of 0.8. Determine the active power dissipated in the load if it consumes a current of 2 A at 110 V.

Since active power

$$P = PF \times V_{rms} \times I_{rms}$$

$$P = 0.8 \times 110 \times 2$$

$$P = 176 \text{ W}$$

Example 3

A coil having an inductance of 150 mH and resistance of 250Ω is connected to a 115 V 400 Hz AC supply. Determine:

- (a) the power factor of the coil
- (b) the current I_{rms} taken from the supply
- (c) the power dissipated as heat in the coil.

(a) First we must find the reactance of the inductor, X_L , and the impedance, Z , of the coil at 400 Hz .

$$X_L = 2\pi \times 400 \times 0.015 = 376 \Omega$$

Thus

$$Z = R + jX_L = 250 + j376 \Omega$$

The power factor is

$$\cos\gamma = \frac{R}{|Z|}$$

Since

$$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{250^2 + 376^2} = 452 \Omega$$

Thus
$$\cos\gamma = \frac{R}{|Z|} = \frac{250}{452} = \mathbf{0.553}$$

(b)

$$I_{rms} = \frac{V_{rms}}{|Z|} = \frac{115}{452} = \mathbf{0.254 \text{ A}}$$

(c) The power dissipated as heat is the active power

$$P = V_{rms}I_{rms} \cos\gamma = 0.254 \times 115 \times 0.553$$

$$\mathbf{P = 16.15 \text{ W}}$$



- Revision of circuits
 - **Sinusoidal** waveform – phase **angle** v **time**?
 - **Phasors**
 - Series/Parallel **clarification**
 - **Impedance**
 - **General Rule to solve circuits**
 - **Potential Divider Rule**
- Power in AC circuits
 - **Active** v **Reactive** v **Apparent Power**
 - **Power Factor**
 - **Resonance**