



University of
Nottingham

UK | CHINA | MALAYSIA

LECTURE 4

Digital Electronics 1

Electromechanical Devices

MMME2051

Module Convenor – Surojit Sen




- Introduction to **Information**
 - **Exchange of information** – essence of any machine!
 - **Digital v Analog** signal
 - **Accuracy v Precision**
- **Electronics**
 - Revisit Engineering
 - Information in Electronics and Software
 - Common terminologies (**PCB, IC**)
- Logic **Gates**

Information

Generation, sensing, communication, transformation, storage

- When you press the light switch in your room, a mechanical signal (pressing/flicking action) gets converted to an electrical signal, that lights up an LED by converting the electrical energy into light and heat.
- Everything is **conversion of energy** from one form to another
- Energy can be used to:
 - Do **work** – motor
 - Communicate **information**
 - **Digital**
 - **Analog**

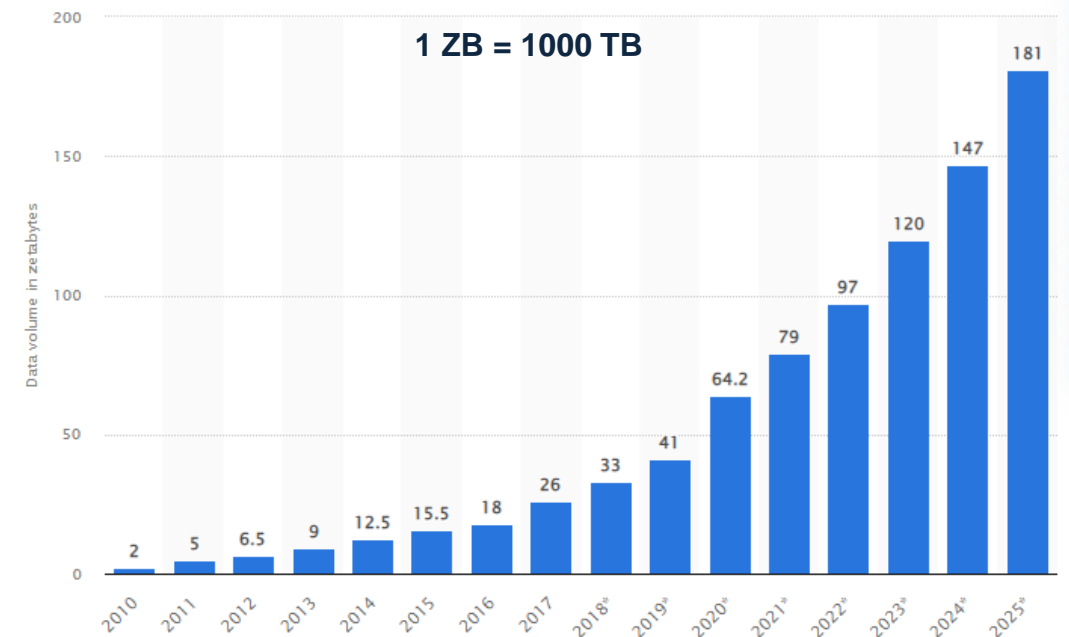Volume of data/information created, captured, copied, and consumed worldwide from 2010 to 2020, with forecasts from 2021 to 2025



Credit: <https://www.statista.com/statistics/871513/worldwide-data-created/>

Digital

You **ask** the computer/digital device:

“Is the room temperature:”

Q1 – **“15-16°C?”** A1 – **“No”**


Q2 – **“16-17°C?”** A1 – **“No”**

Q3 – **“17-18°C?”** A1 – **“No”**

Q4 – **“18-19°C?”** A1 – **“No”**

Q5 – **“19-20°C?”** A1 – **“Yes”**

Q6 – **“20-21°C?”** A1 – **“No”**

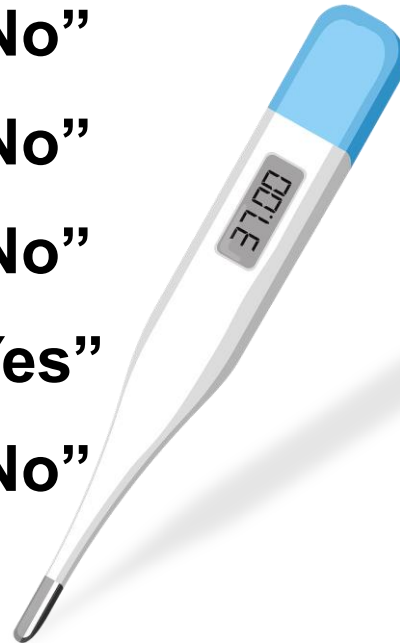

Analog


You ask a **question** to someone/something, e.g., **“what is the temperature of the room?”**

They reply, **“19.2°C”**



Digital


10 unique colours values, or levels

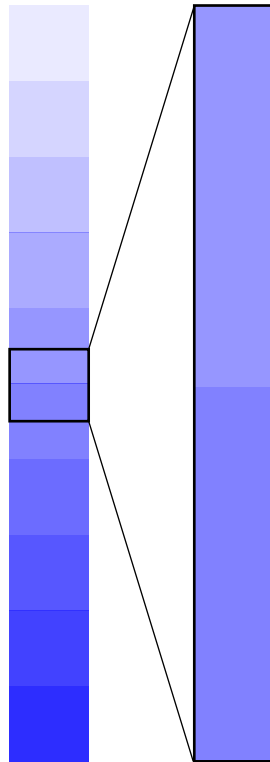

2 unique colours when zoomed in


Analog

∞ unique colours values, or levels

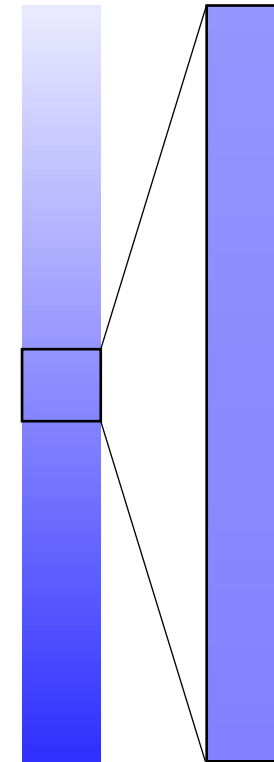

∞ unique colours when zoomed in

Digital vs Analog!

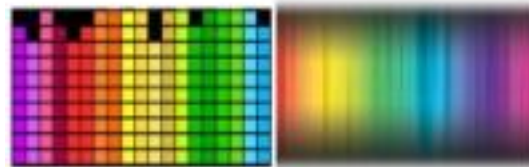

Digital

Information in form of **discrete** symbols, or **levels**

Variable can be only 1 out of a **finite number of options**

Humans interpret physical values in discrete levels

- **Alphabets**
- **Binary number**
- **Logic state**
- **Answer to the question** – “*Are you enjoying this module?*”

Analog

Information in form of **continuous** and **real-valued levels**

Variable can be only 1 out of an **infinite number of options**

The physical values exist naturally in continuous spectrum levels

- **Air pressure in this room**
- **Volume of my voice**
- **Battery voltage in your laptop**
- **Answer to the question** – “*How much are you enjoying this module?*”

Language – using letters

There are 26 alphabets in the English language – digital!

Binary

e.g.,
11100100

Octal

e.g.,
344

Numbers

Every number that we use, uses a distinct number of symbols (including the decimal point)

Decimal

e.g.,
228

Hexadecimal

e.g.,
E4

Let us look at an example of a Binary and Octal question

What is the temperature of the room?

- **Option 0** – Not 18-19°C
- **Option 1** – 18-19°C

In **Binary**, you can respond with **2 choices** only.

In **Octal**, you can respond with **8 choices**.

Similarly, in **Decimal**, you respond with **10 choices**, and in **Hexadecimal**, you respond with **16 choices**.


What is the temperature of the room?

- **Option 0** – 15-16°C
- **Option 1** – 16-17°C
- **Option 2** – 17-18°C
- **Option 3** – 18-19°C
- **Option 4** – 19-20°C
- **Option 5** – 20-21°C
- **Option 6** – 21-22°C
- **Option 7** – 22-23°C

How does this actually relate to “numbers”?

Let us look at a number in the “Decimal” number-format, the one that we have grown up with.

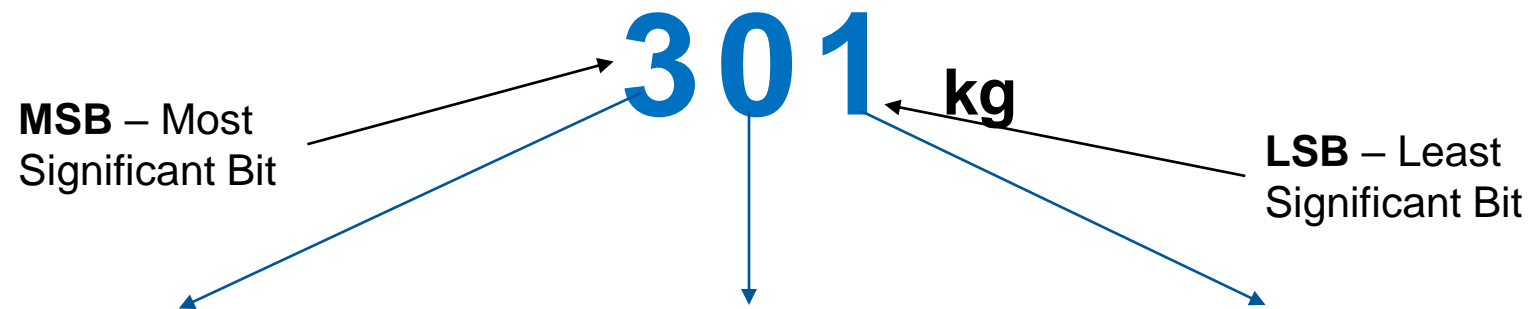Weight of the Formula Student 2021 car is



$$3 \times 10^2 = 300$$


$$0 \times 10^1 = 0$$

$$1 \times 10^0 = 1$$

How does this actually relate to “numbers”?

The same number in the Hexadecimal format will be

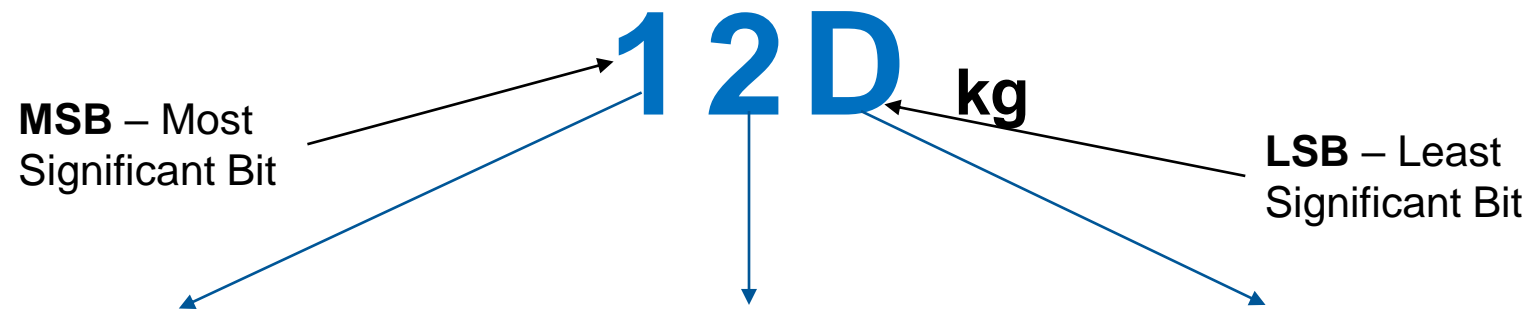Weight of the Formula Student 2021 car is



$$1 \times 16^2 = 256$$

$$2 \times 16^1 = 32$$

$$D \times 16^0 = 13$$

How does this actually relate to “numbers”?

How about in Binary?

Weight of the Formula Student 2021 car is

LSB – Least Significant Bit

MSB – Most Significant Bit

0001 0010 1101 kg

- $0 \times 2^{11} = 0$
- $0 \times 2^{10} = 0$
- $0 \times 2^9 = 0$
- $1 \times 2^8 = 256$

256

- $0 \times 2^7 = 0$
- $0 \times 2^6 = 0$
- $1 \times 2^5 = 32$
- $0 \times 2^4 = 0$

32



- $1 \times 2^3 = 8$
- $1 \times 2^2 = 4$
- $0 \times 2^1 = 0$
- $1 \times 2^0 = 1$

13

Some Important Terminologies


Accuracy is a measure of how close a “number” is to the **true value** of what it **represents**

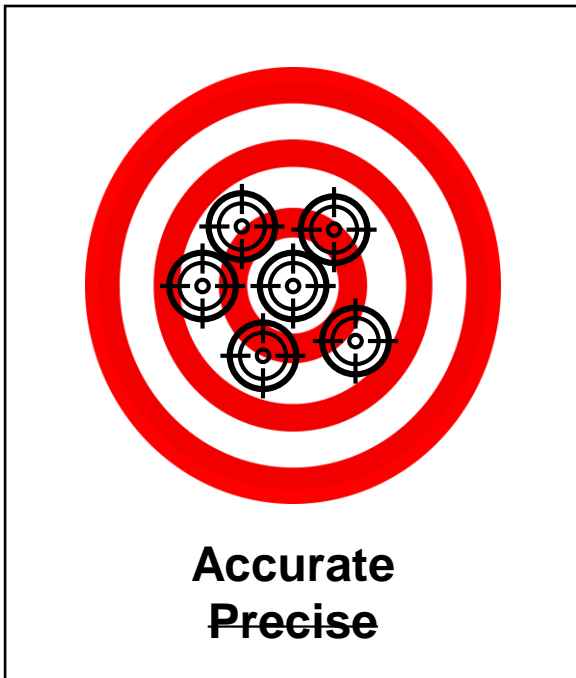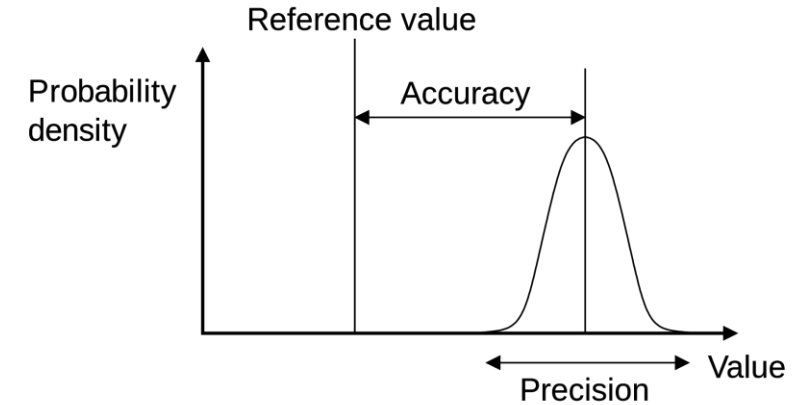Precision is a measure of how dispersed a “number” is to the central value (central value may be widely inaccurate!)






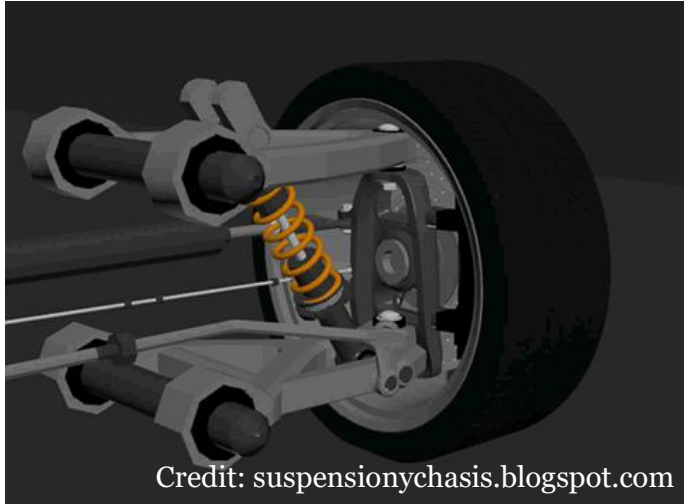- Introduction to **Information**
 - **Exchange of information** – essence of any machine!
 - **Digital v Analog** signal
 - **Accuracy v Precision**
- **Electronics**
 - Revisit Engineering
 - Information in Electronics and Software
 - Common terminologies (**PCB, IC**)
- Logic **Gates**



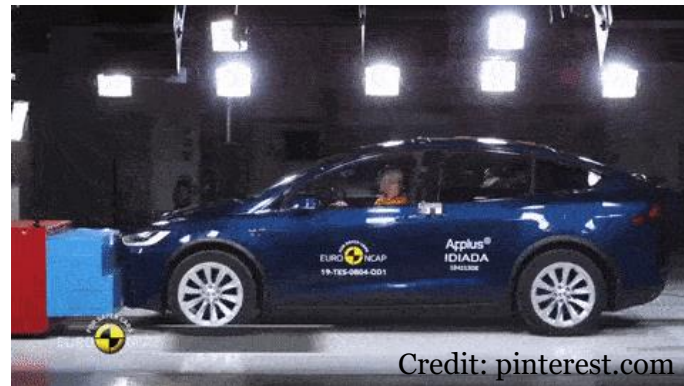Suspension & chasses
Mechanical Engineering



Vehicle Control Unit (VCU) that sends signals/commands to drive/stop the car
Electronic Engineering


Code written to program the VCU
Computer/Software Engineering



Motor that converts electrical power from battery to mechanical motion
Electromechanical Engineering



Battery that supplies power to drive the motor
Electrical Engineering

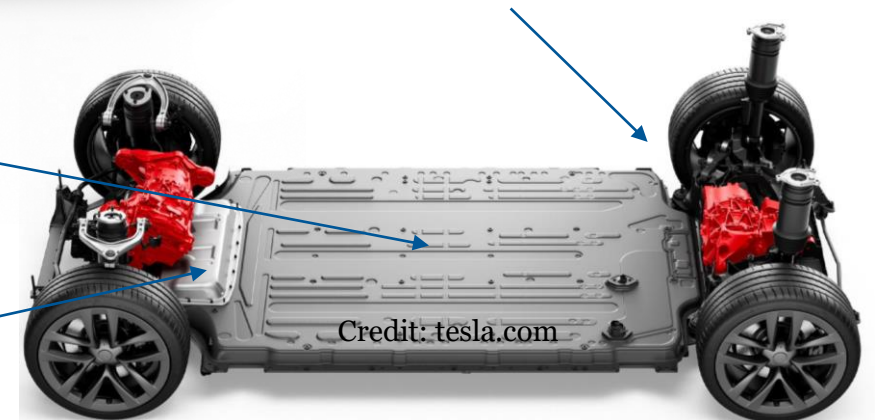Power Converter that controls the flow of electrical power between battery and motor
Power Electronics



Electronic

LESS

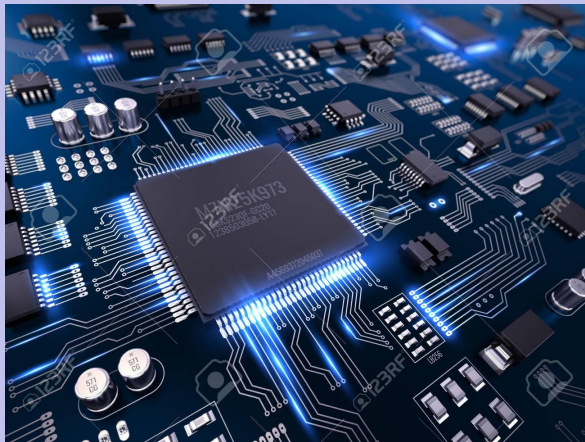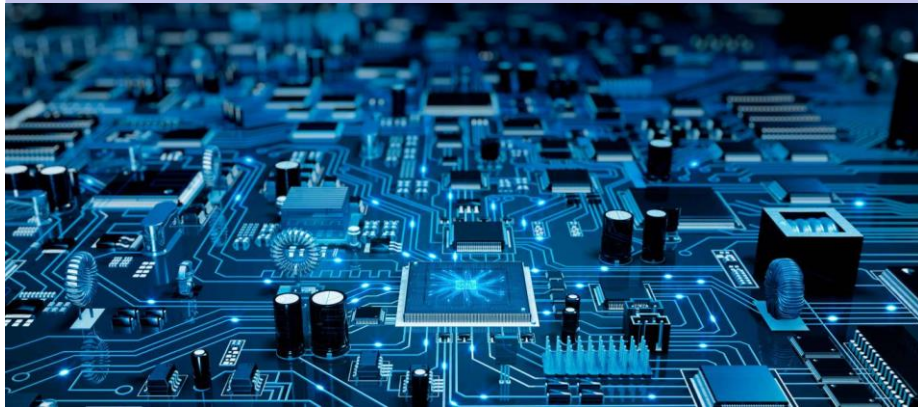

5V

50mA

Electrical

MORE



We use **binary number system** in logical circuits in electronics

This aligns with computer/software engineering – binary system used


Logic – TRUE/FALSE

We said that **301** (weight of the FS21 in kg) is represented in binary as

0001 0010 1101

How is this actually done in reality?

Two voltage levels – **High & Low**

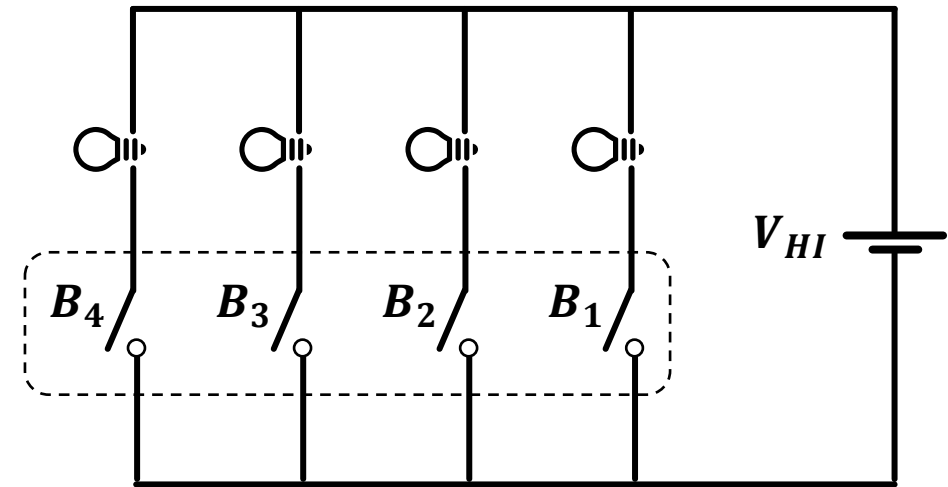

0 0 0 0 = 0000
↑ ↑
MSB – Most Significant Bit **LSB** – Least Significant Bit

We use **binary number system** in logical circuits in electronics

This aligns with computer/software engineering – binary system used


Logic – TRUE/FALSE

We said that **301** (weight of the FS21 in kg) is represented in binary as

0 0 0 1 0 0 1 0 1 1 0 1

How is this actually done in reality?

Two voltage levels – **High & Low**

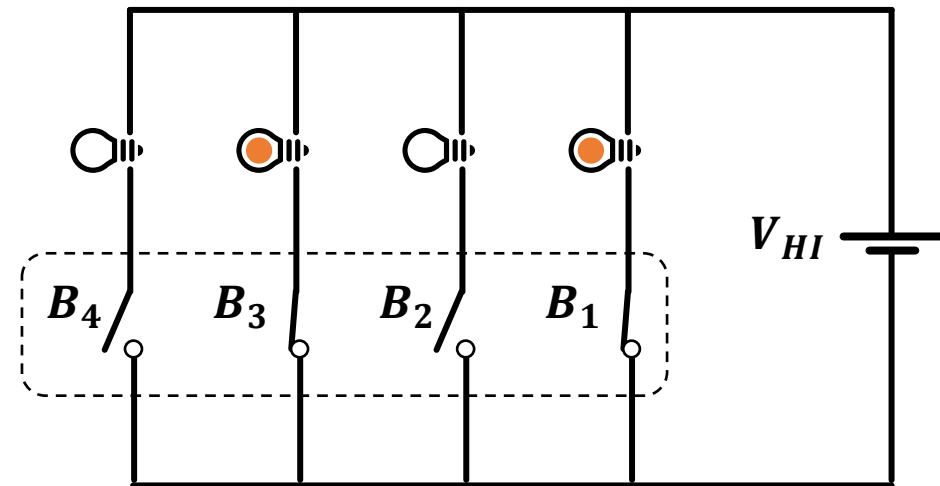

0 **1** **0** **1** = **0101**
↑ ↑
MSB – Most Significant Bit **LSB** – Least Significant Bit

We use **binary number system** in logical circuits in electronics

This aligns with computer/software engineering – binary system used


Logic – TRUE/FALSE

We said that **301** (weight of the FS21 in kg) is represented in binary as

0 0 0 1 0 0 1 0 1 1 0 1

How is this actually done in reality?

Two voltage levels – **High & Low**

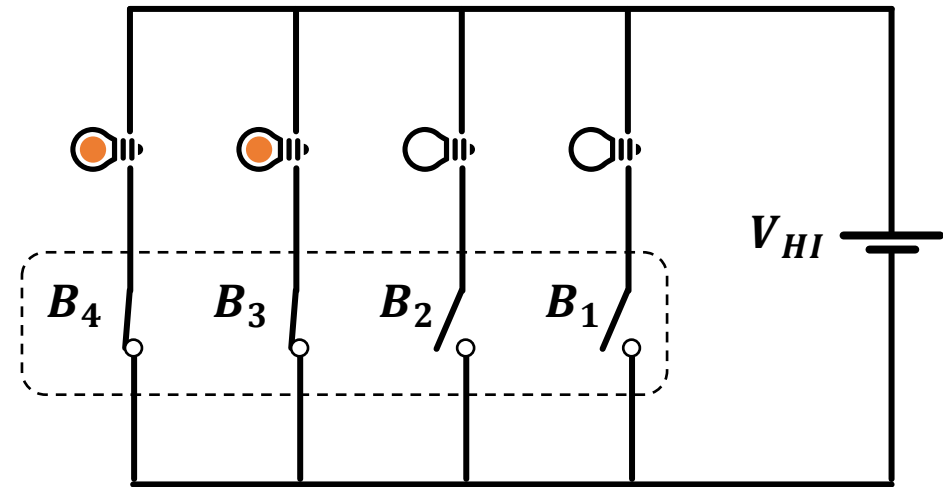

1 **1** **0** **0** = **1100**
 ↑ ↑
MSB – Most Significant Bit **LSB** – Least Significant Bit

How to Add/Subtract Binary Numbers?

Just the same way you do for decimal numbers!

Decimal

$$\begin{array}{r}
 1 \\
 124 \\
 +229 \\
 \hline
 \mathbf{353}
 \end{array}$$

$$\begin{array}{r}
 124 \\
 - 47 \\
 \hline
 \mathbf{77}
 \end{array}$$

Binary

$$\begin{array}{r}
 1\ 1\ 1\ 1\ 1 \\
 0111\ 1100 \\
 +1110\ 0101 \\
 \hline
 \mathbf{1\ 0110\ 0001}
 \end{array}$$

$$\begin{array}{r}
 0111\ 1100 \\
 - 0010\ 1111 \\
 \hline
 \mathbf{0100\ 1101}
 \end{array}$$

We won't do **multiplication** and **division** operations on binary numbers

If you did, you would use a XOR gate – we will study that soon

We shall study **Binary Algebra** later

How to Add/Subtract Binary Numbers?

Decimal	B ₄	B ₂	B ₂	B ₁	Binary
0	0	0	0	0	0000
1	0	0	0	1	0001
2	0	0	1	0	0010
3	0	0	1	1	0011
4	0	1	0	0	0100
5	0	1	0	1	0101
6	0	1	1	0	0110
7	0	1	1	1	0111
8	1	0	0	0	1000
9	1	0	0	1	1001
10	1	0	1	0	1010
11	1	0	1	1	1011
12	1	1	0	0	1100
13	1	1	0	1	1101
14	1	1	1	0	1110
15	1	1	1	1	1111

We would call this a 4-bit binary number – it is made of 4 bits

Maximum number we can count up to for a binary number is given by $2^n - 1$


1 byte = 8 bits

Modern computers use **32-bit** or **64-bit** numbers in its operating system


Remember the numeric data types you learnt in MATLAB last year?

- **Single** – 4 bytes
- **Double** – 8 bytes
- **Int8** – 1 byte

Some Important Terminologies

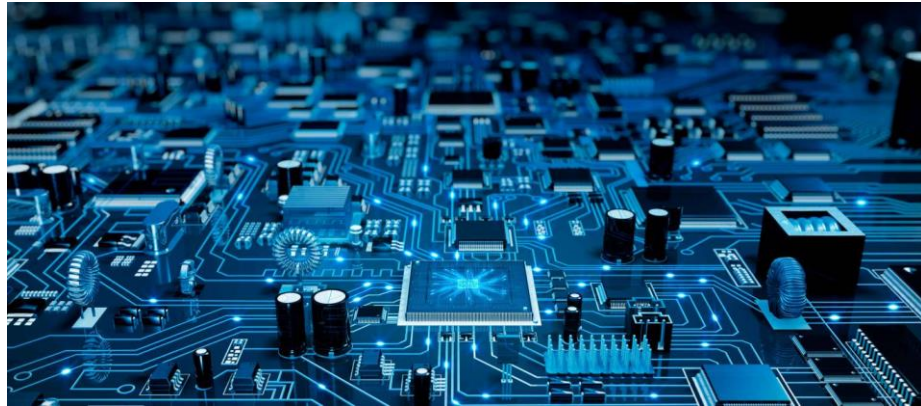


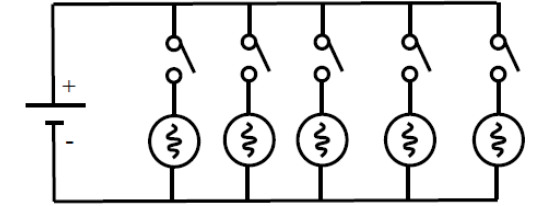Step 1 – Design the electrical/electronic circuit you want




Printed Circuit Board

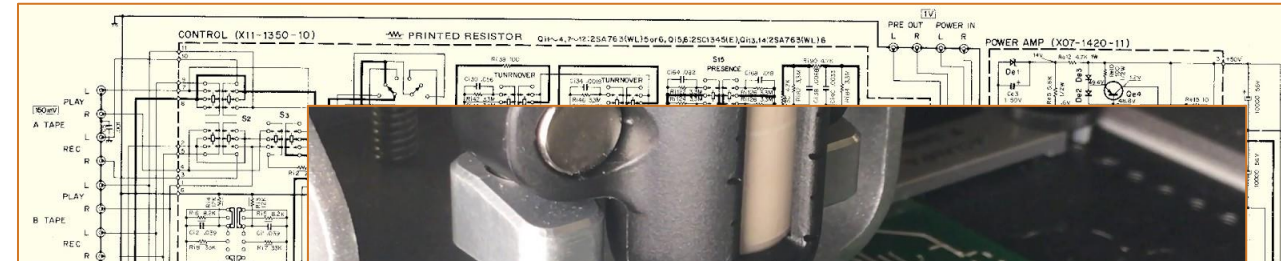Step 2 – “Print” the circuit on a fibreglass board



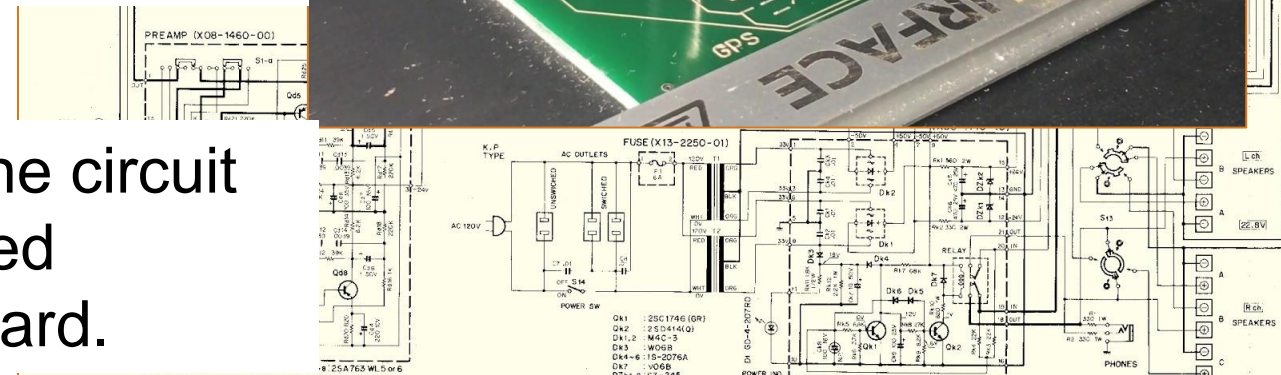Step 3 – “Complete” the circuit by “placing” the required components on the board.






Yamaha YSM12 PCB Pick and Place Machine



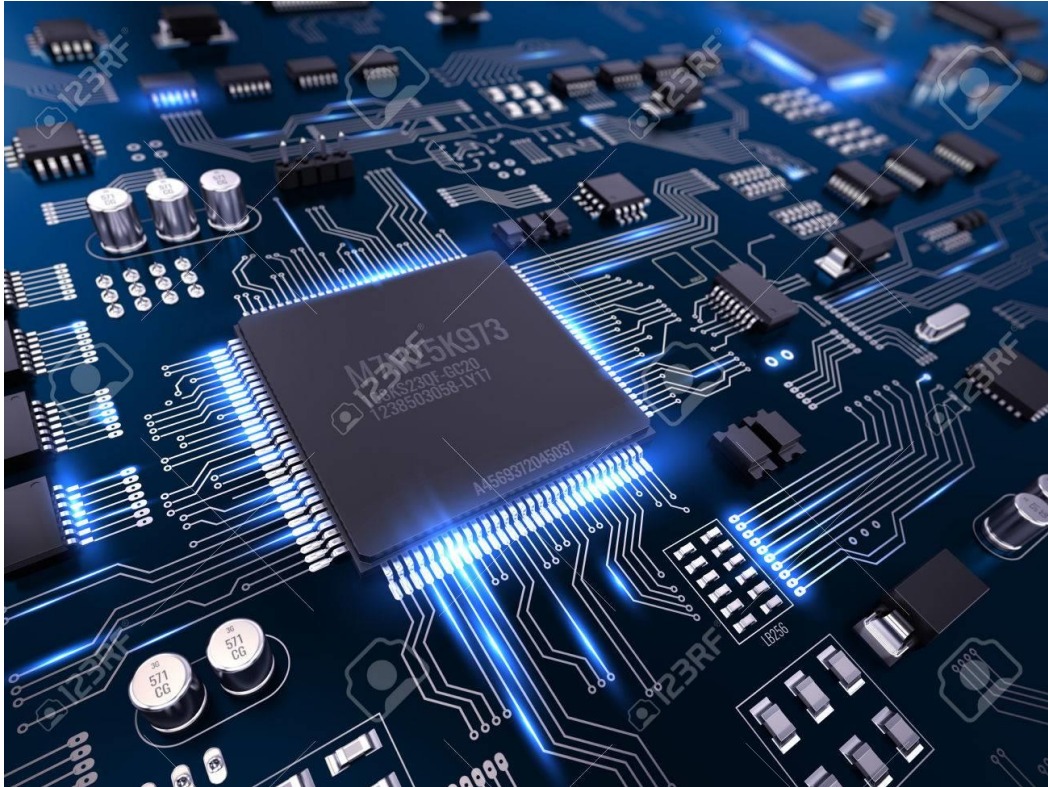
<https://www.youtube.com/watch?v=li7L6jsVdaE>



It is essentially a PCB within a small monolithic plastic package!

[555 timer teardown \(link\)](#)

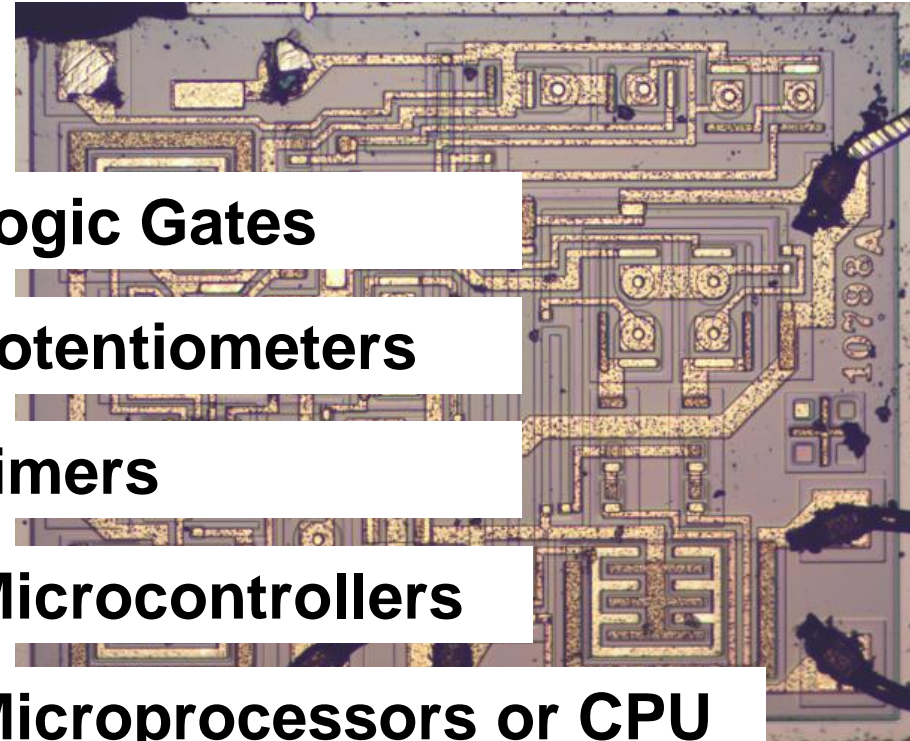

- Logic Gates
- Potentiometers
- Timers
- Microcontrollers
- Microprocessors or CPU

Integrated Circuit

<https://www.youtube.com/watch?v=cIlwGFcDLhI>
30-min intro course on IC design and manufacture



- Introduction to **Information**
 - **Exchange of information** – essence of any machine!
 - **Digital v Analog** signal
 - **Accuracy v Precision**
- **Electronics**
 - Revisit Engineering
 - Information in Electronics and Software
 - Common terminologies (**PCB, IC**)
- **Logic Gates**



What is a Computer?

It is essentially a really big and complex electronic circuit that **processes binary information** using **logical circuits**

Logical circuit (as the name suggests) uses logic (*if “A is happening” then “make B happen”*) to arrive at decisions

The basic building block of logical circuits is a **logic gate**


There are mainly 3 kinds of gates:

AND – outputs HI if all inputs are HI

OR – outputs HI if any input is HI

NOT – inverts the binary input (HI becomes LO and LO becomes HI)


AND

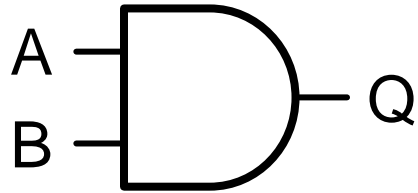

Truth Table


A	B	Q	Remark
0	0	0	HI if all inputs are HI
0	1	0	
1	0	0	
1	1	1	

OR

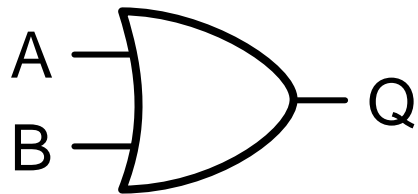



A	B	Q	Remark
0	0	0	HI if any input is HI
0	1	1	
1	0	1	
1	1	1	

NOT

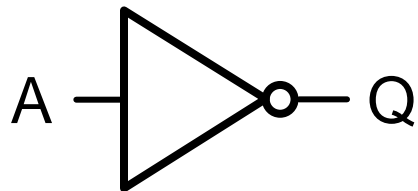


A	Q	Remark
0	1	Bit inversion
1	0	

This is an Integrated Circuit, or IC!

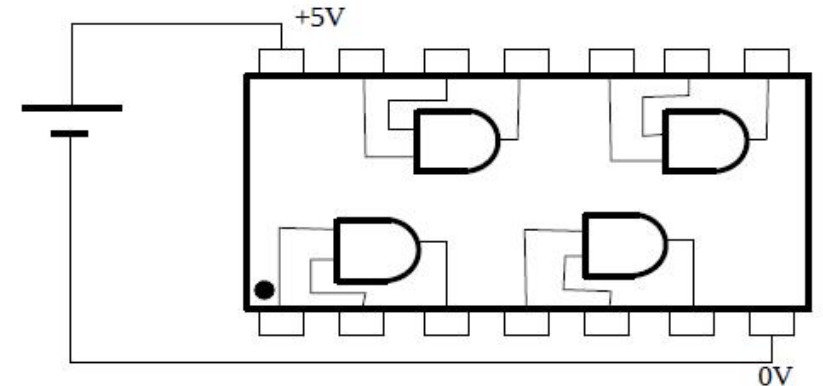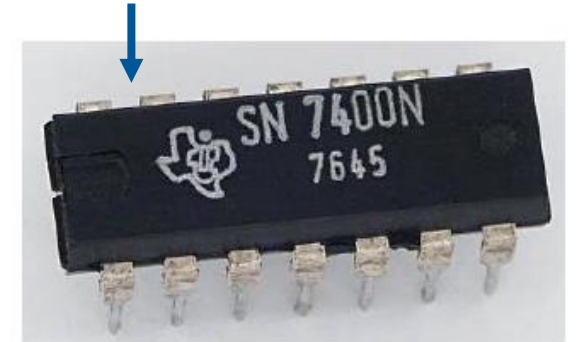


NAND

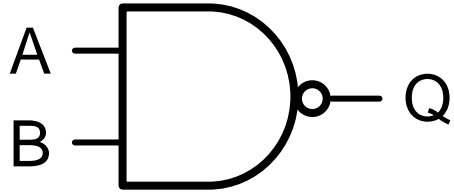

Truth Table


A	B	Q	Remark
0	0	1	LO if all inputs are HI
0	1	1	
1	0	1	
1	1	0	

NOR

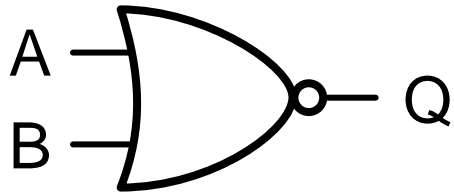



A	B	Q	Remark
0	0	1	LO if any input is HI
0	1	0	
1	0	0	
1	1	0	

XOR

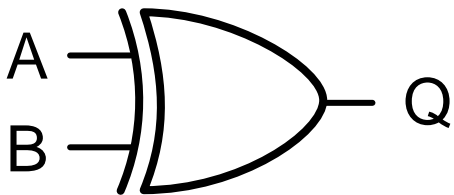

A	B	Q	Remark
0	0	0	HI if at least one input is HI and one is LO
0	1	1	
1	0	1	
1	1	0	

This is an Integrated Circuit, or IC!

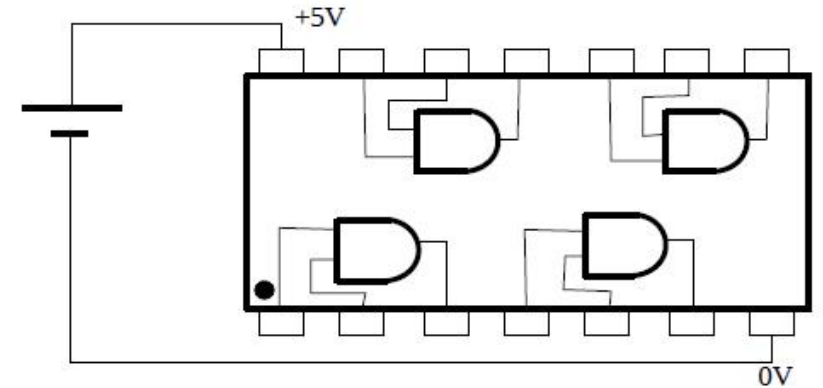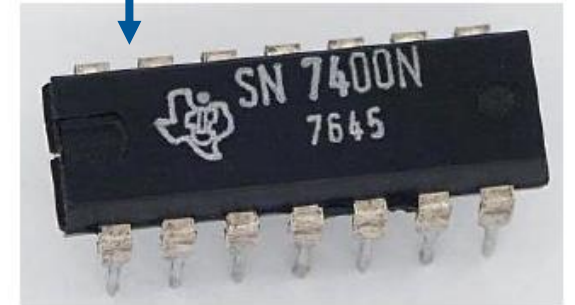


Example 1

We want to sound a siren when:

The alarm has been **set**

AND

Someone **steps on** the pressure sensor

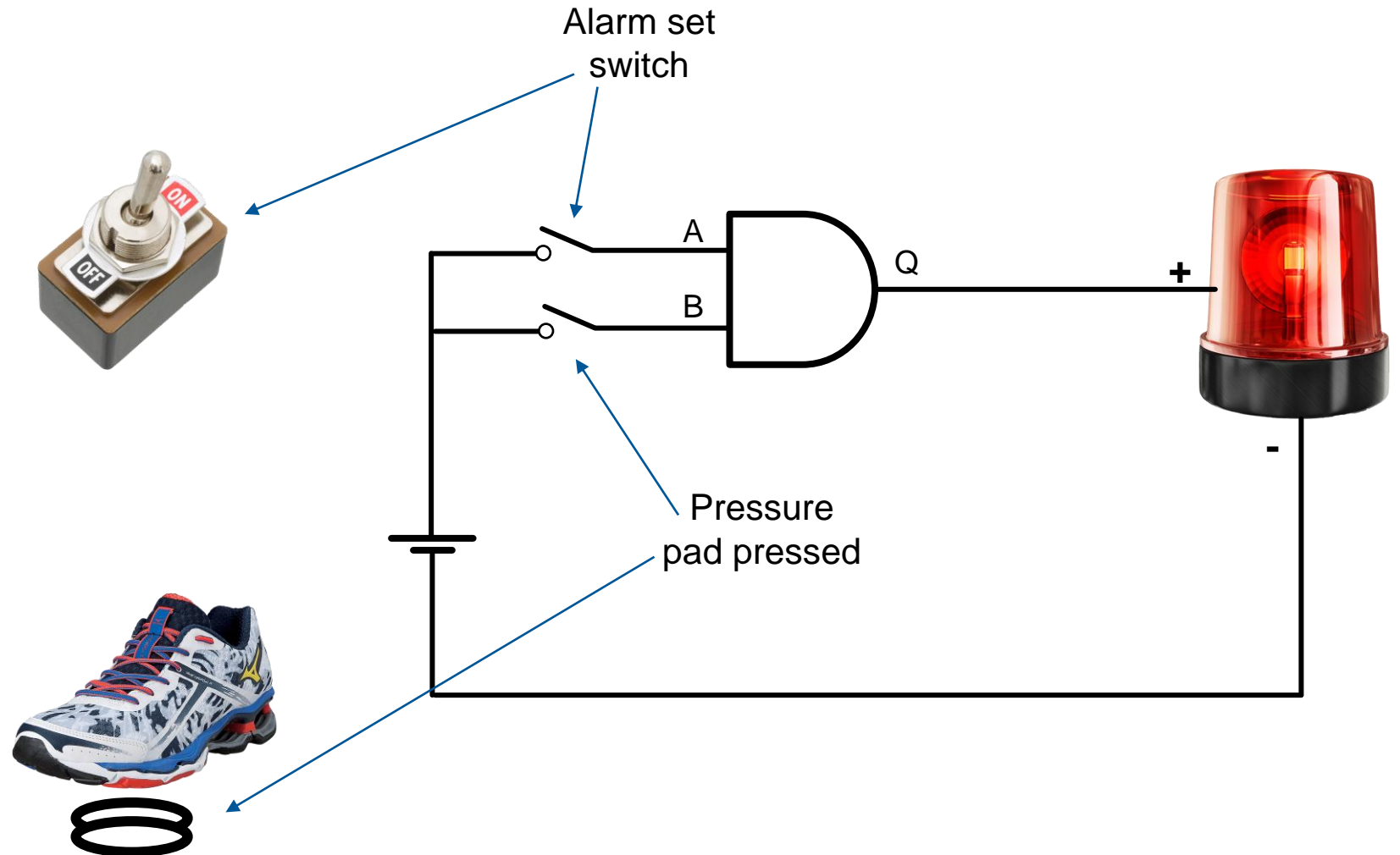

Example 2

We want to sound a siren when:


The alarm has been **set**

AND

Someone **steps on** the pressure sensor


OR

Smoke detected

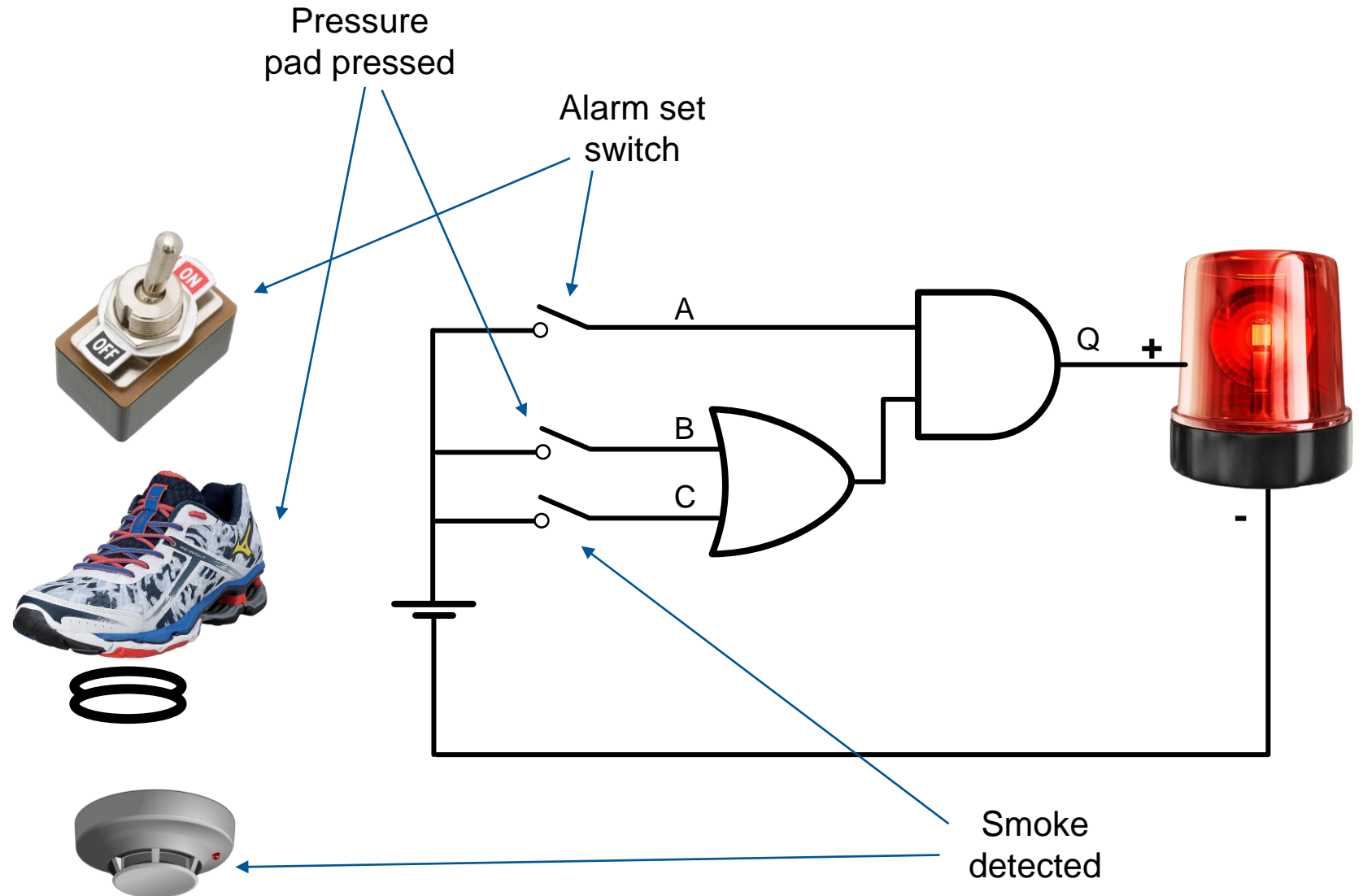



Example 3

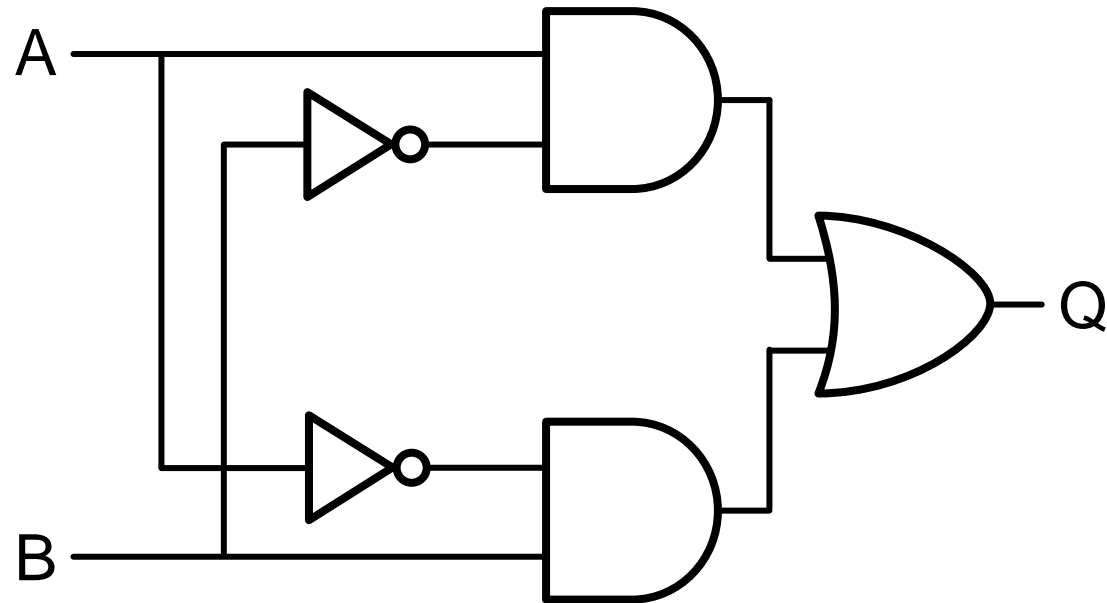

Step 1 – Identify how many inputs there are

Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits


Step 3 – Try each input combination in the logic gate

Step 4 – Propagate the “logic” all the way to output

Step 5 – Fill the truth table row by row



Example 3

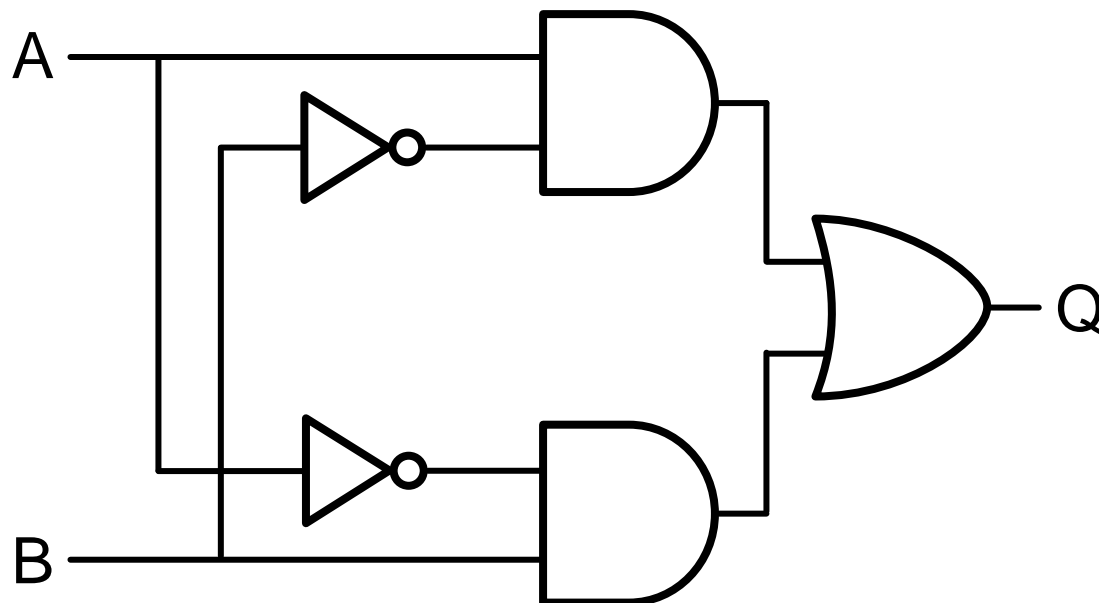

Total inputs = 2

Total combinations possible = $2^n = 4$

4 rows in truth table

~~Step 1 – Identify how many inputs there are~~


Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits

Step 3 – Try each input combination in the logic gate

Step 4 – Propagate the “logic” all the way to output

Step 5 – Fill the truth table row by row

Example 3

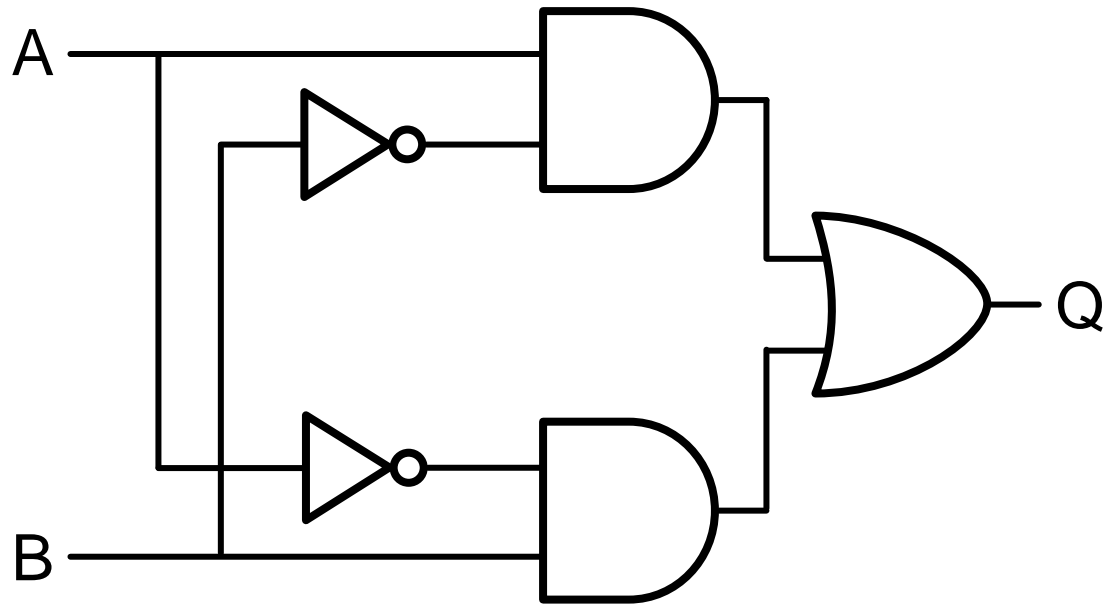

Total inputs = 2

Total combinations possible = $2^n = 4$

4 rows in truth table

A	B	Q	Remark
0	0		
0	1		
1	0		
1	1		

~~Step 1 – Identify how many inputs there are~~


~~Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits~~

~~Step 3 – Try each input combination in the logic gate~~

~~Step 4 – Propagate the “logic” all the way to output~~

~~Step 5 – Fill the truth table row by row~~

Example 3

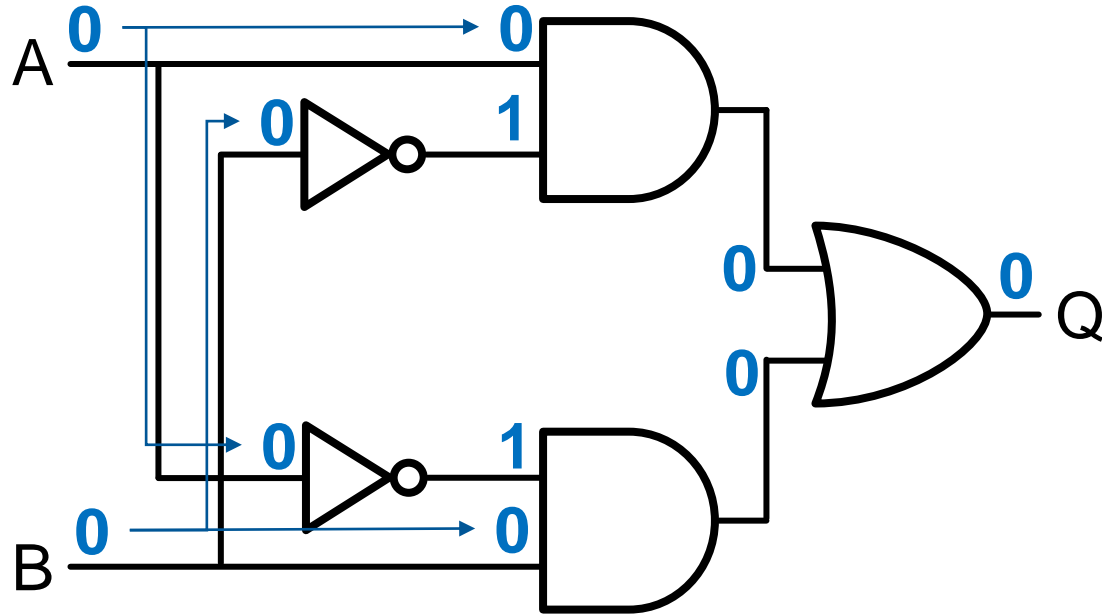

Total inputs = 2

Total combinations possible = $2^n = 4$

4 rows in truth table

A	B	Q	Remark
0	0		
0	1		
1	0		
1	1		

~~Step 1 – Identify how many inputs there are~~


~~Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits~~

~~Step 3 – Try each input combination in the logic gate~~

~~Step 4 – Propagate the “logic” all the way to output~~

~~Step 5 – Fill the truth table row by row~~

Example 3

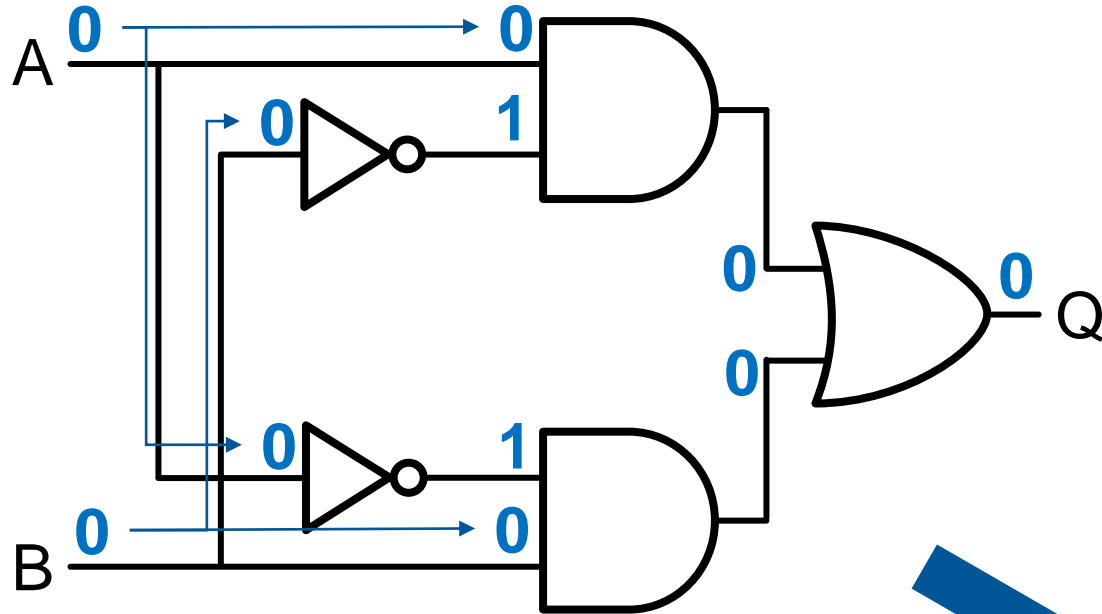

Total inputs = 2

Total combinations possible = $2^n = 4$

4 rows in truth table

A	B	Q	Remark
0	0	0	This is XOR gate
0	1	1	
1	0	1	
1	1	0	


~~Step 1 – Identify how many inputs there are~~

~~Step 2 – Draw a truth table with as many number of rows as possible combinations of input bits~~

~~Step 3 – Try each input combination in the logic gate~~

~~Step 4 – Propagate the “logic” all the way to output~~



~~Step 5 – Fill the truth table row by row~~

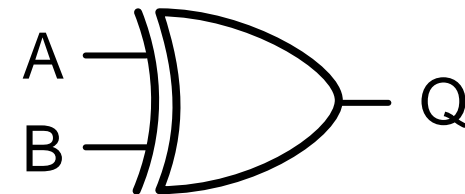



Example 4

- Imagine you are designing a circuit to monitor a digital thermometer embedded in a nuclear reactor
- You want to automatically shut off the reactor when the cooling fluid rises above 50°C
- It would also be bad if the coolant froze – shut down the reactor!
- Thermometer gives a 3-bit binary output in 10°C steps –
 - $2^3 = 8$ levels
 - Count from 0 to $2^3 - 1 = 7$
 - **0°C to 80°C** range of output

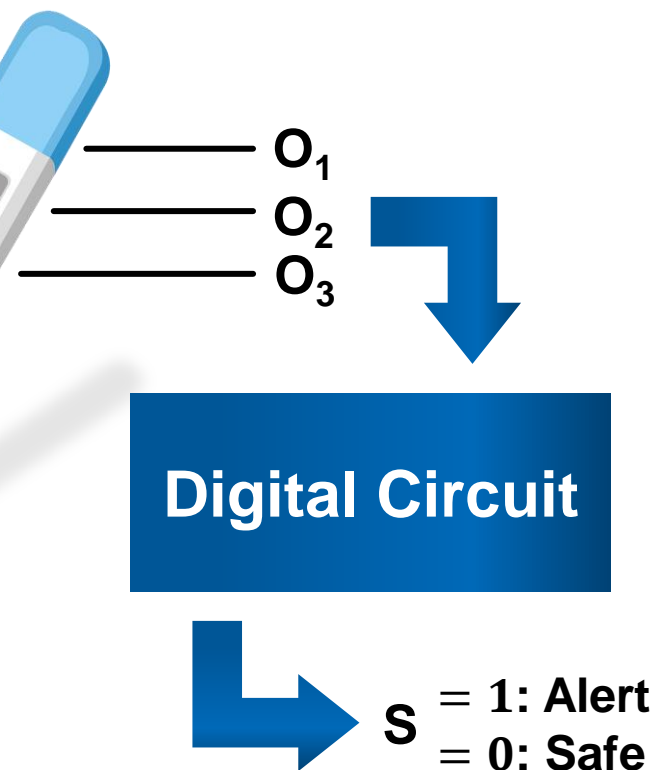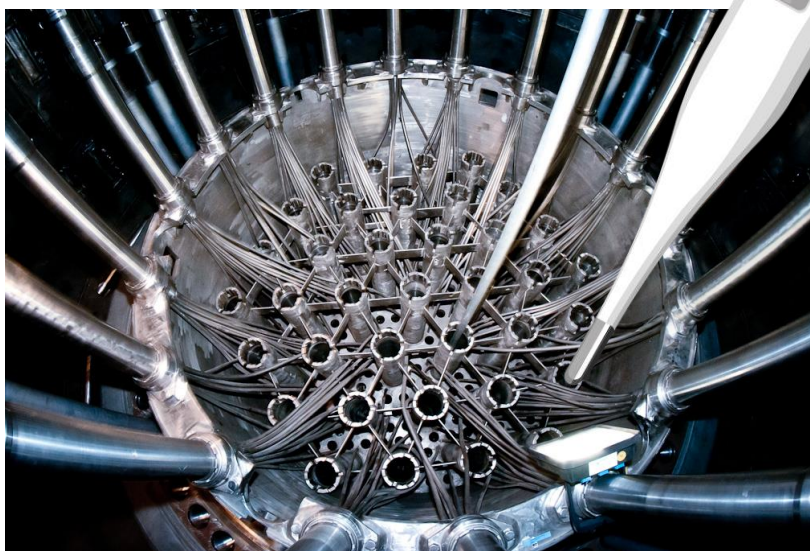




Example 4

O ₁	O ₂	O ₃
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Remember what Step-1 was?

Identify all possible **combinations of input bits** and make the **truth table** – one row per combination

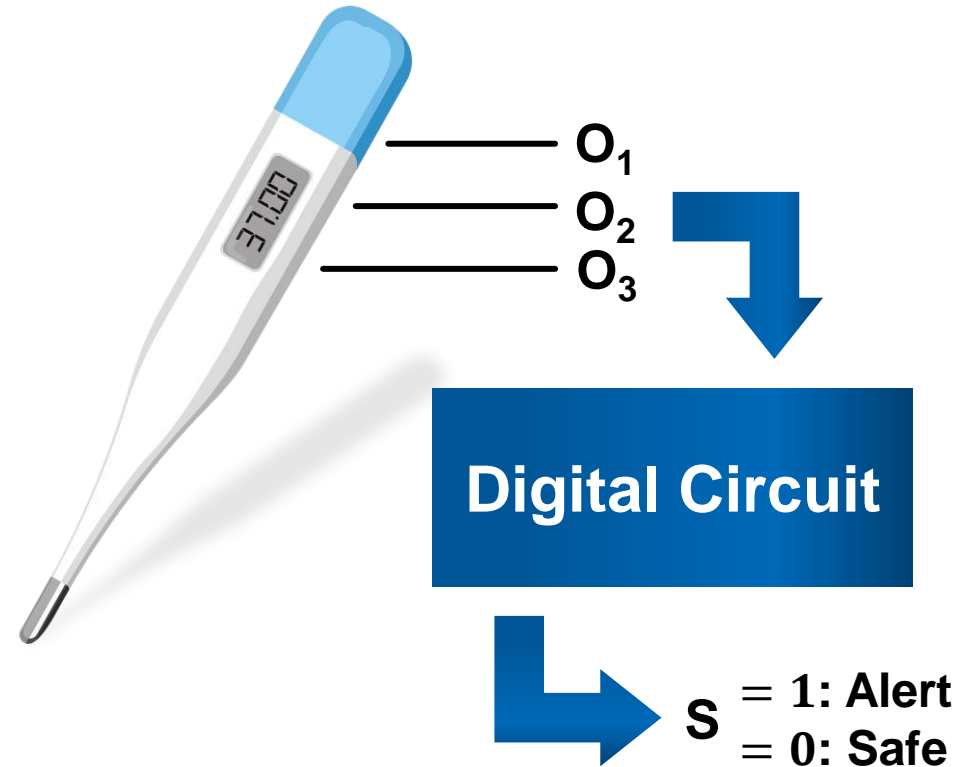




Example 4

O ₁	O ₂	O ₃	Dec
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

For this case, what would help is to have the **decimal conversion of the binary** number

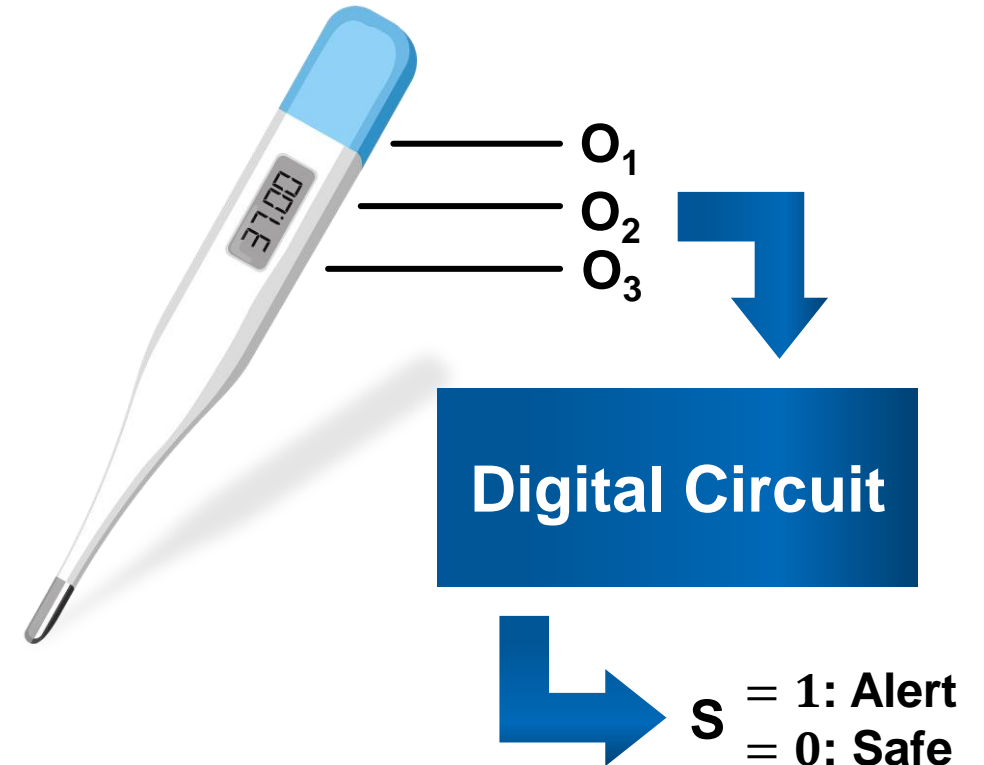




Example 4

O ₁	O ₂	O ₃	Dec	Temp
0	0	0	0	0°C
0	0	1	1	10°C
0	1	0	2	20°C
0	1	1	3	30°C
1	0	0	4	40°C
1	0	1	5	50°C
1	1	0	6	60°C
1	1	1	7	70°C

We know that the binary number represents the physical temperature in **steps of 10°C**, i.e., scaling factor of 10x

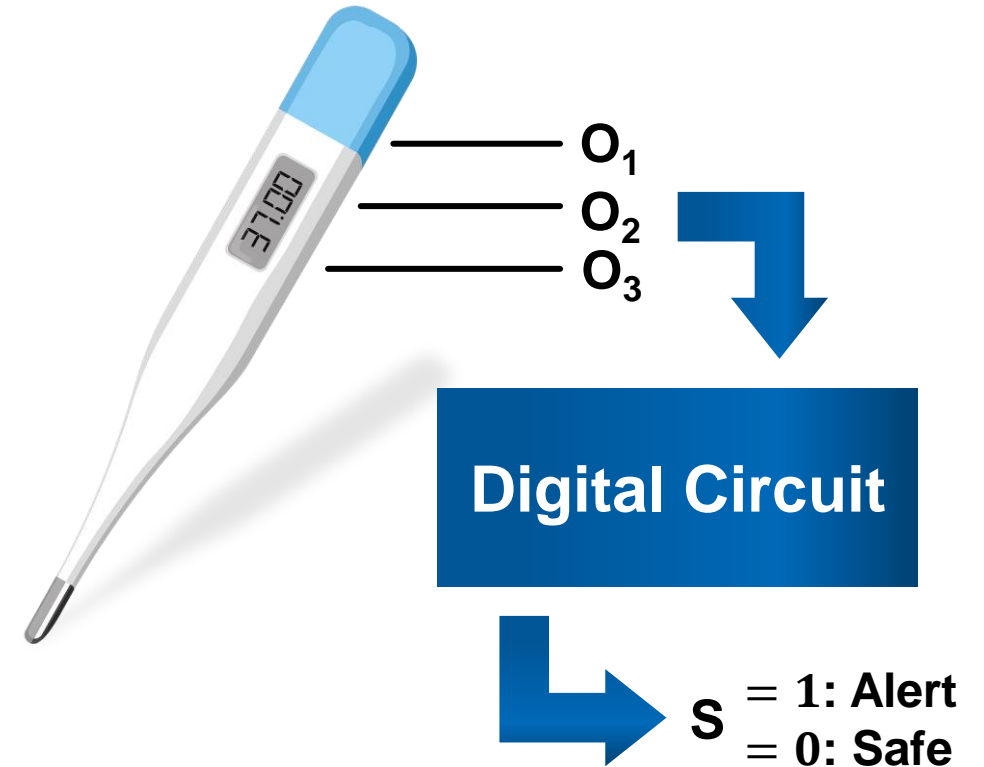




Example 4

O ₁	O ₂	O ₃	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

S = 1 indicating Alert when temperature is either $<0^{\circ}\text{C}$ OR $>50^{\circ}\text{C}$

Otherwise, **S = 0 indicating Safe**

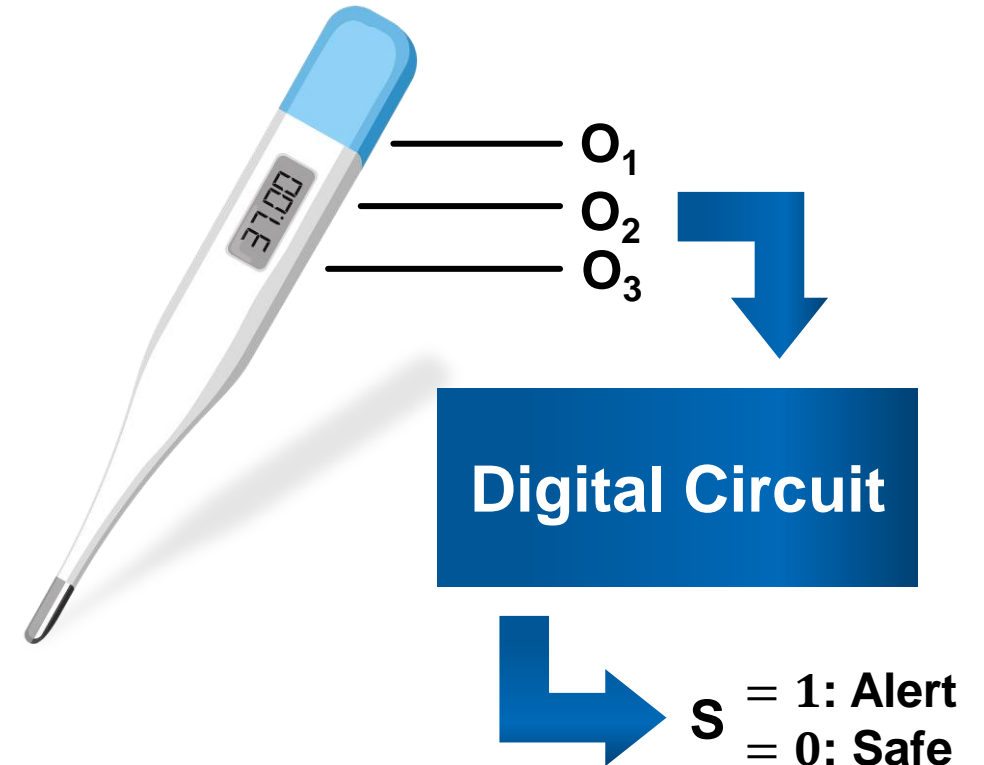




Example 4

O ₁	O ₂	O ₃	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

Once you have the truth table, you have a choice:

- Design for the **HI**, or **1s** (use AND/OR)
- Design for the **LO**, or **0s** (use NAND/NOR)

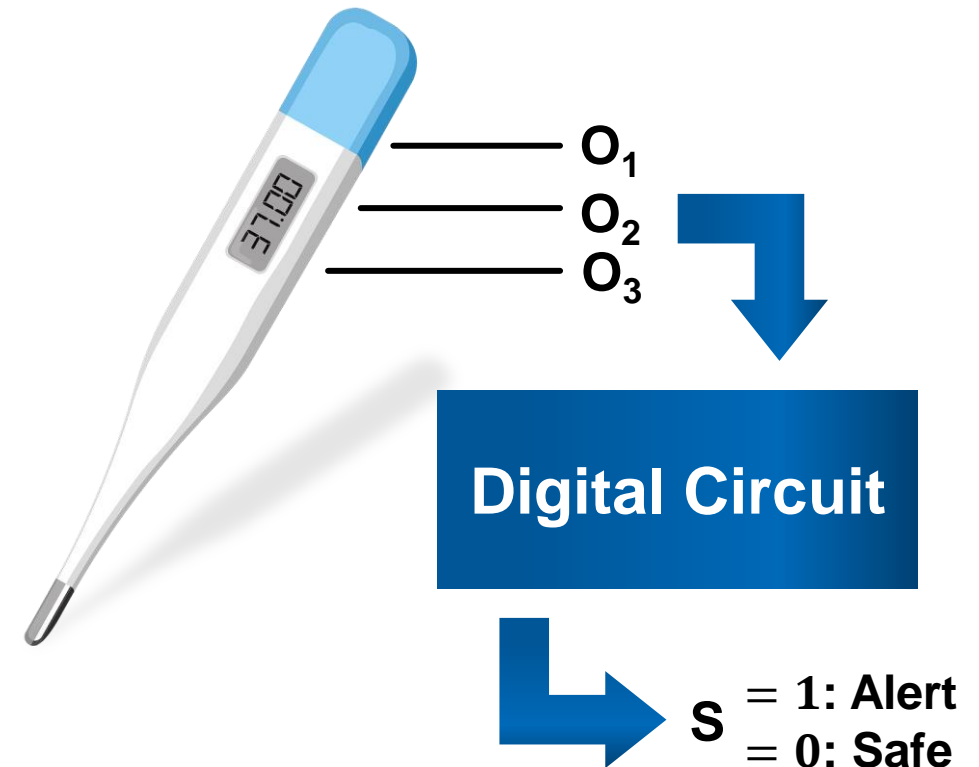

Example 4


O ₁	O ₂	O ₃	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

The choice usually requires thinking about practical issues, like what would happen if a fault in the circuit occurs (concept of Active HI and Active LO logic, we don't need to study this), is the default state of output safe etc.

In our example, we will simply see that there are 5 LOs and 3 HIs. This means its less time-consuming to build for HIs.

Once you have the truth table, you have a choice:

- Design for the **HI**, or **1s** (use AND/OR)
- Design for the **LO**, or **0s** (use NAND/NOR)

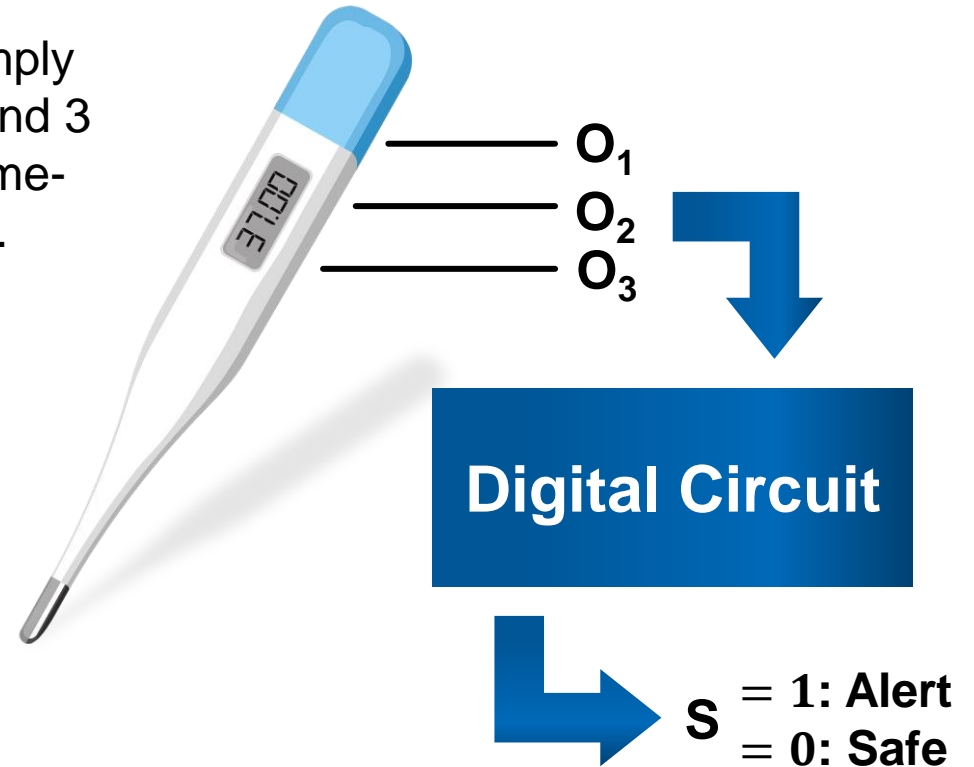


Example 4

O ₁	O ₂	O ₃	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

Now let us try to think of this truth table in “if-then-else” decision-making process


S=1 (as we said solving for HI) if:

- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$

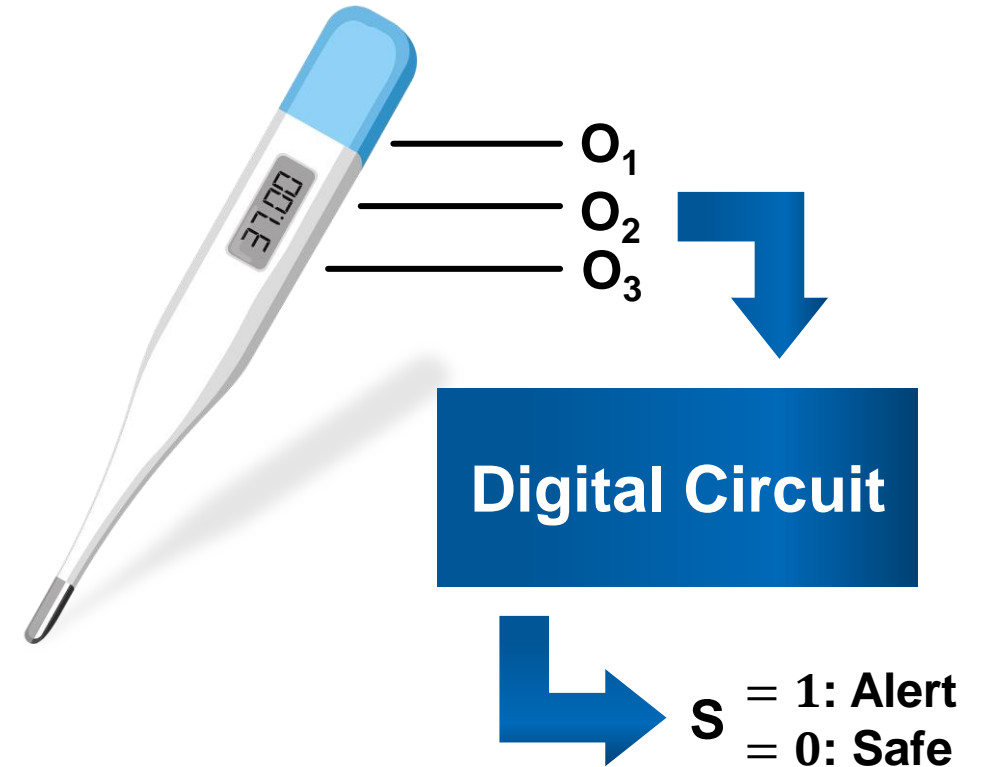

Example 4

O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

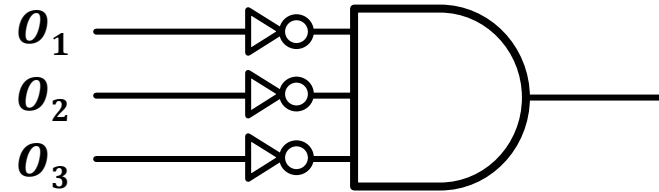


$S=1$ (as we said solving for HI) if:

- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$

Example 4

O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

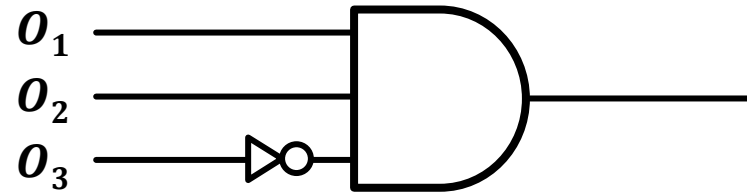

$S=1$ (as we said solving for HI) if:


- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$

Example 4

O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

S=1 (as we said solving for HI) if:

- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$

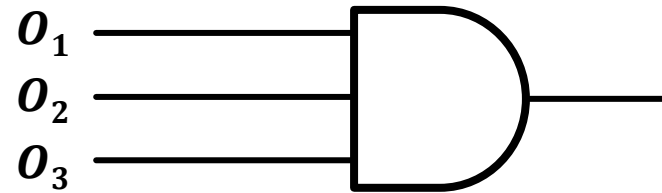


Example 4

O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1

$S=1$ (as we said solving for HI) if:

- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ **OR**
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ **OR**
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$


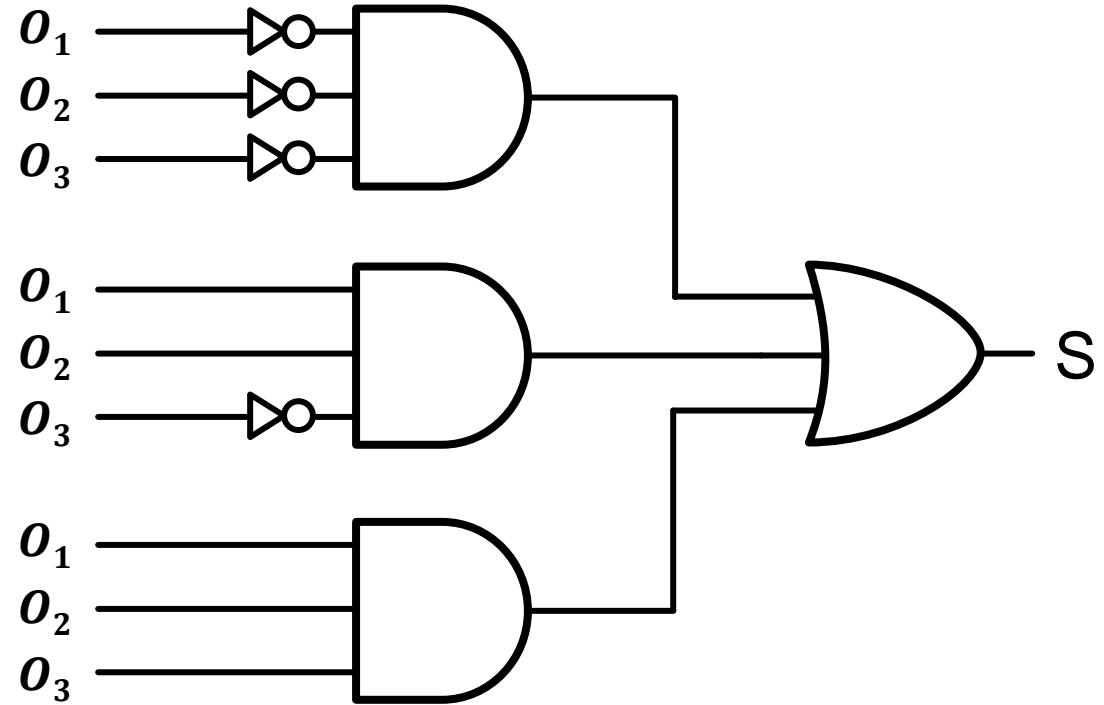


Example 4

O_1	O_2	O_3	Dec	Temp	S
0	0	0	0	0°C	1
0	0	1	1	10°C	0
0	1	0	2	20°C	0
0	1	1	3	30°C	0
1	0	0	4	40°C	0
1	0	1	5	50°C	0
1	1	0	6	60°C	1
1	1	1	7	70°C	1


S=1 (as we said solving for HI) if:

- $O_1 = 0$ AND $O_2 = 0$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 0$ OR
- $O_1 = 1$ AND $O_2 = 1$ AND $O_3 = 1$

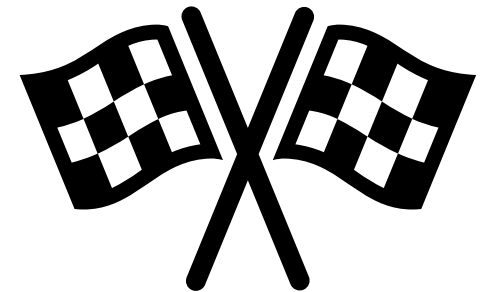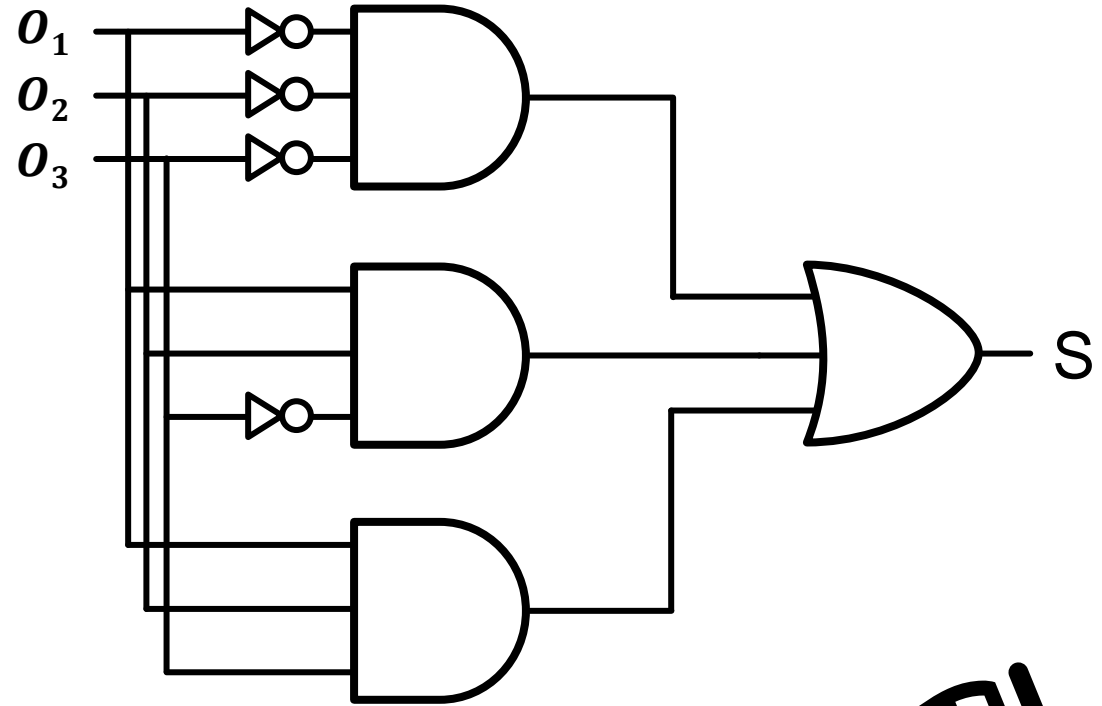


Example 5

What Floor are you on?
Digital Display

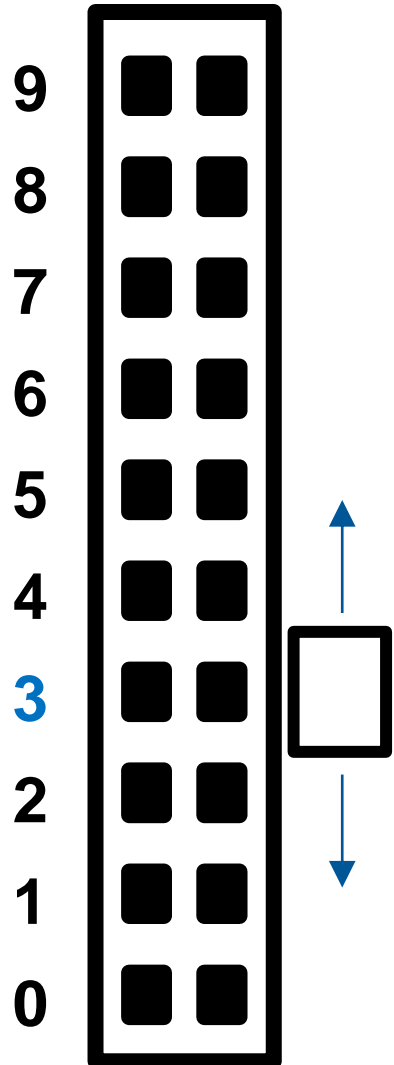



Lift

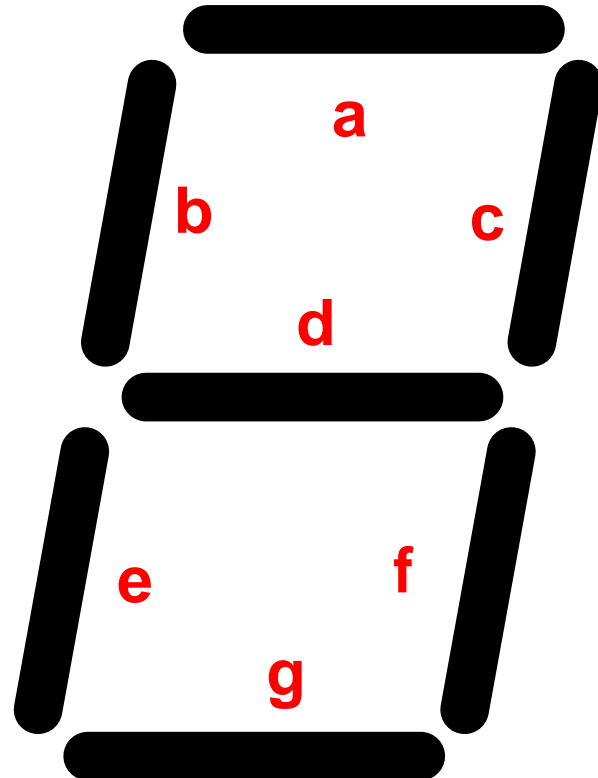

	a	b	c	d	e	f	g
0							
1							
2							
3							
4							
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

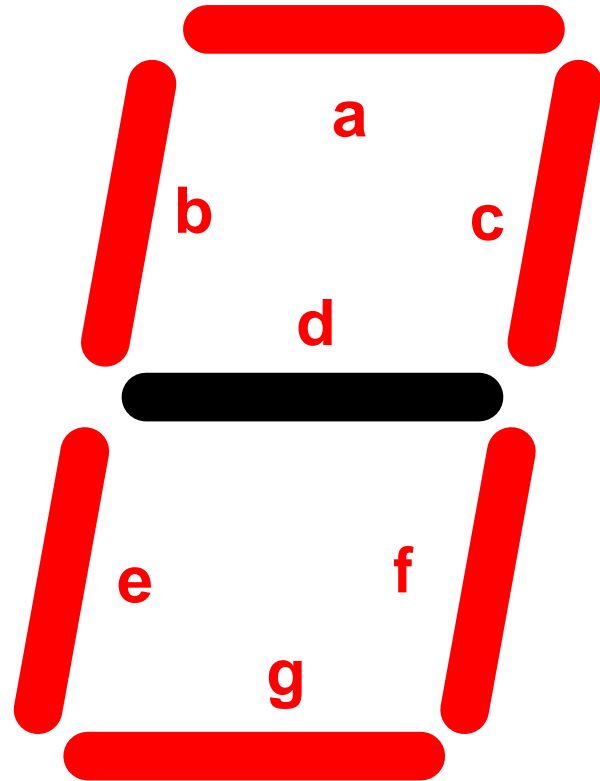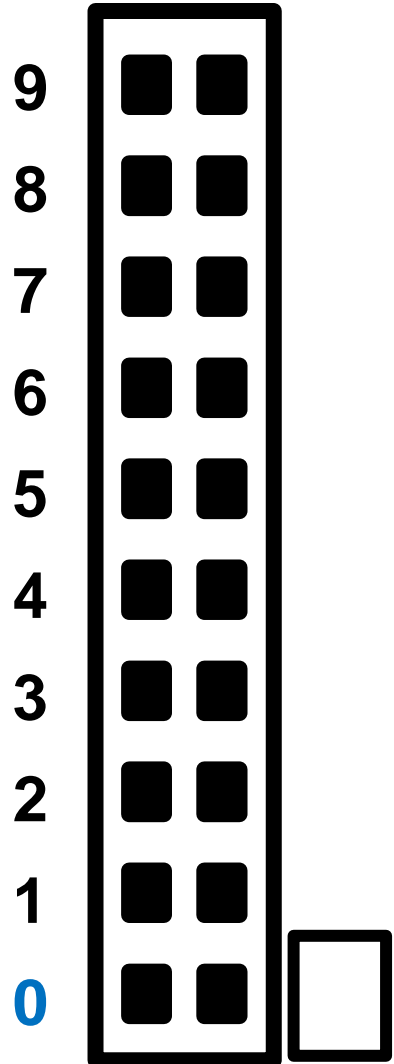

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1							
2							
3							
4							
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

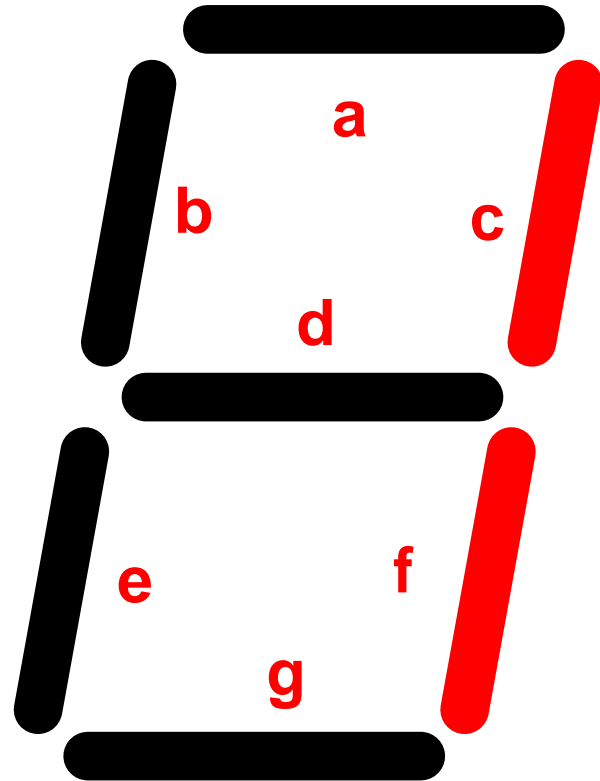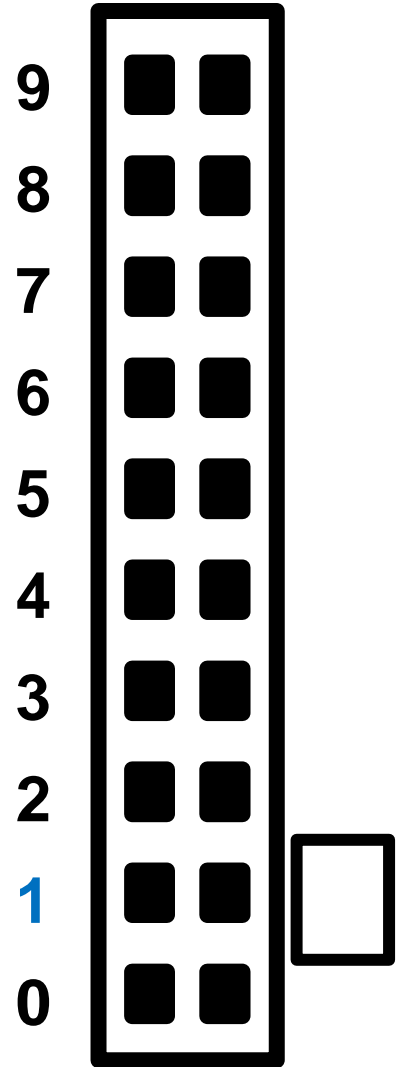

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2							
3							
4							
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

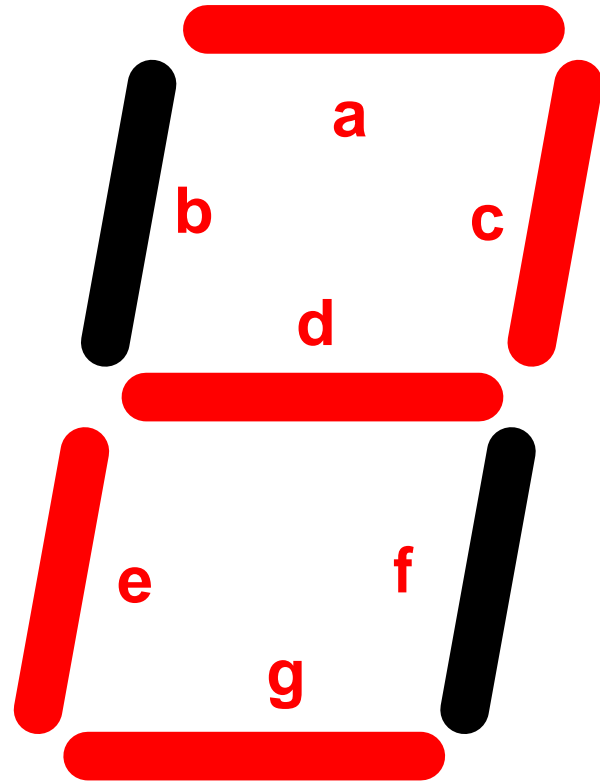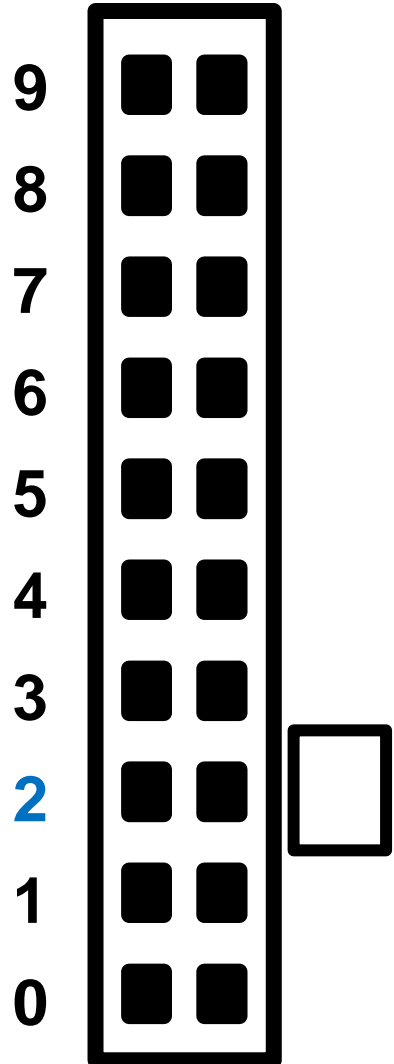

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3							
4							
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

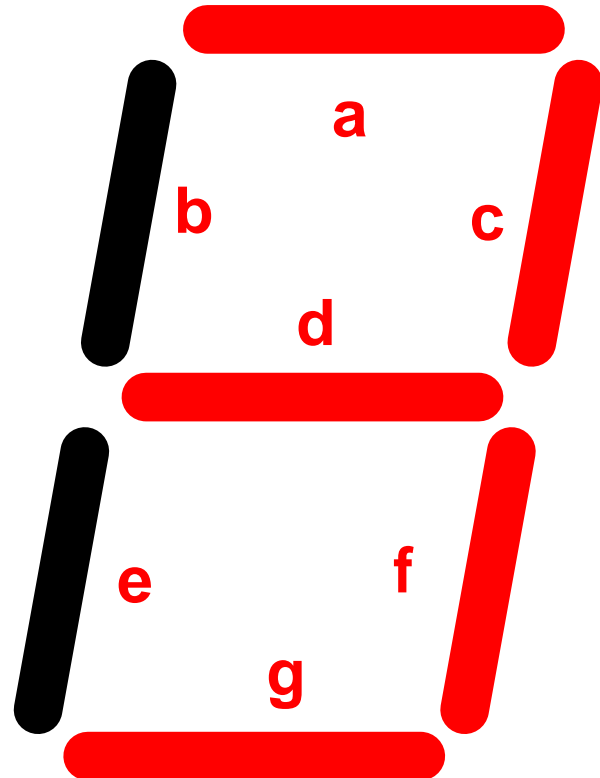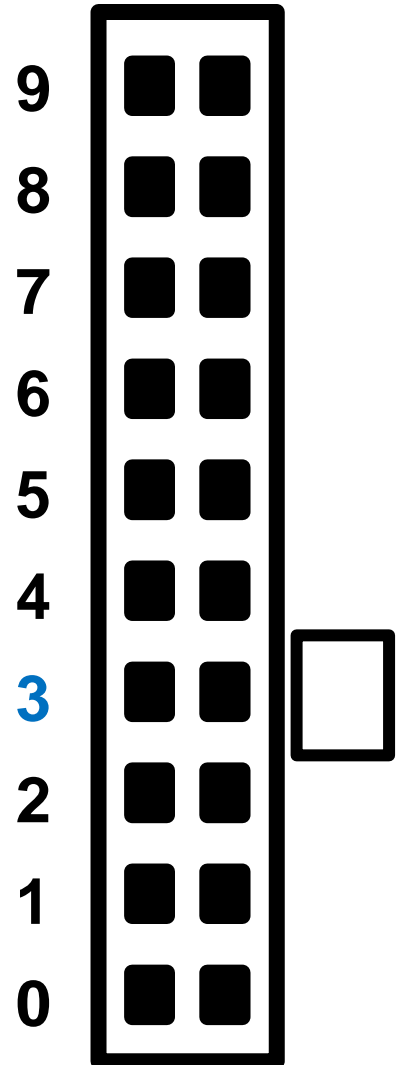

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4							
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

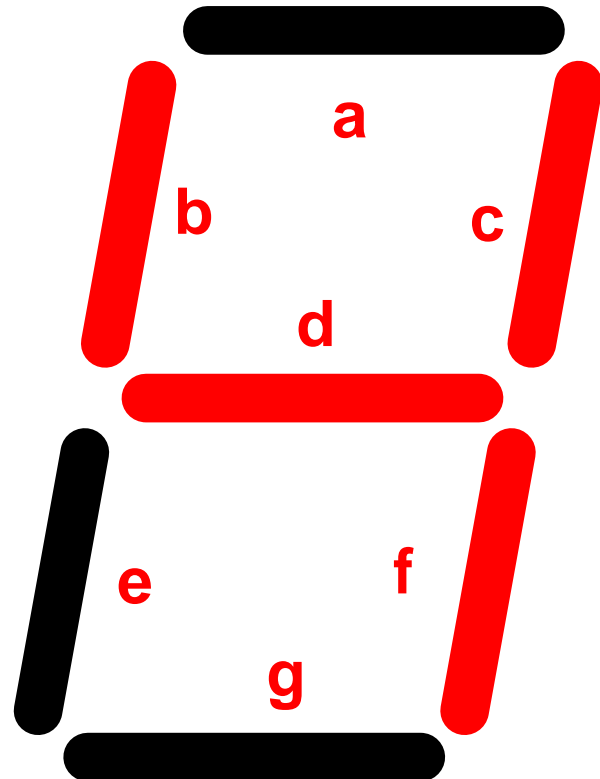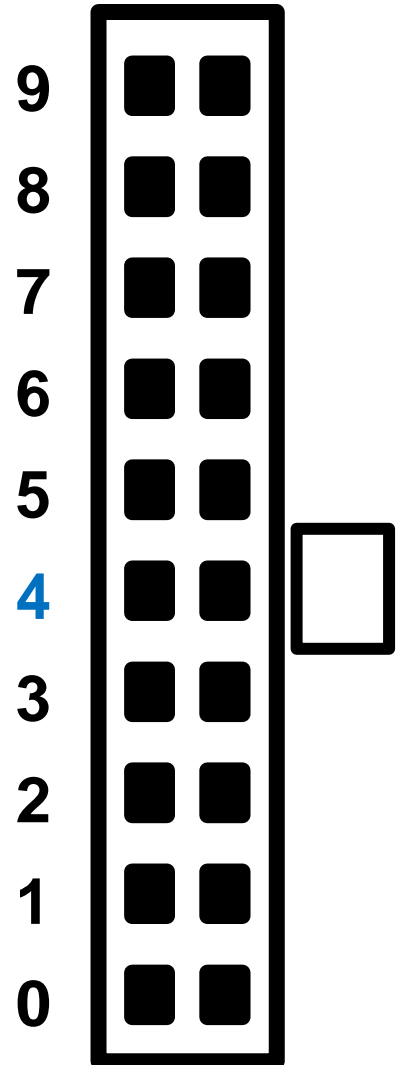

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5							
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

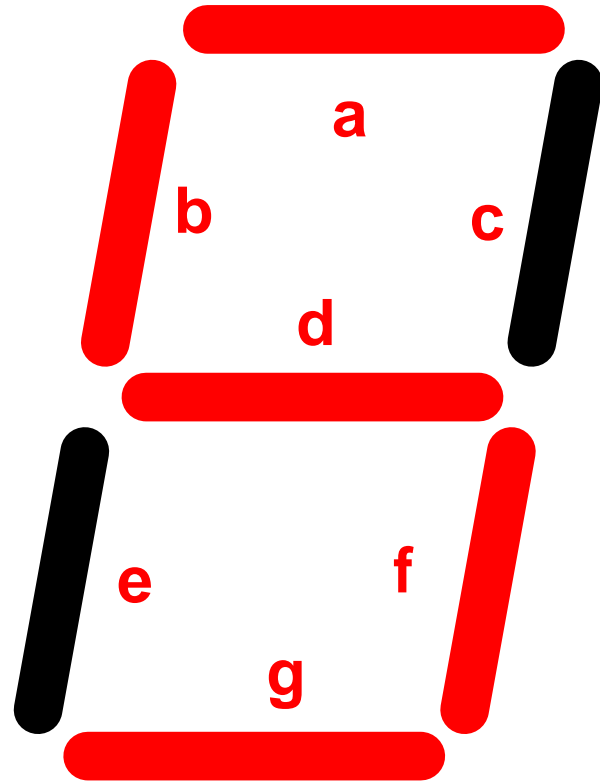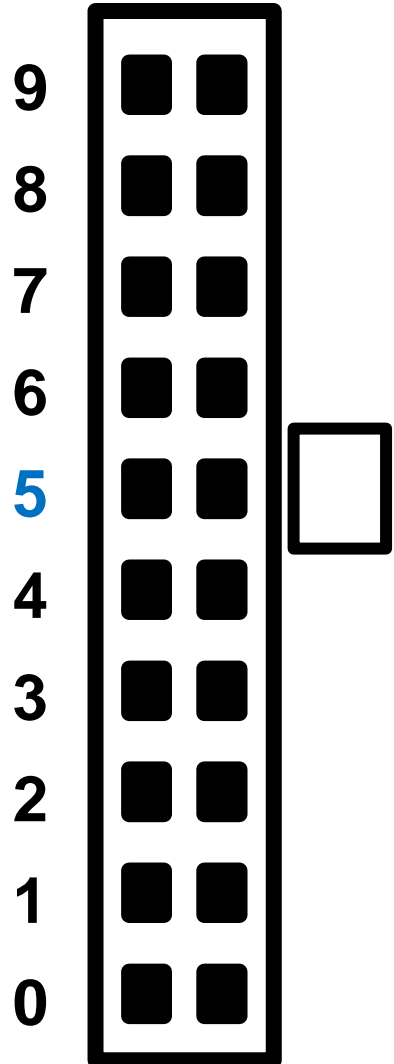

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6							
7							
8							
9							

Example 5



What Floor are you on?
Digital Display

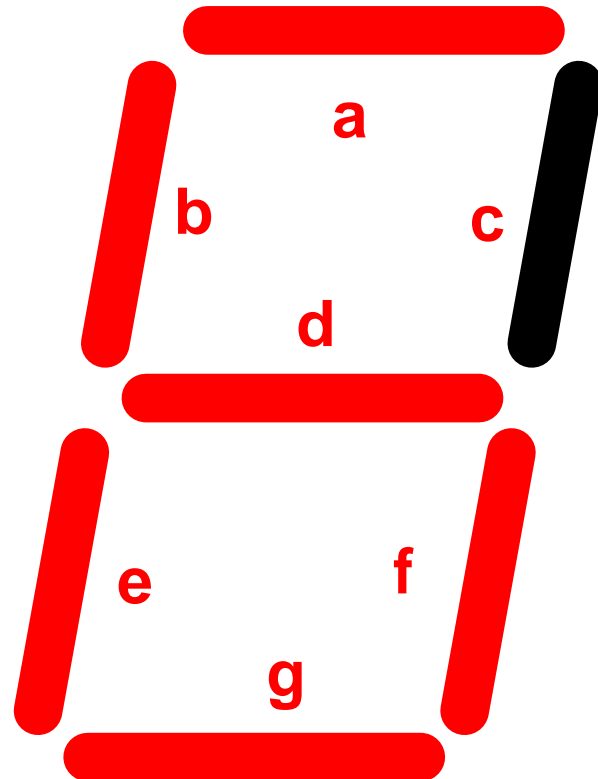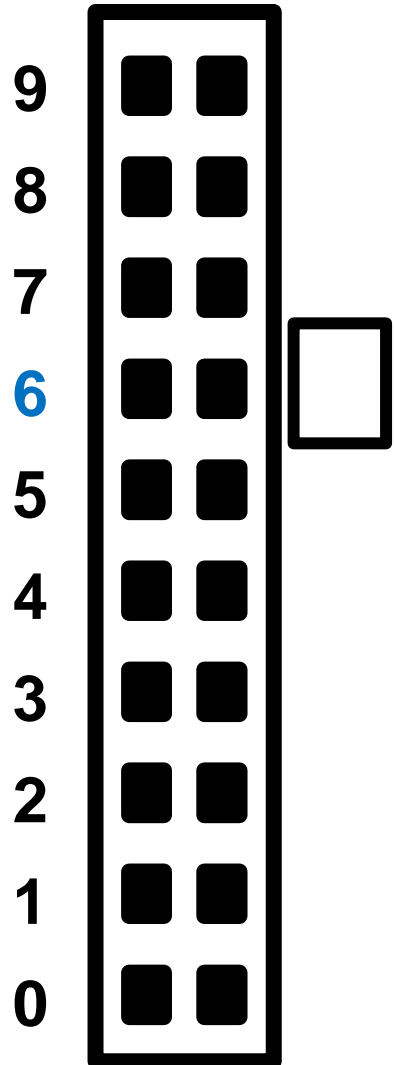

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7							
8							
9							


Example 5

What Floor are you on?
Digital Display

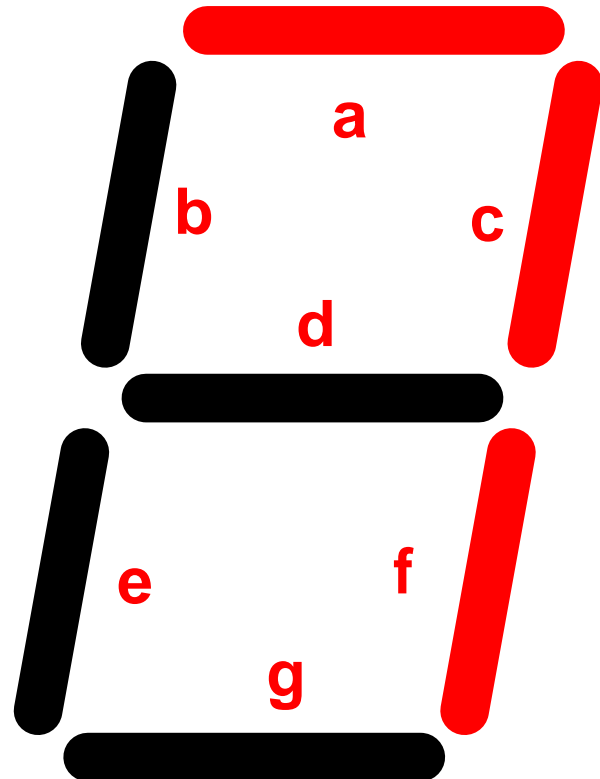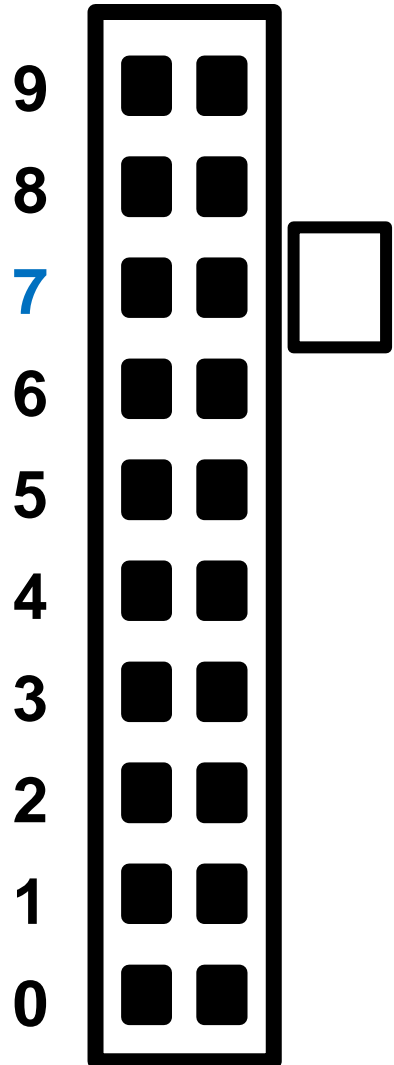


	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7	1	0	1	0	0	1	0
8							
9							

Example 5

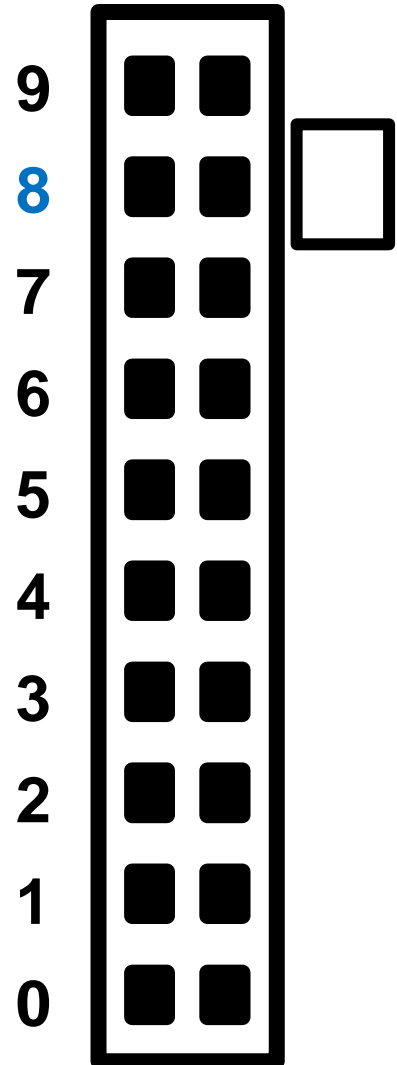


What Floor are you on?
Digital Display

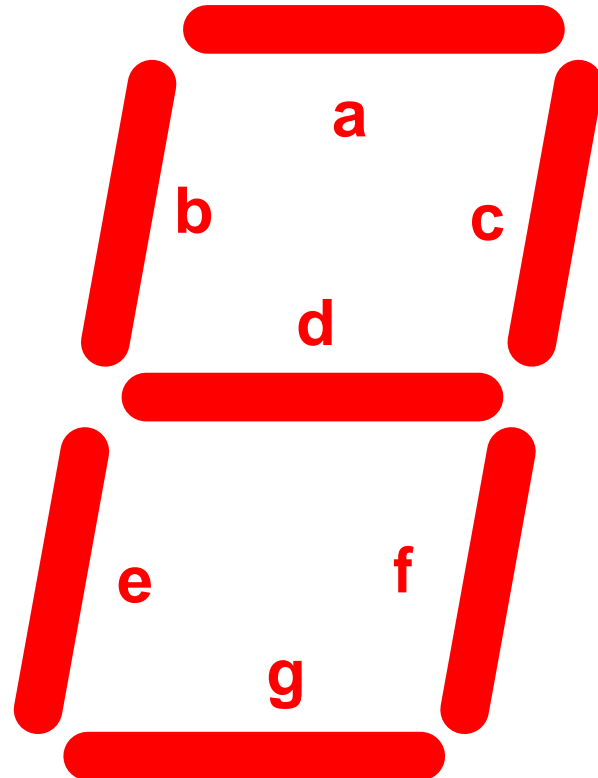


	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7	1	0	1	0	0	1	0
8	1	1	1	1	1	1	1
9							








Example 5

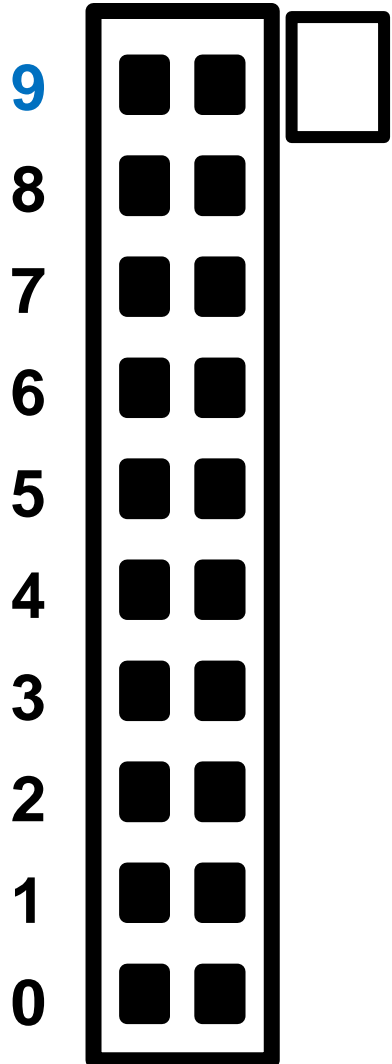

What Floor are you on?
Digital Display

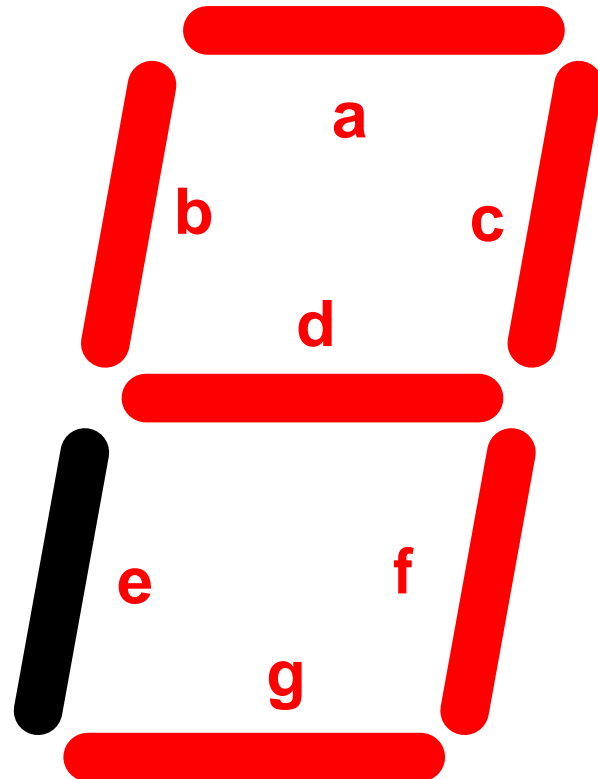

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7	1	0	1	0	0	1	0
8	1	1	1	1	1	1	1
9	1	1	1	1	0	1	1

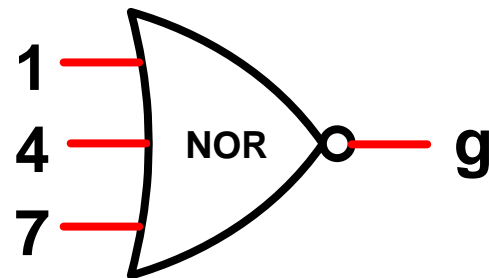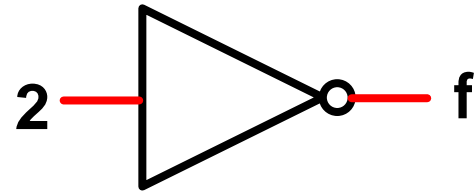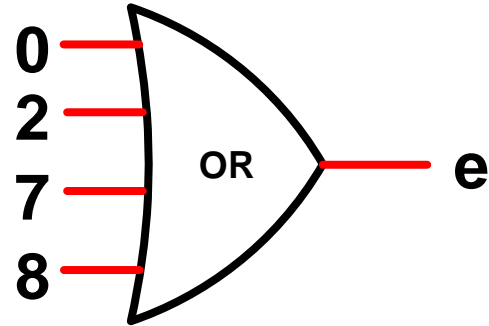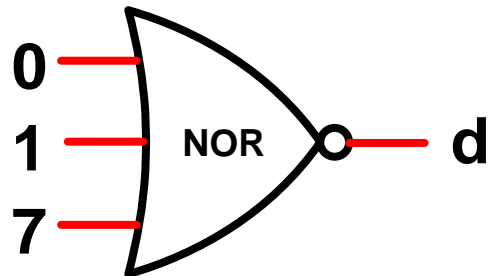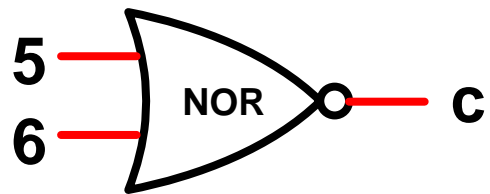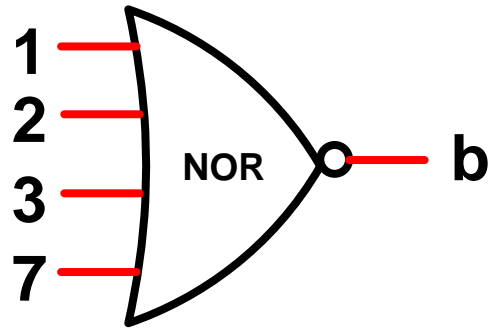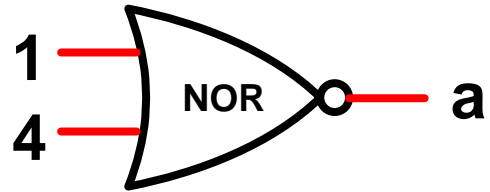

	a	b	c	d	e	f	g
0	1	1	1	0	1	1	1
1	0	0	1	0	0	1	0
2	1	0	1	1	1	0	1
3	1	0	1	1	0	1	1
4	0	1	1	1	0	1	0
5	1	1	0	1	0	1	1
6	1	1	0	1	1	1	1
7	1	0	1	0	0	1	0
8	1	1	1	1	1	1	1
9	1	1	1	1	0	1	1



- Introduction to **Information**
 - **Exchange of information** – essence of any machine!
 - **Digital v Analog** signal
 - **Accuracy v Precision**
- **Electronics**
 - Revisit Engineering
 - Information in Electronics and Software
 - Common terminologies (**PCB, IC**)
- Logic **Gates**



Attendance



UP|PHY|B1-MMME2051EMD