



University of  
**Nottingham**

UK | CHINA | MALAYSIA

# LECTURE 2A

## Simple Electrical Circuits


## Electromechanical Devices

MMME2051

Module Convenor – Surojit Sen



- **Basic Concepts (& Recap)**
  - Charge, current, voltage
  - Ohm's/Kirchhoff's Laws
  - Power & Energy
  - Measurement of Voltage & Current
  - Electrical symbols & notations
  - Solution of a simple electrical circuit using just Ohm's and Kirchhoff's Laws
- Electrical circuits
  - **Series & Parallel**
  - **Combination** of series & parallel
  - **Example circuits** (to be discussed in upcoming seminar)
- Further Reading

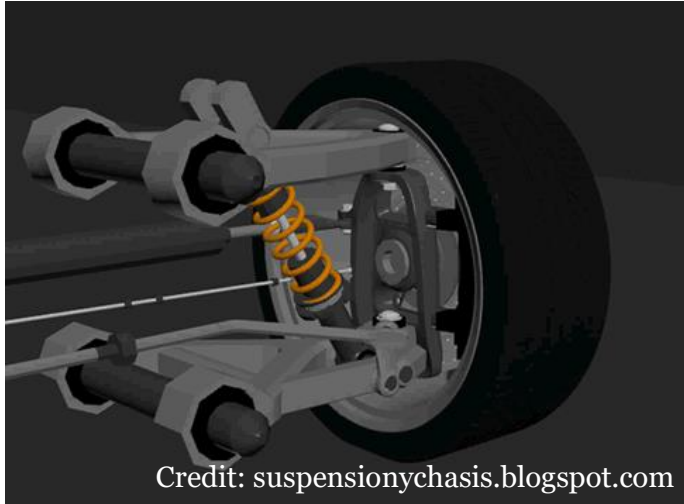

Suspension & chasses  
**Mechanical Engineering**



**Vehicle Control Unit (VCU)** that sends signals/commands to drive/stop the car  
**Electronic Engineering**


Code written to program the VCU  
**Computer/Software Engineering**



**Motor** that converts electrical power from battery to mechanical motion  
**Electromechanical Engineering**

**Battery** that supplies power to drive the motor  
**Electrical Engineering**

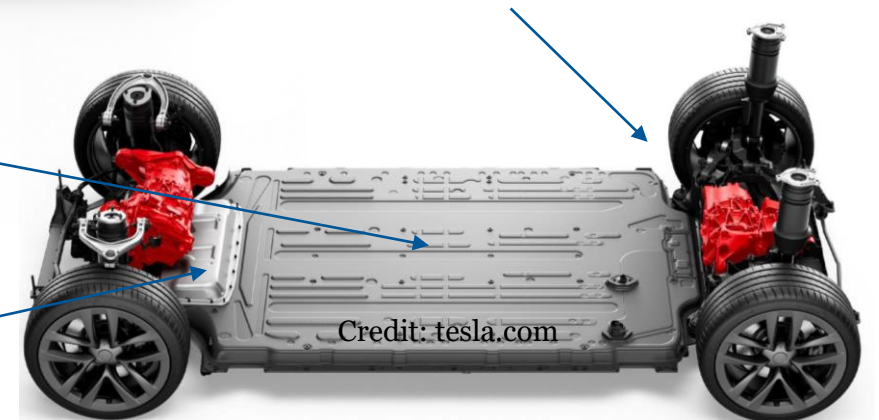**Power Converter** that controls the flow of electrical power between battery and motor  
**Power Electronics**




## Electric Charge

Some important characteristics of electric charge

- Charge can be positive or negative
- Nature's basic carrier of negative charge is the **electron**
- Nature's basic carrier of positive charge is the **proton**
- If an object has a deficit of electrons, it will exhibit a **net positive charge**
- If an object has a surplus of electrons, it will exhibit a **net negative charge**

Like  
charges  
repel

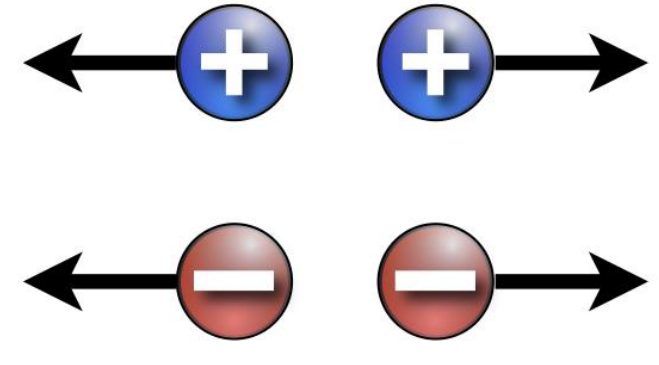

Opposite  
charges attract





## Electric Current



In a conductor, there are many free electrons and they move randomly

If the free electrons move consistently, a  
electron flow will be seen

Free electrons      Metal atom

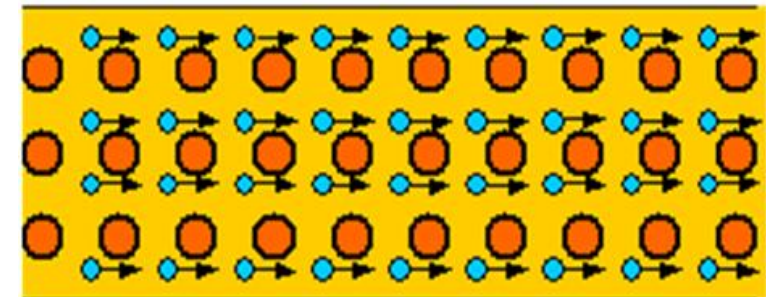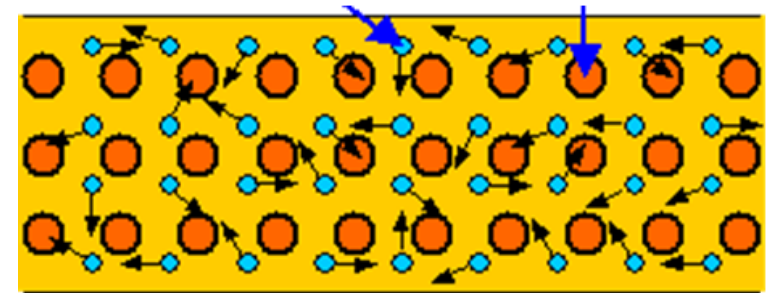


## Electric Potential (Voltage)

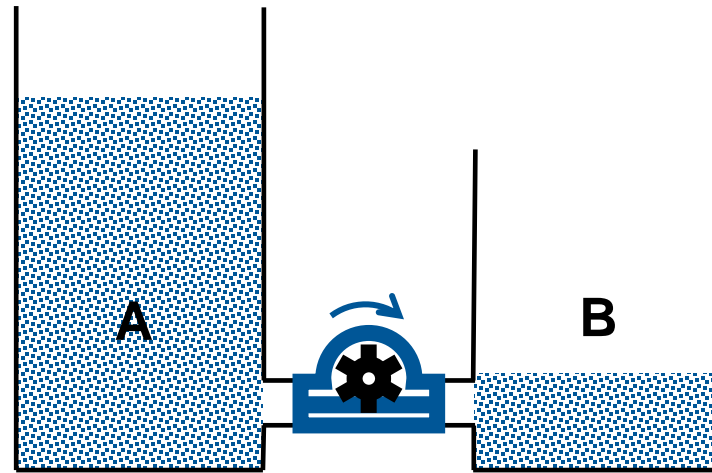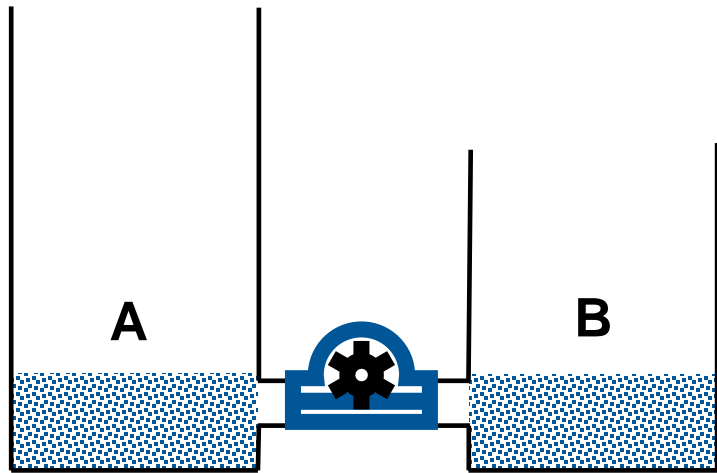

Higher  
Potential  
Energy

Lower  
Potential  
Energy

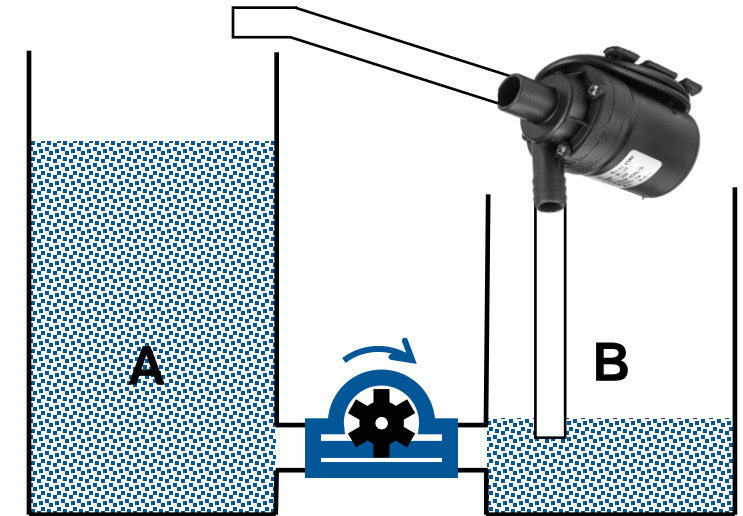

Higher  
Potential  
Energy


Lower  
Potential  
Energy

## Ohm's Law

Voltage is linearly proportional to resistance

$$V = IR$$

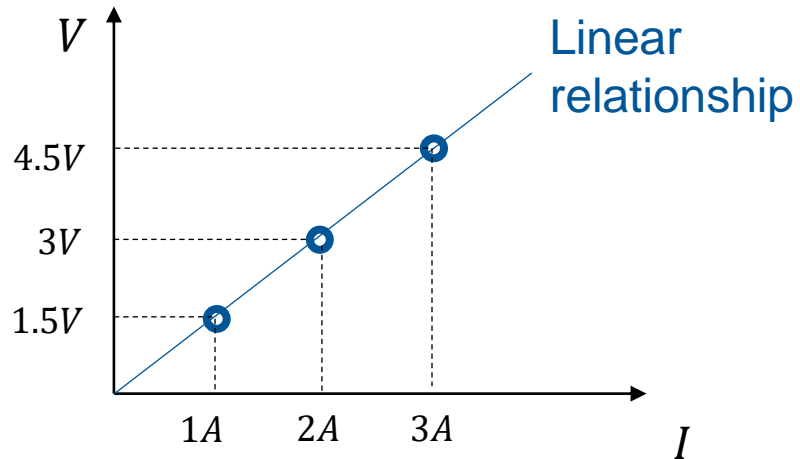Voltage →  $V$  ← Current  
Resistance →  $R$  ←



## Power

Product of voltage and current

$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

Unit is **Watt** (W)

## Energy

Accumulation of power over time

$$E = P\Delta t$$

$$E = I^2 R\Delta t$$

$$E = \frac{V^2}{R} \Delta t$$

Unit is **Joule** (J)


**Kilowatt-hour** (kWh) often used

## Conductor

Easily allows current to flow through it

$$R \rightarrow 0\Omega$$

All metals are conductors

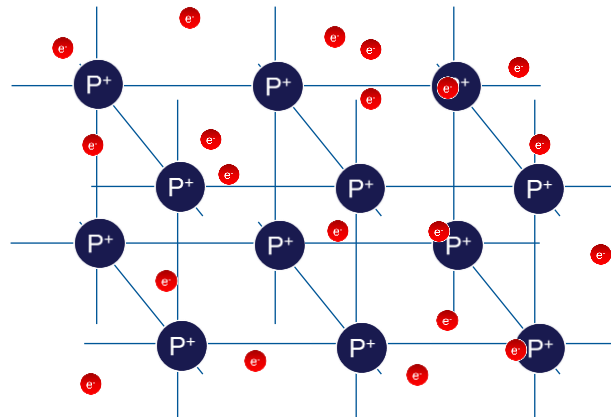


## Insulator

Strongly impedes flow of current through it

$$R \rightarrow \infty\Omega$$


Plastic, rubber, wood etc.

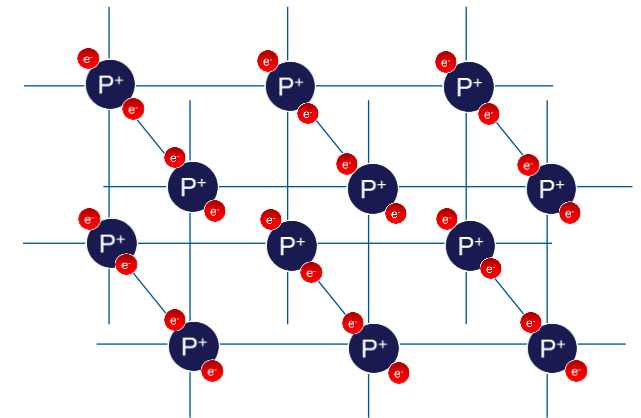


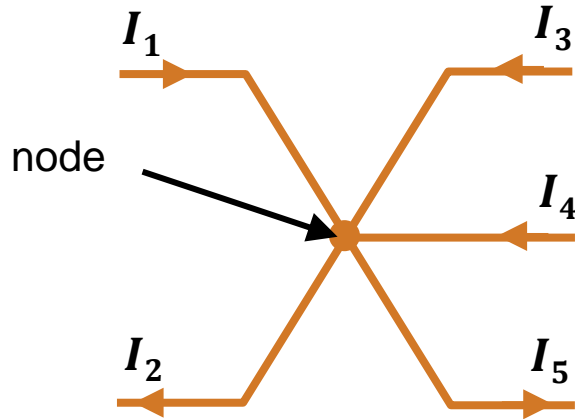
## Kirchhoff's Current Law


Algebraic sum of current entering a node is zero



$$\sum I_i = 0$$


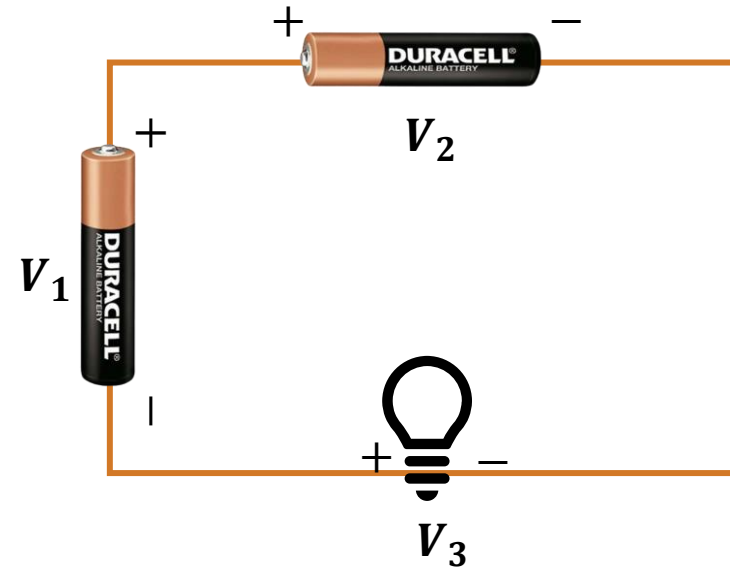
## Kirchhoff's Voltage Law

Algebraic sum of voltages around a closed loop is zero



$$\sum V_i = 0$$

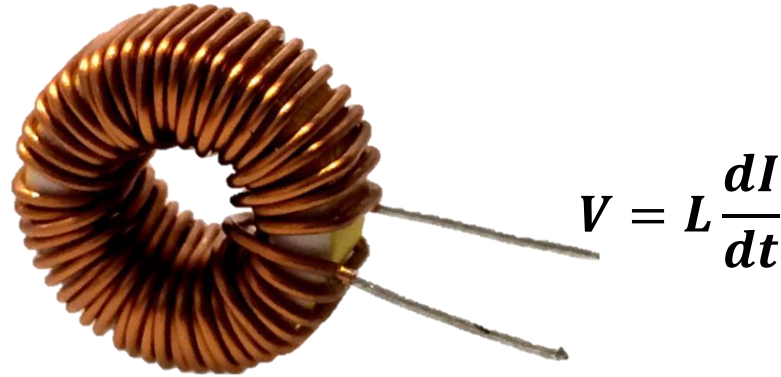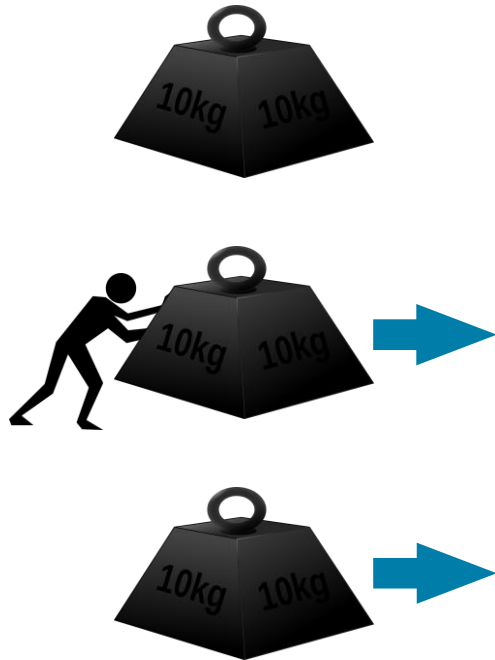Reactive elements store energy, and responds/behaves according to the **present AND the past!**



$$V = L \frac{dI}{dt}$$

Inductor **opposes sudden changes in current**

By **inducing** as much **voltage** is theoretically needed to **keep the current steady**







$$I = C \frac{dV}{dt}$$


Capacitor **opposes sudden changes in voltage**

By **generating** as much **current** is theoretically needed to **keep the voltage steady**
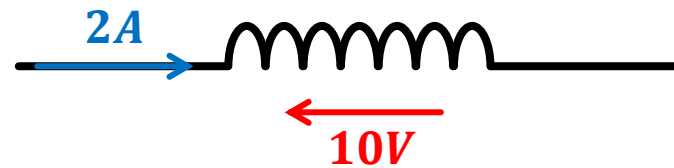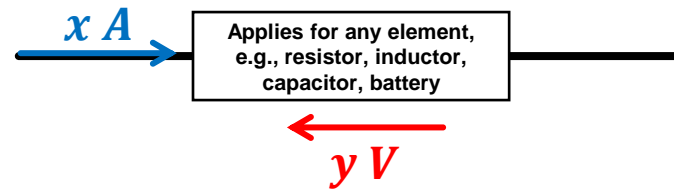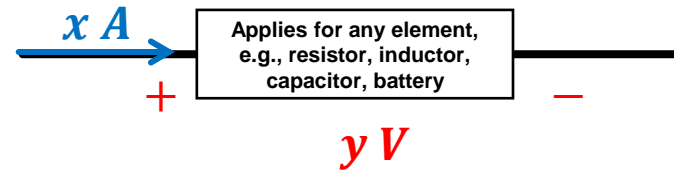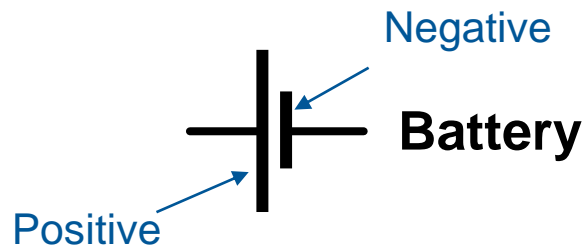
# Symbols & Notations used in circuit diagrams



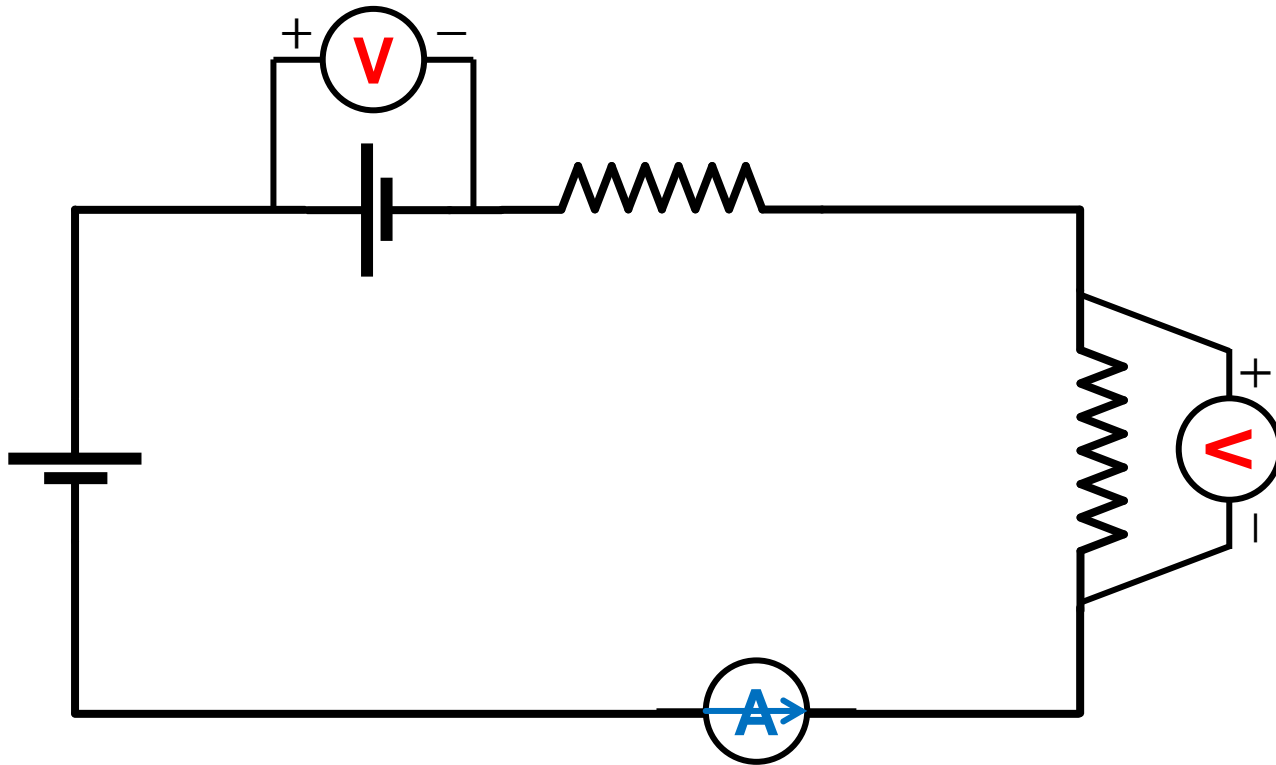A physical device that is added to an electrical circuit (that you want to observe) **without affecting** the working of the circuit



**Voltmeter** is added in **parallel to the element** (or group of elements) to measure the voltage across it

Its internal impedance is **very high**

$$R \rightarrow \infty \Omega$$


**Ammeter** is added in **series to the element** (or group of elements) to measure the current through it

Its internal impedance is **very low**

$$R \rightarrow 0 \Omega$$
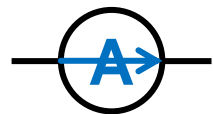
# Measurement of Current & Voltage

A physical device that is added to an electrical circuit (that you want to observe) **without affecting** the working of the circuit



Ammeter




Voltmeter




## Multimeter

Can measure voltage, current, resistance, diode test, continuity

# Application of Kirchhoff's Law

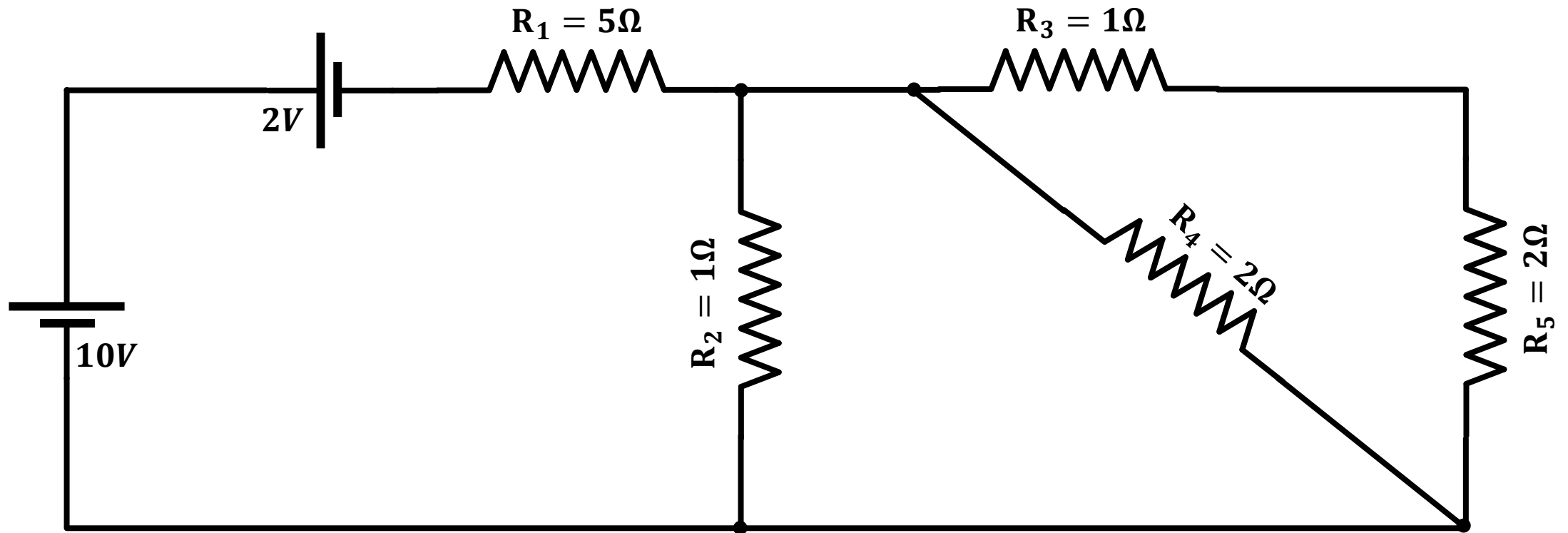

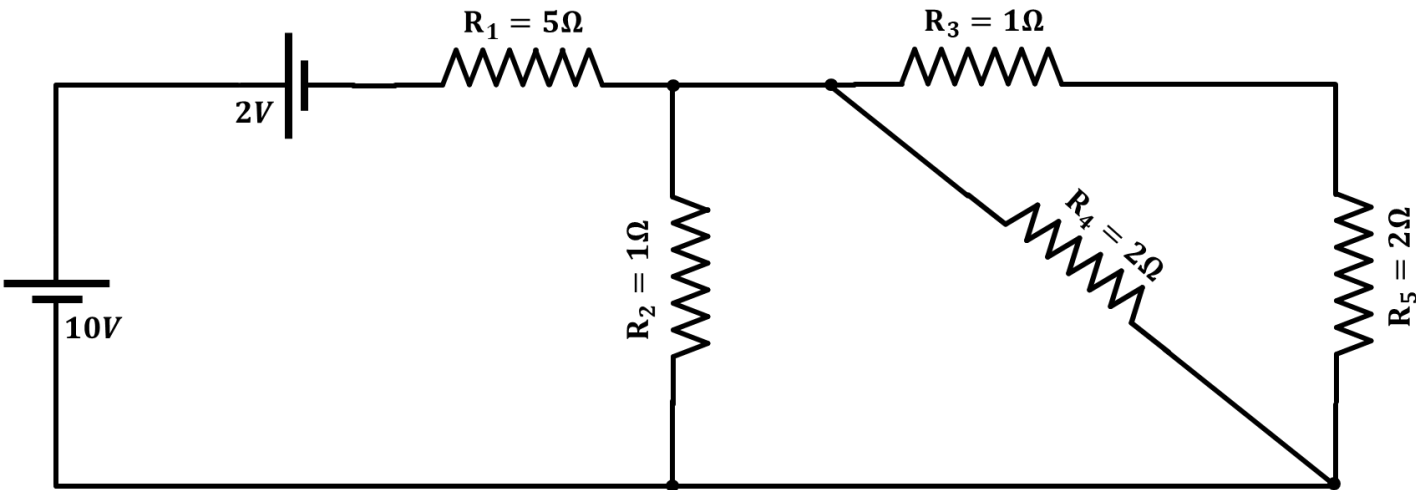*Find out the current and voltage of every resistor*



**Step 1 – Identify all the loops in the circuit**


**Step 2 – Assign a “loop current” variable**

**Step 3 – Identify “branch current” values (apply KCL)**

**Step 4 – Apply KVL to each loop**

**Step 5 – Apply Ohm's Law**

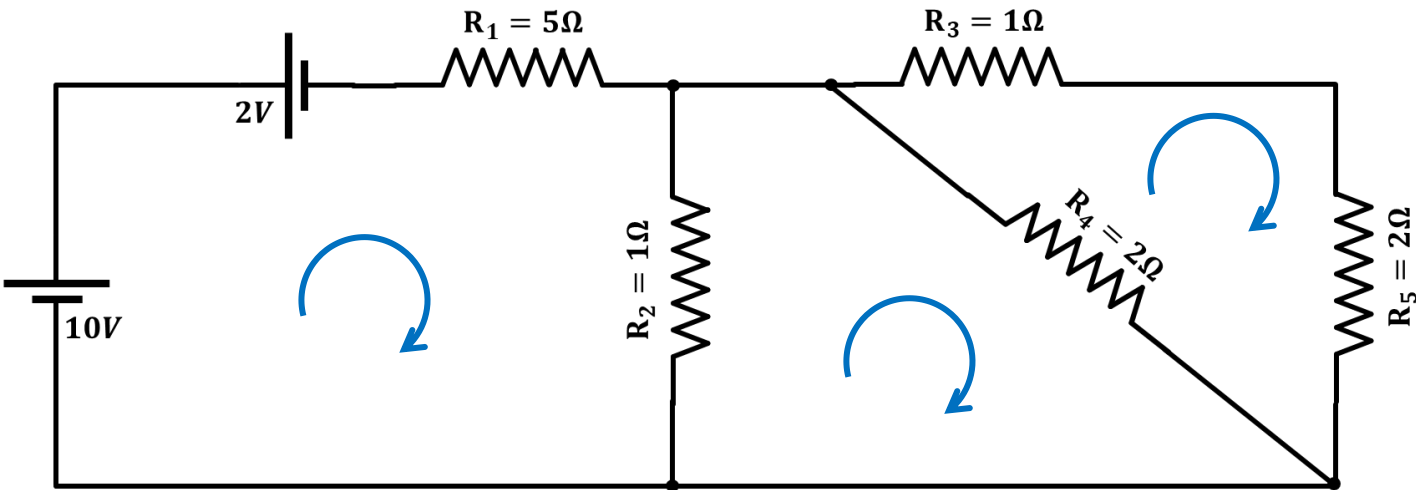**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**



**Step 1 – Identify all the loops in the circuit**

**Step 2 – Assign a “loop current” variable**


**Step 3 – Identify “branch current” values (apply KCL)**

**Step 4 – Apply KVL to each loop**

**Step 5 – Apply Ohm's Law**

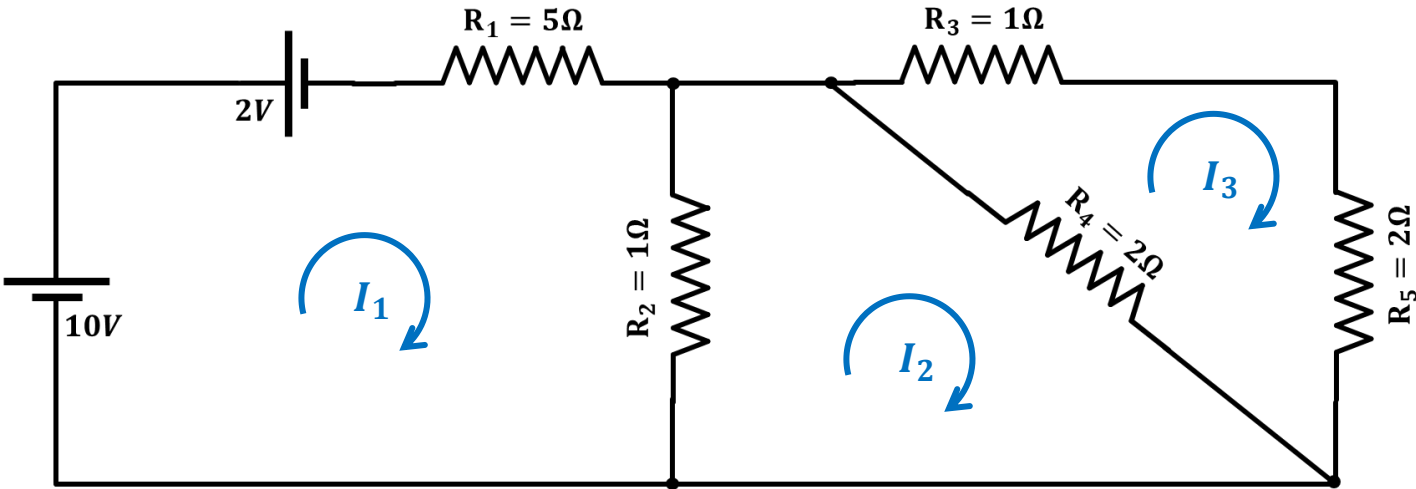**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**





**Step 1 – Identify all the loops in the circuit**


**Step 2 – Assign a “loop current” variable**

**Step 3 – Identify “branch current” values (apply KCL)**

**Step 4 – Apply KVL to each loop**

**Step 5 – Apply Ohm's Law**

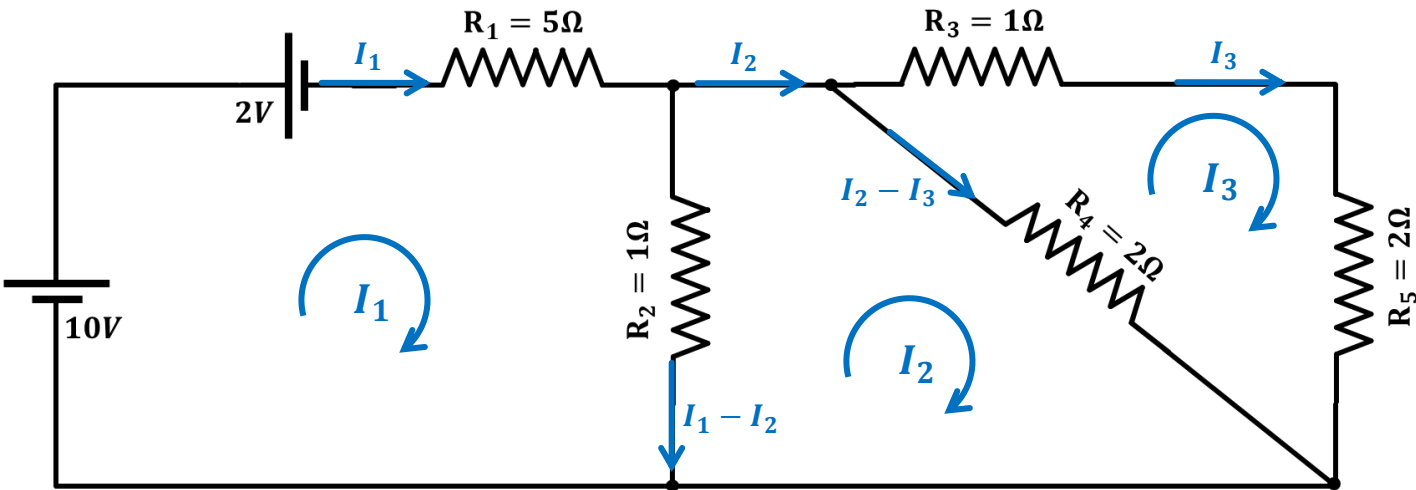**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**



**Step 1 – Identify all the loops in the circuit**

**Step 2 – Assign a “loop current” variable**


**Step 3 – Identify “branch current” values (apply KCL)**

**Step 4 – Apply KVL to each loop**

**Step 5 – Apply Ohm’s Law**

**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**

# Application of Kirchhoff's Law

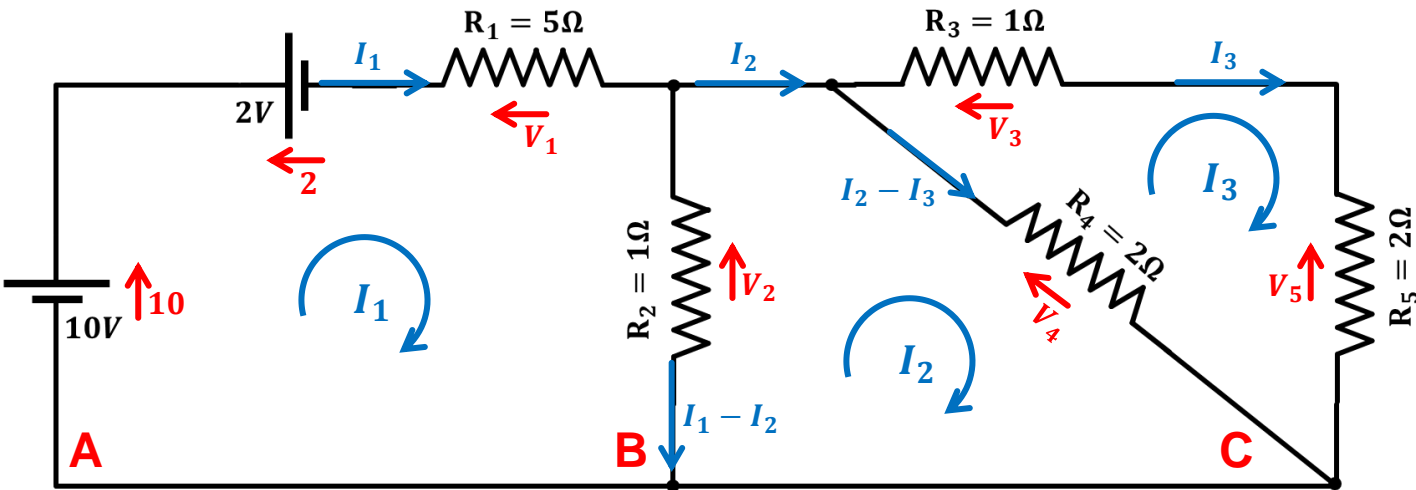

**Loop 1 KVL (node A origin):**

$$10 - 2 - V_1 - V_2 = 0$$

**Loop 2 KVL (node B origin):**

$$V_2 - V_4 = 0$$

**Loop 3 KVL (node C origin):**

$$V_4 - V_3 - V_5 = 0$$

~~Step 1 – Identify all the loops in the circuit~~


~~Step 2 – Assign a “loop current” variable~~

~~Step 3 – Identify “branch current” values (apply KCL)~~

~~Step 4 – Apply KVL to each loop~~

~~Step 5 – Apply Ohm’s Law~~

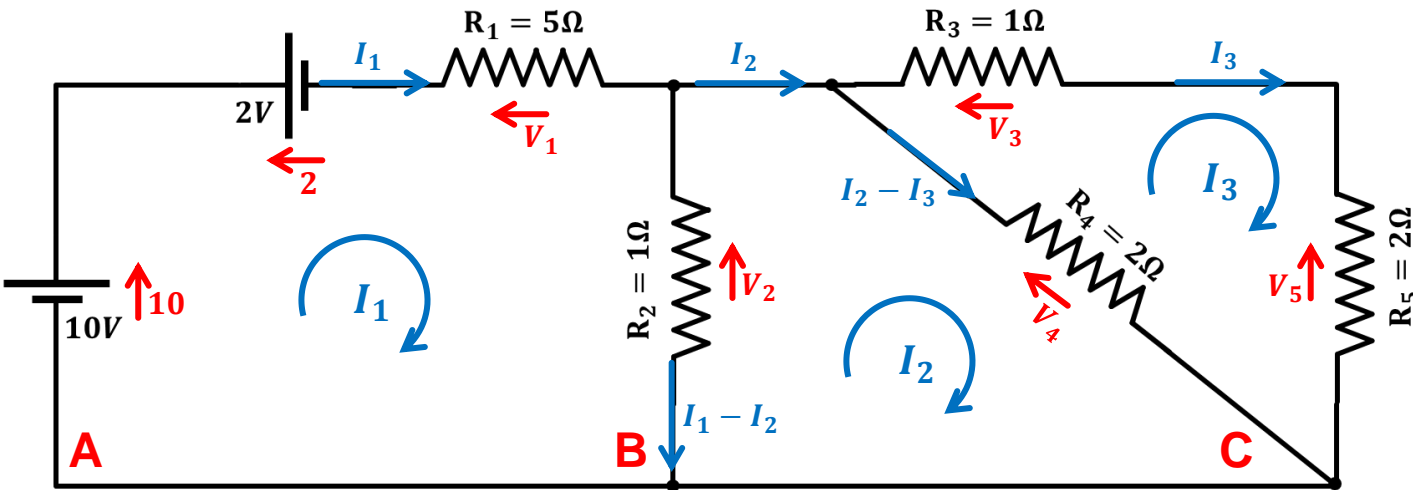**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**



~~Step 1 – Identify all the loops in the circuit~~

~~Step 2 – Assign a “loop current” variable~~

~~Step 3 – Identify “branch current” values (apply KCL)~~

~~Step 4 – Apply KVL to each loop~~

~~Step 5 – Apply Ohm’s Law~~

**Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations**

**Loop 1 KVL (node A origin):**

$$\begin{aligned} 10 - 2 - V_1 - V_2 &= 0 \\ 8 - I_1 R_1 - (I_1 - I_2) R_2 &= 0 \\ I_1 (R_1 + R_2) - I_2 R_2 &= 8 \\ I_1 (5 + 1) - I_2 1 &= 8 \\ 6I_1 - I_2 &= 8 \end{aligned}$$


**Loop 2 KVL (node B origin):**

$$\begin{aligned} V_2 - V_4 &= 0 \\ (I_1 - I_2) R_2 - (I_2 - I_3) R_4 &= 0 \\ I_1 R_2 - I_2 (R_2 + R_4) + I_3 R_4 &= 0 \\ I_1 1 - I_2 (1 + 2) + I_3 2 &= 0 \\ I_1 - 3I_2 + 2I_3 &= 0 \end{aligned}$$

**Loop 3 KVL (node C origin):**

$$\begin{aligned} V_4 - V_3 - V_5 &= 0 \\ (I_2 - I_3) R_4 - I_3 R_3 - I_3 R_5 &= 0 \\ I_2 R_4 - I_3 (R_3 + R_4 + R_5) &= 0 \\ I_2 2 - I_3 (1 + 2 + 2) &= 0 \\ 2I_2 - 5I_3 &= 0 \end{aligned}$$

# Application of Kirchhoff's Law

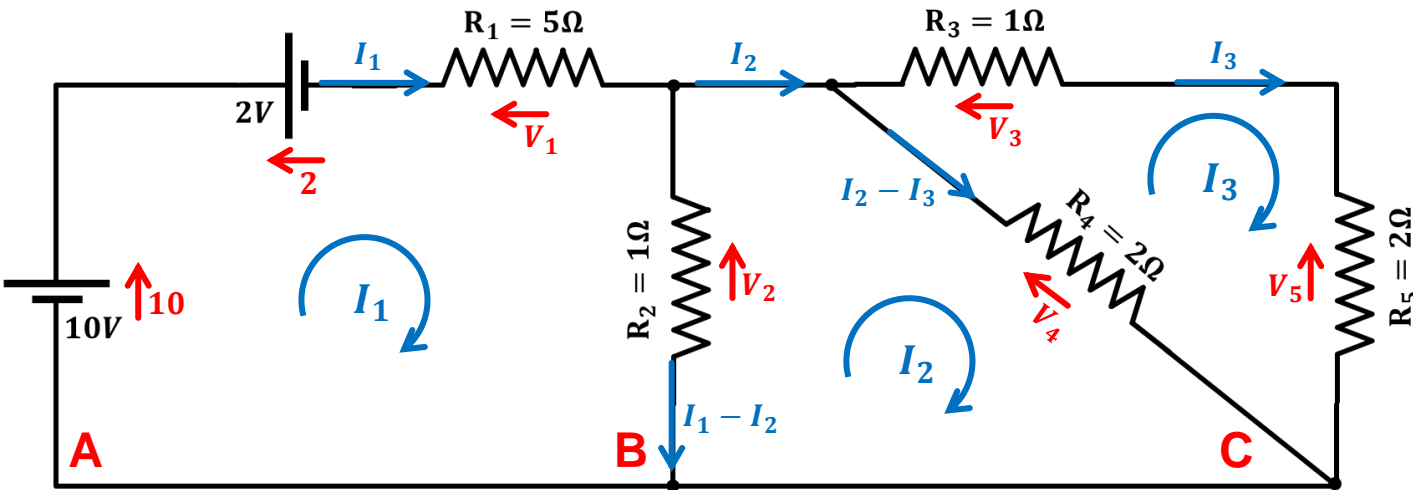

~~Step 1 – Identify all the loops in the circuit~~

~~Step 2 – Assign a “loop current” variable~~

~~Step 3 – Identify “branch current” values (apply KCL)~~

~~Step 4 – Apply KVL to each loop~~

~~Step 5 – Apply Ohm’s Law~~

~~Step 6 – Solve the linear system of equations – you can solve for  $n$  unknowns with  $n$  equations~~

$$6I_1 - I_2 = 8 \quad \text{Eq1}$$

$$I_1 - 3I_2 + 2I_3 = 0 \quad \text{Eq2}$$

$$2I_2 - 5I_3 = 0 \quad \text{Eq3}$$

**Apply 3(Eq1) – (Eq2):**

$$18I_1 - 3I_2 - I_1 + 3I_2 - 2I_3 = 24$$

$$17I_1 - 2I_3 = 24 \quad \text{Eq4}$$

**Apply (Eq3) + 2(Eq1):**

$$2I_2 - 5I_3 + 12I_1 - 2I_2 = 16$$

$$12I_1 - 5I_3 = 16 \quad \text{Eq5}$$

**Apply 12(Eq4) – 17(Eq5):**

$$204I_1 - 24I_3 - 204I_1 + 85I_3 = 288 - 272$$

$$61I_3 = 16$$

$$I_3 = 0.262A \quad \text{Eq6}$$

**Use (Eq6) in (Eq3)**

$$I_2 = \frac{5I_3}{2} = \frac{5(0.262)}{2} = 0.656A \quad \text{Eq7}$$


**Use (Eq7) in (Eq1)**

$$I_1 = \frac{8 + I_2}{6} = \frac{8 + 0.656}{6} = 1.443A \quad \text{Eq8}$$



- **Basic Concepts (& Recap)**
  - Charge, current, voltage
  - Ohm's/Kirchhoff's Laws
  - Power & Energy
  - Measurement of Voltage & Current
  - Electrical symbols & notations
  - Solution of a simple electrical circuit using just Ohm's and Kirchhoff's Laws
- **Electrical circuits**
  - **Series & Parallel**
  - **Combination** of series & parallel
  - **Example circuits** (to be discussed in upcoming seminar)
- **Further Reading**

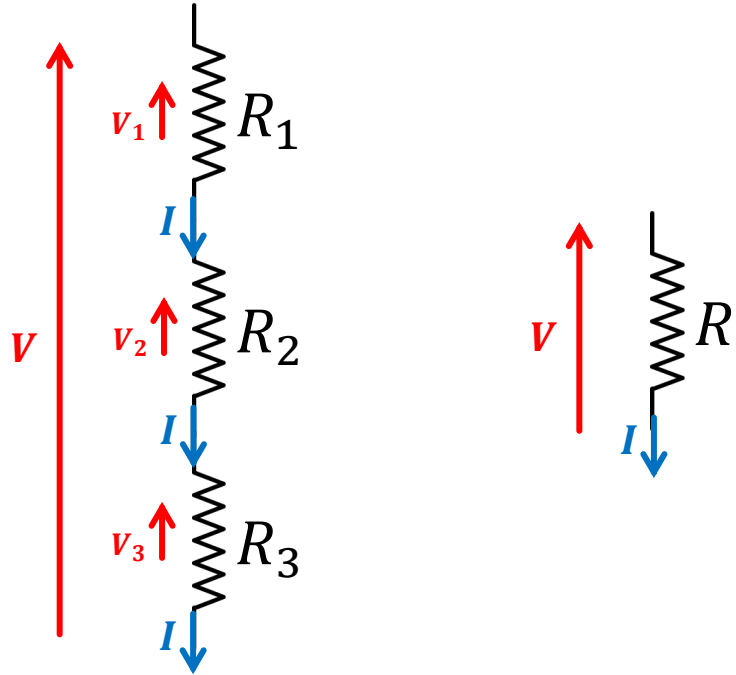**When two (or more) elements are connected together head-to-toe**



Same current flows through each element

$$I = I_1 = I_2 = I_3$$

Voltage gets split between elements


$$V = V_1 + V_2 + V_3$$

**More resistors in series, the harder it is for voltage source to push the current through**

Resistance value adds up

$$R = R_1 + R_2 + R_3$$

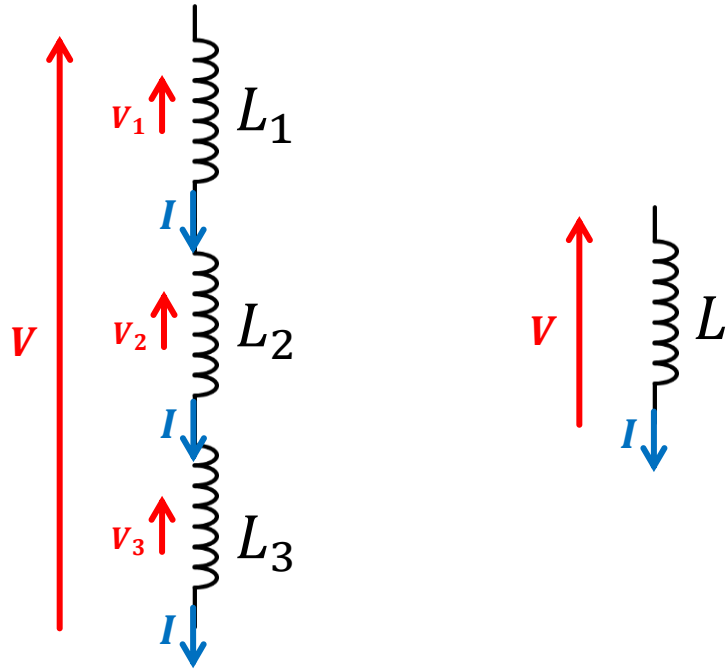**When two (or more) elements are connected together head-to-toe**



Same current flows through each element

$$I = I_1 = I_2 = I_3$$

Voltage gets split between elements

$$V = V_1 + V_2 + V_3$$


**More inductors in series, the harder it is for current to change rapidly**

Inductance value adds up

$$L = L_1 + L_2 + L_3$$



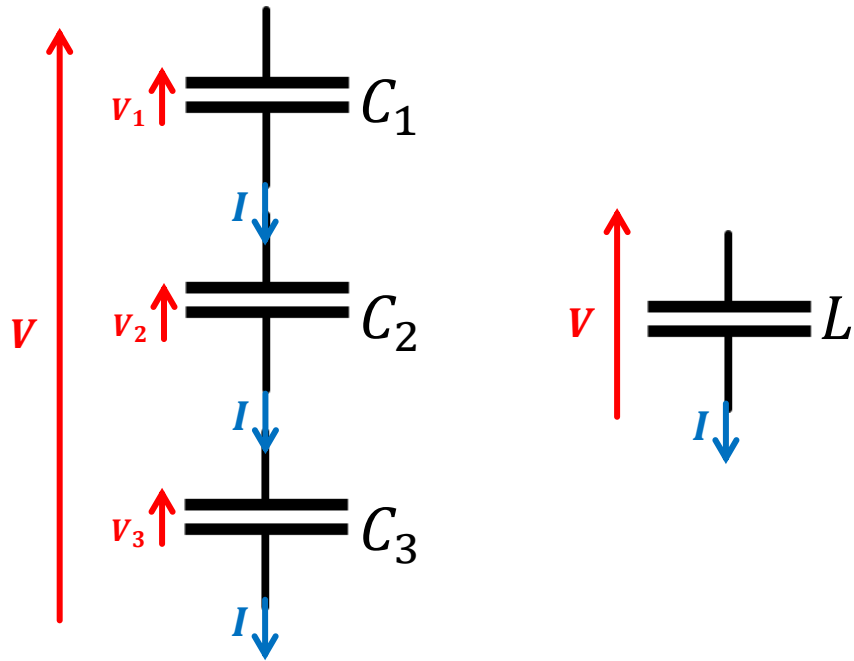**When two (or more) elements are connected together head-to-toe**



Same current flows through each element

$$I = I_1 = I_2 = I_3$$

Voltage gets split between elements

$$V = V_1 + V_2 + V_3$$

**More capacitors in series, the easier it is for voltage to change rapidly**



Apply KVL: in series, voltage gets divided, so each capacitor needs to oppose change of only part of the total voltage change

Reciprocal of capacitance value adds up

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
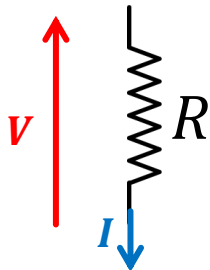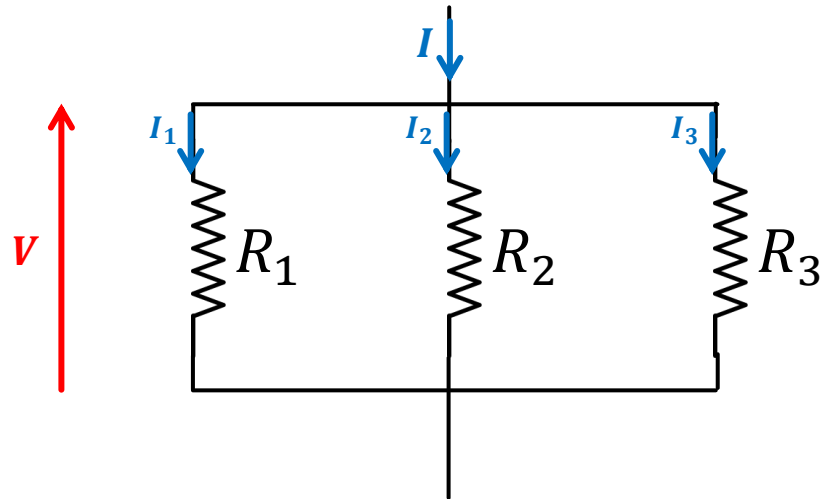
# Parallel Circuit

When two (or more) elements are connected together head-to-head



Same current flows through each element

$$I = I_1 + I_2 + I_3$$

Voltage gets split between elements


$$V = V_1 = V_2 = V_3$$

More resistors in parallel, more “effective paths” for electrons to pass through

Reciprocal of resistance value (conductance) adds up

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

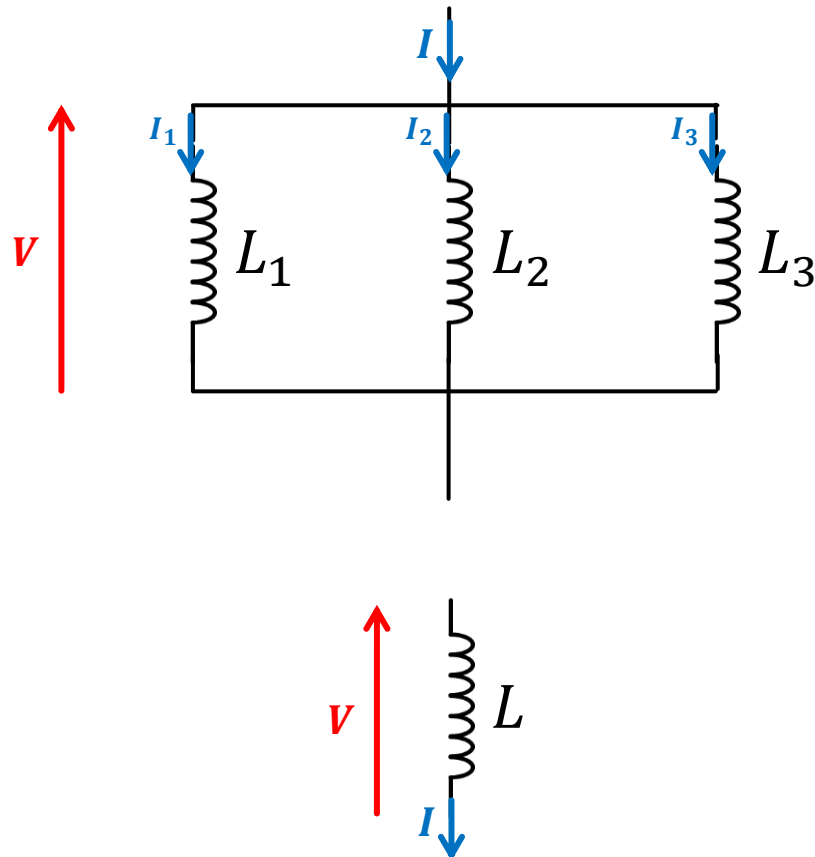**When two (or more) elements are connected together head-to-head**



Same current flows through each element

$$I = I_1 + I_2 + I_3$$

Voltage gets split between elements

$$V = V_1 = V_2 = V_3$$



**More inductors in parallel, easier it is for current to change rapidly**

Apply KCL: in parallel, current gets divided, so each inductor needs to oppose change of only part of the total current change

Reciprocal of inductance value adds up

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

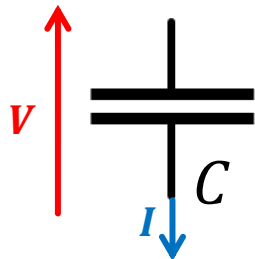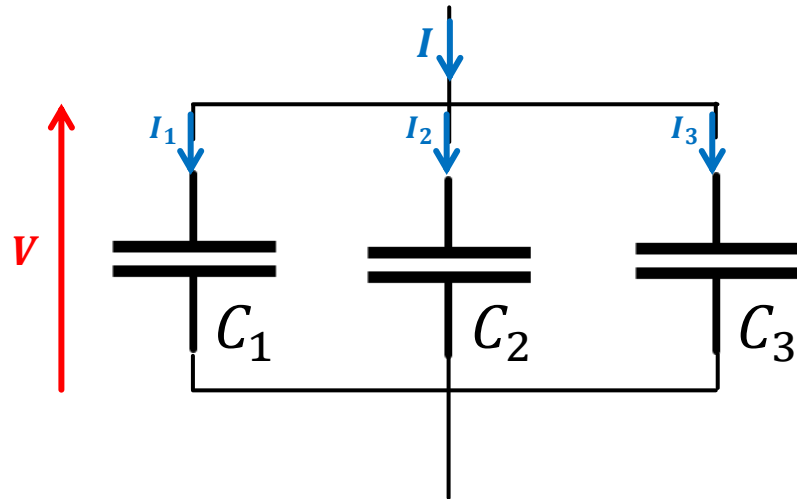**When two (or more) elements are connected together head-to-head**



Same current flows through each element

$$I = I_1 + I_2 + I_3$$

Voltage gets split between elements

$$V = V_1 = V_2 = V_3$$


**More capacitors in parallel, harder it is for voltage to change rapidly**

Reciprocal of inductance value adds up

$$C = C_1 + C_2 + C_3$$
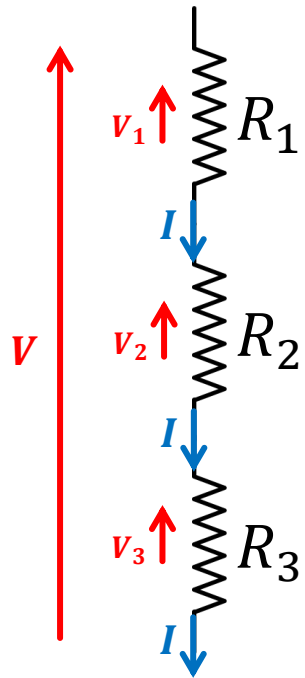
## Series

When two (or more) elements are connected together head-to-toe




Same current flows through each element

Voltage gets split:  $V = V_1 + V_2 + V_3$
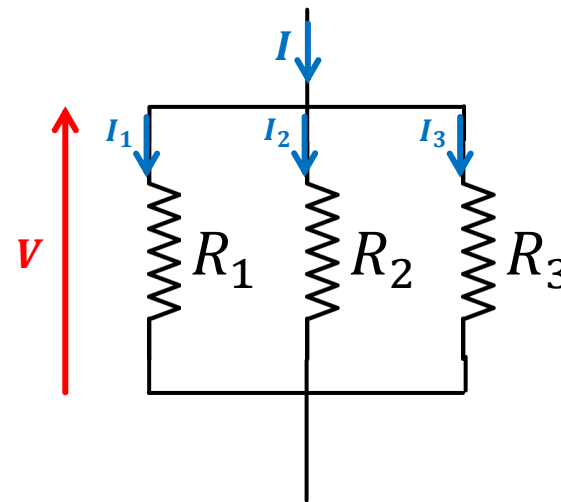
## Parallel

When two (or more) elements are connected head-to-head and toe-to-toe




Same voltage across each element

Current gets split:  $I = I_1 + I_2 + I_3$

## Series-Parallel

Combination of the both

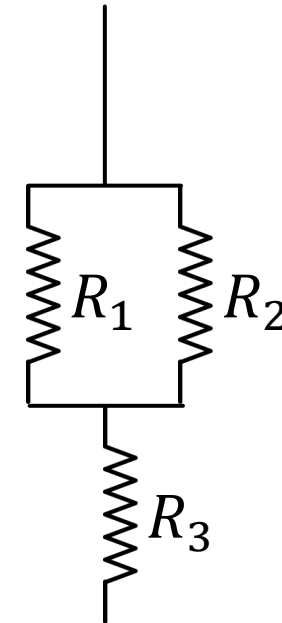


Break the circuit up into series and parallel and solve individually




# Types of Circuit

	Resistor	Inductor	Capacitor
V-I relation	$V = IR$	$V = L \frac{dI}{dt}$	$I = C \frac{dV}{dt}$
Power	$P = VI = \frac{V^2}{R} = I^2R$	$P = VI$	$P = VI$
Energy Stored	No energy stored	$E = \frac{1}{2} CV^2$	$E = \frac{1}{2} LI^2$
Series	$R = \sum R_i$	$L = \sum L_i$	$\frac{1}{C} = \sum \frac{1}{C_i}$
Parallel	$\frac{1}{R} = \sum \frac{1}{R_i}$	$\frac{1}{L} = \sum \frac{1}{L_i}$	$C = \sum C_i$

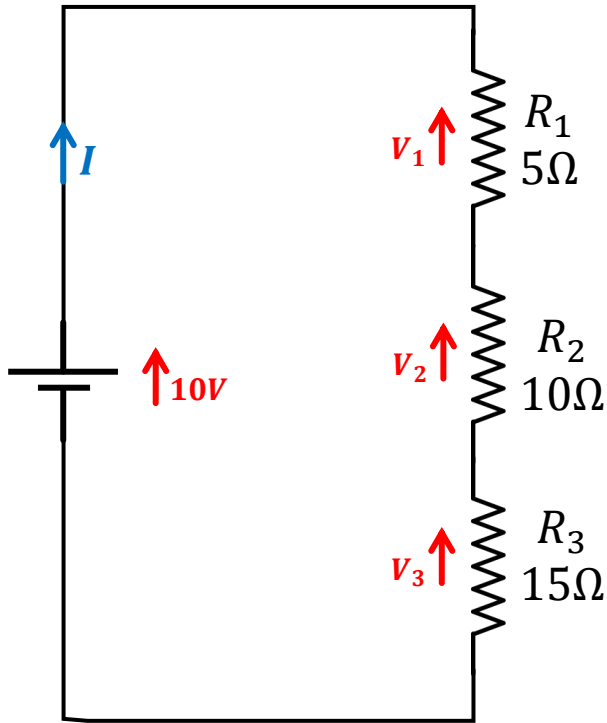
# Can you prove these formulae using Kirchhoff's and Ohm's Laws?



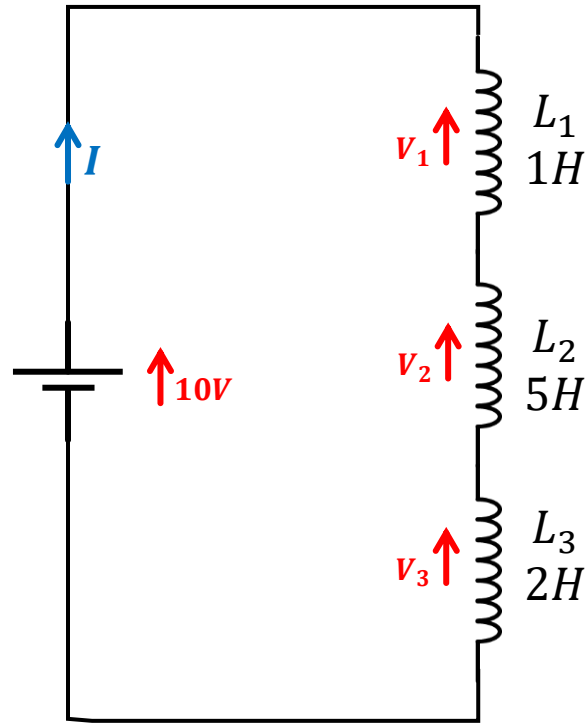- What is the values of  $V_1$ ,  $V_2$ ,  $V_3$ ?
- What is the value of  $I$ ?



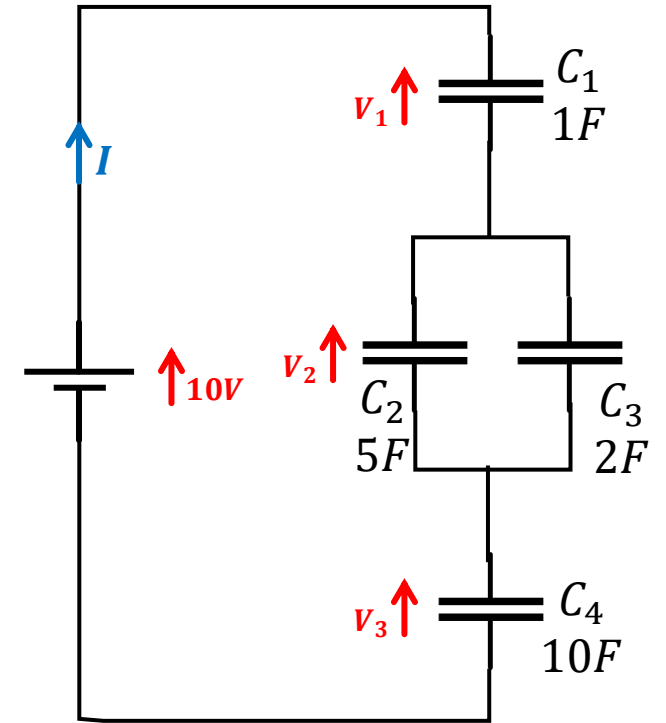- Prove that the set of three inductors can be equivalently replaced with an inductor with inductance of  $8H$



- Prove that the set of four capacitors can be equivalently replaced with a capacitor with capacitance of  $0.805F$



- **Basic Concepts (& Recap)**
  - Charge, current, voltage
  - Ohm's/Kirchhoff's Laws
  - Power & Energy
  - Measurement of Voltage & Current
  - Electrical symbols & notations
  - Solution of a simple electrical circuit using just Ohm's and Kirchhoff's Laws
- Electrical circuits
  - **Series & Parallel**
  - **Combination** of series & parallel
  - **Example circuits** (to be discussed in upcoming seminar)
- Further Reading





University of  
**Nottingham**



UK | CHINA | MALAYSIA

# Further Reading



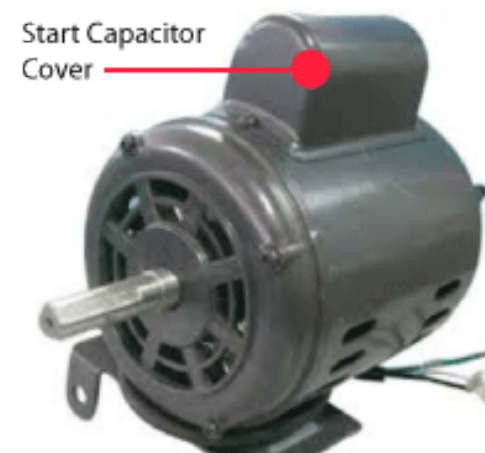
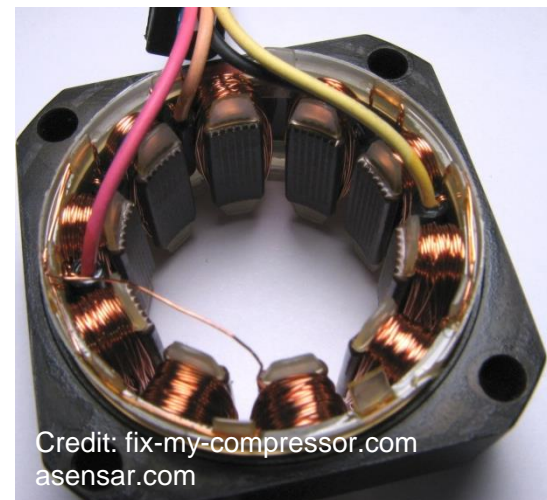
# Inductors & Capacitors – why bother?

- Almost all motors, actuators etc. have (unwanted) inductance due to their coils of wire (windings)
- Capacitors are widely used for filtering and smoothing signals, and creating phase shifts e.g. to start some kinds of motor


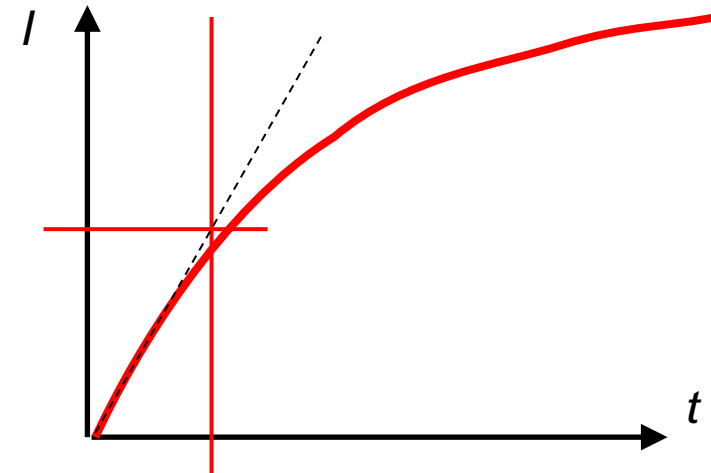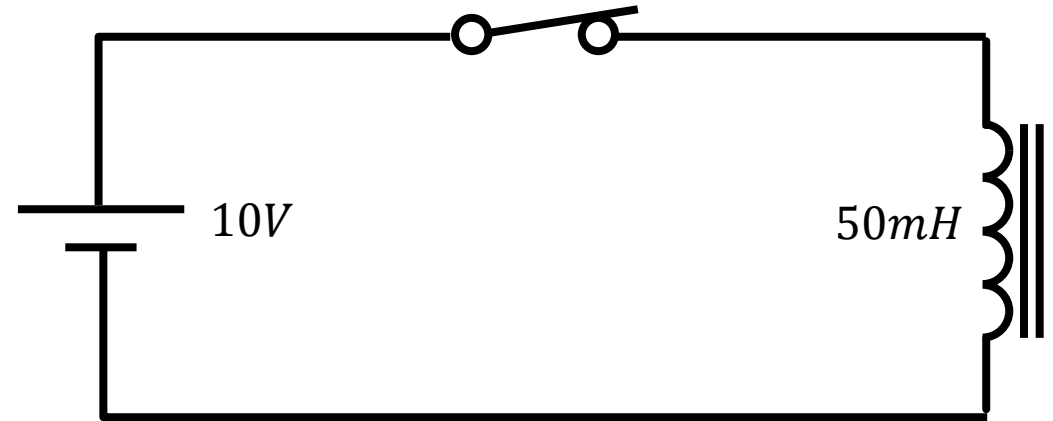
# Example of Inductor calculation

- A solenoid actuator has an inductance of  $50\text{mH}$ .  $0.01\text{s}$  after connecting it to a  $10\text{V}$  dc supply, what value of current is flowing? Ignore the resistance of the actuator.





# Example of Inductor calculation


$$V = L \frac{dI}{dt}$$
$$\frac{dI}{dt} = \frac{V}{L} = \frac{10}{50 \times 10^{-3}}$$
$$= 200 \text{ A/s}$$

So,
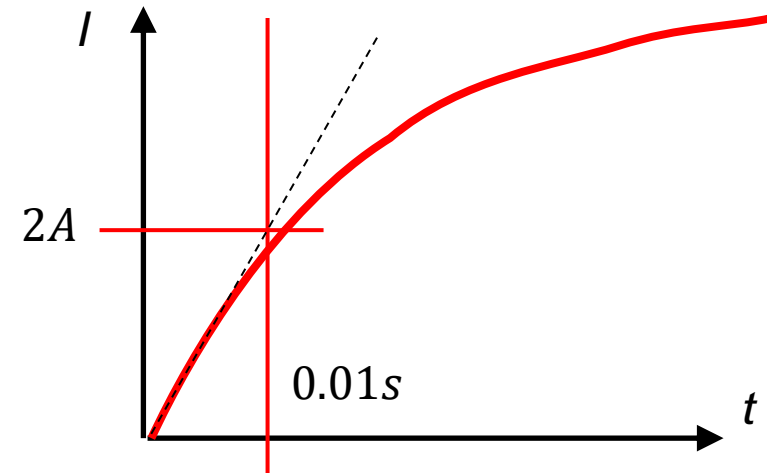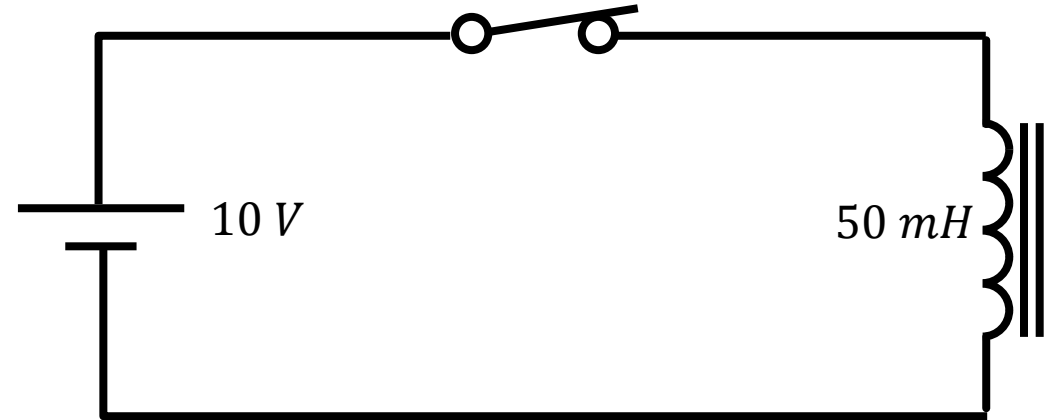
$$\Delta I \approx \left( \frac{dI}{dt} \right) \Delta t = 200 \times 0.01 = 2 \text{ A}$$


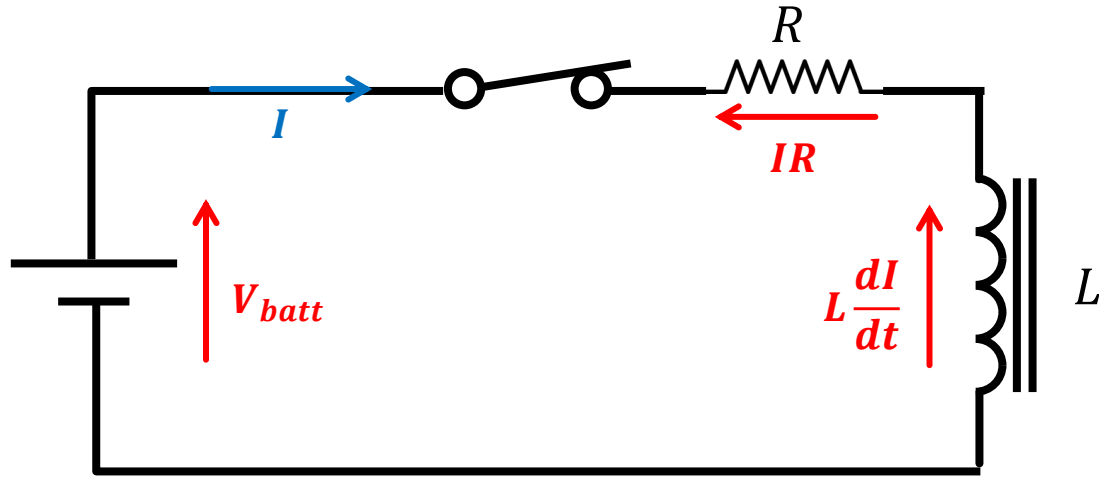
# Example of Inductor calculation – more realistic problem



$$V_{batt} = IR + L \frac{dI}{dt}$$


This is a differential equation, so we need to integrate this

$$V_{batt} dt = IRdt + LdI$$

$$V_{batt} \int dt = R \int I \cdot dt + L \int dI$$



After some complex calculus
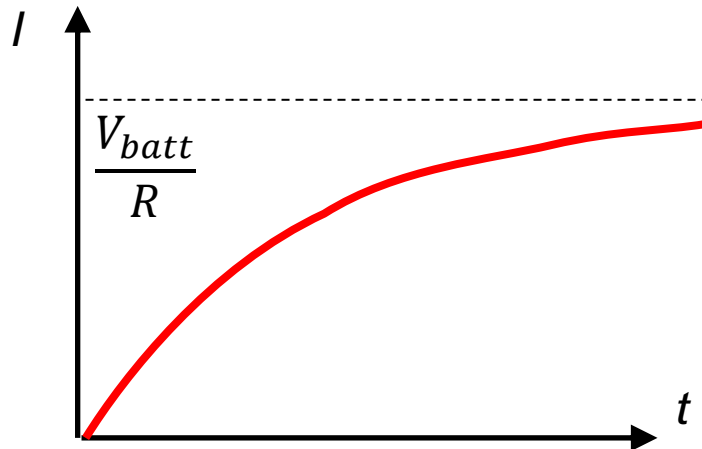
$$I(t) = \frac{V_{batt}}{R} (1 - e^{-\frac{R}{L}t})$$



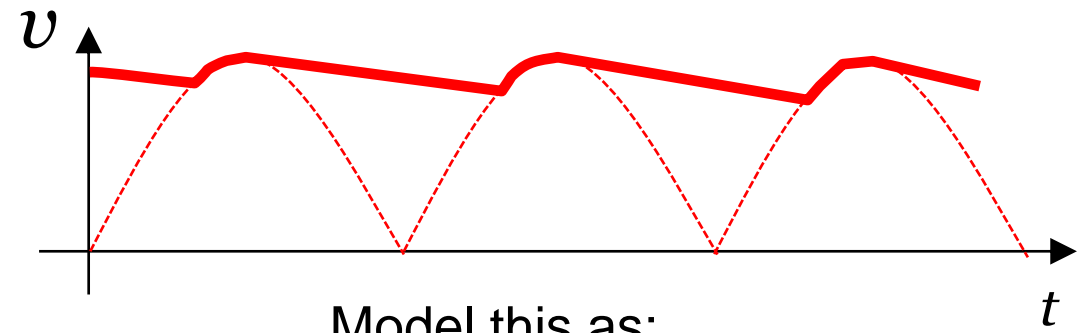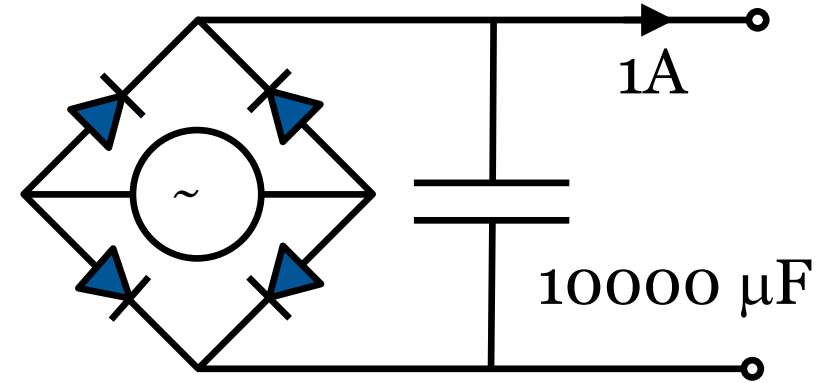
# Example of Capacitor calculation

- A  $10mF$  capacitor is used to smooth the output of a rectified  $50Hz$  power supply.
- Effectively, the capacitor is charged by a voltage peak to  $24V$  every  $0.01s$
- $1A$  is drawn from the power supply
- By what amount does the output voltage drop between charging peaks?
- What is mean voltage?
- Specifically, what is the voltage change  $\Delta v$  in  $0.01s$ ?
- What is  $V_{average}$ ?



Model this as:

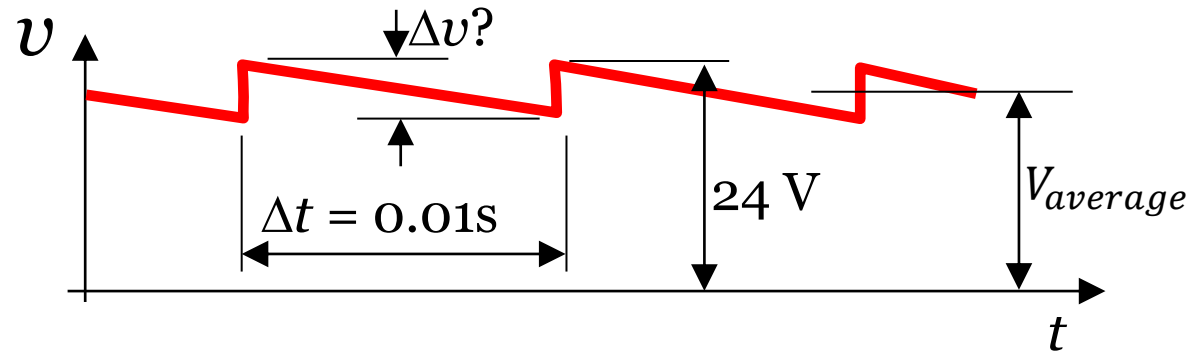

# Example of Capacitor calculation



$$I = C \frac{dV}{dt} = -1A$$

(current flowing out of cap so -ve)

$$\text{so } \frac{dV}{dt} = \frac{I}{C} = \frac{-1}{10000 \times 10^{-6}} = -10^2 \text{ Vs}^{-1}$$


$$\text{So } \Delta v = \frac{dV}{dt} \Delta t = -10^2 \times 0.01 = -1V$$
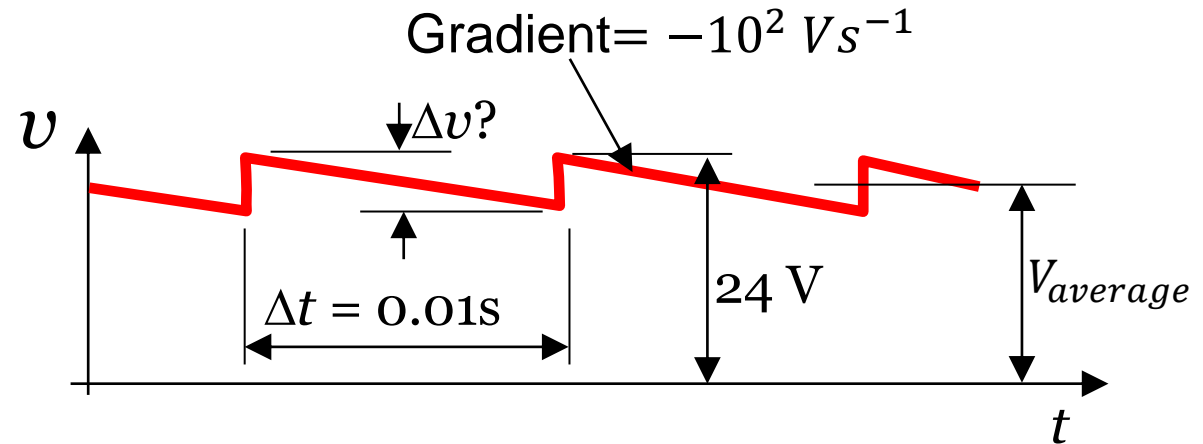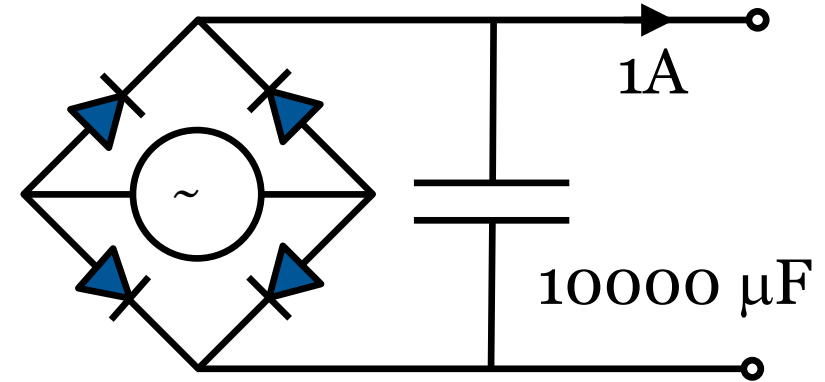
$$\text{Mean voltage is therefore } \frac{24 + (24 - 1)}{2} = \mathbf{23.5V}$$


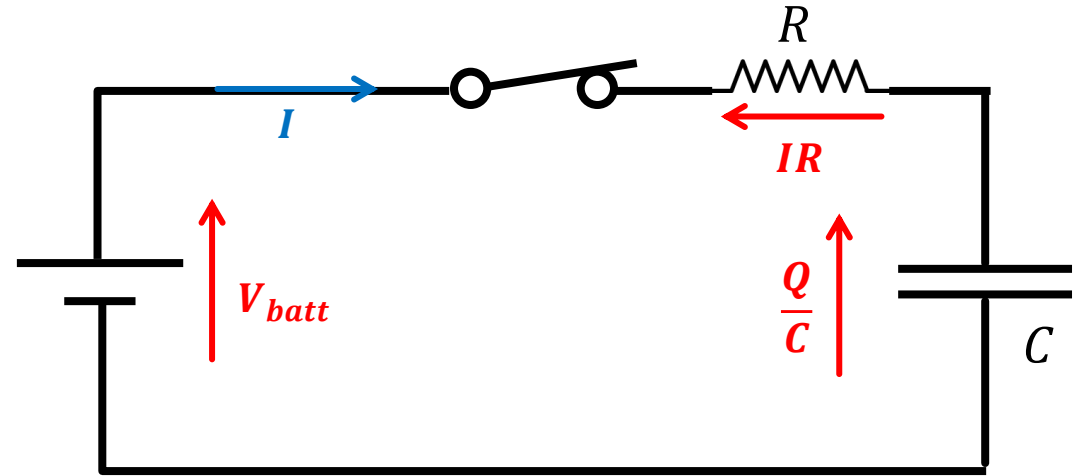
# Another example of Capacitor calculation

- A capacitor of value  $1000\mu F$  is connected to a  $12V$  battery via a  $10000\Omega$  resistor. At what rate does the capacitor voltage increase initially?





# Another example of Capacitor calculation

Initially: voltage across capacitor = 0

So

$$V_{batt} - IR - 0 = 0$$


$$I = \frac{V_{batt}}{R}$$

But

$$I = \frac{dQ}{dt} = C \frac{dV_{cap}}{dt}$$

So
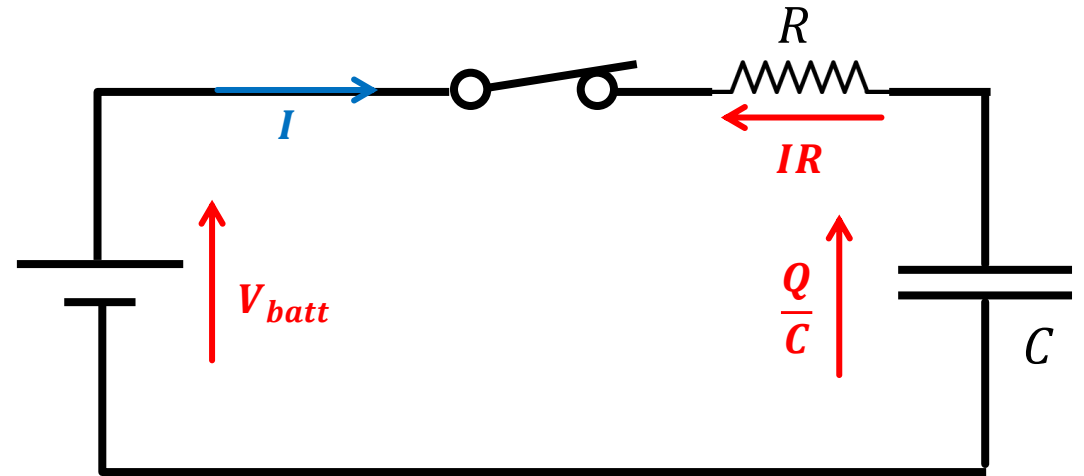
$$\frac{dV_{cap}}{dt} = \frac{V_{batt}}{RC} = \frac{12}{10000 \times 1000 \times 10^{-6}} = 1.2 \text{ V s}^{-1}$$



# Another example of Capacitor calculation

